

Logic Design with Verilog IV: Design Example (Bus) and Synthesizable Code

Jae W. Lee (jaewlee@snu.ac.kr)

Department of Computer Science and Engineering

Seoul National University


Slide credits: Prof. Ming-Bo Lin (Digital System Designs and Practices Using Verilog HDL and FPGAs)

Outline


- Design example: bus
 - Tri-state based bus
 - Multiplexer-based bus
 - Bus arbitration
 - Simple bus controller example
- Verilog synthesis flow
 - Design environment and constraints
 - Architecture of logic synthesizers
 - Synthesizable operators and constructs
 - Logic optimization

Bus: A Basic Microprocessor System

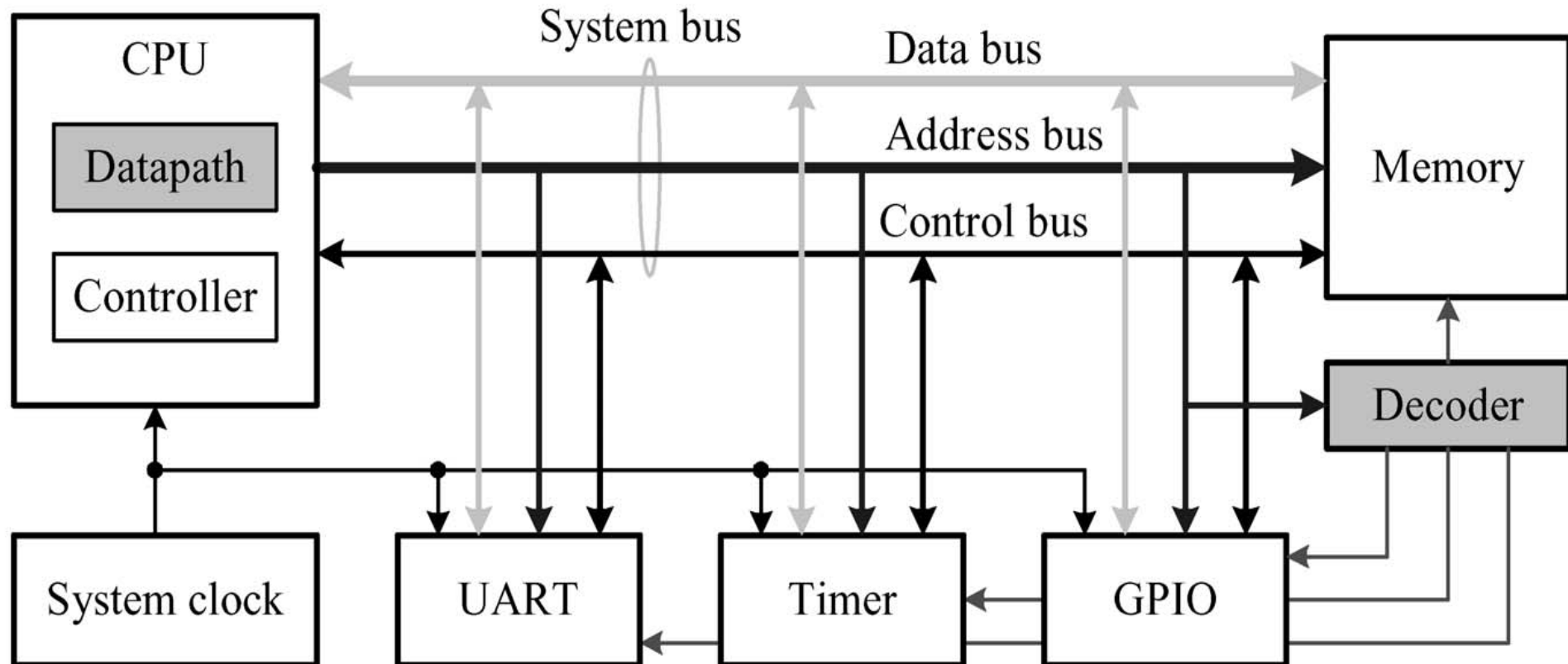- Bus: a set of wires used to transport information between two or more devices in a digital system



Bus: A Tristate Bus

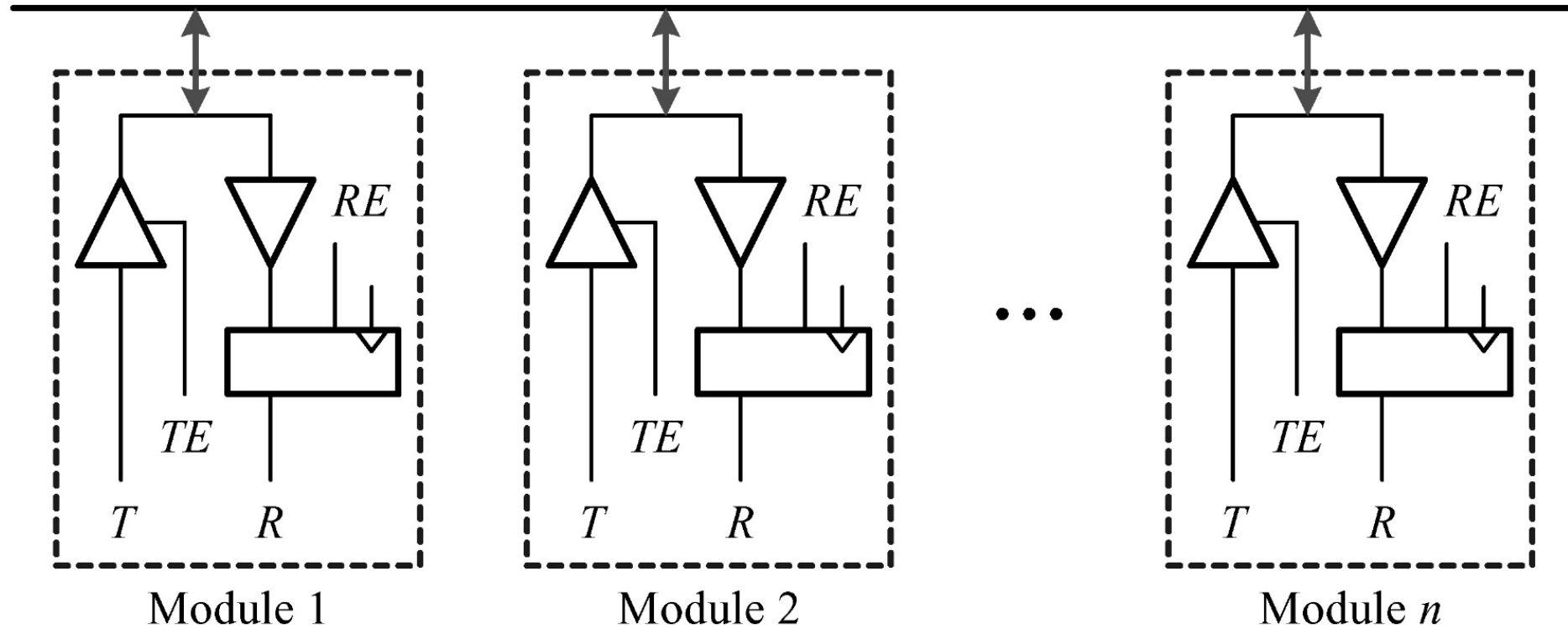


T : transmit TE : transmit enable R: receive RE : receive enable

Bus: A Tristate Bus

- Verilog code

```
// a tristate bus example
module tristate_bus (data, enable, qout);
parameter          N = 2;    // define bus width
input               enable;
input [N-1:0]       data;
output [N-1:0]      qout;

 // the body of tristate bus
assign qout = enable ? data : {N{1'bz}};
endmodule
```



Bus: A Bidirectional Bus

// a bidirectional bus example

```
module bidirectional_bus (data_to_bus, send, receive, data_from_bus, qout);
```

```
parameter          N = 2;          // define bus width
```

```
input              send, receive;
```

```
input [N-1:0]      data_to_bus;
```

```
output [N-1:0]     data_from_bus;
```



```
inout [N-1:0]      qout;          // bidirectional bus
```

// the body of tristate bus

```
assign data_from_bus = receive ? qout : {N{1'bz}};
```


```
assign qout = send ? data_to_bus : {N{1'bz}};
```

```
endmodule
```

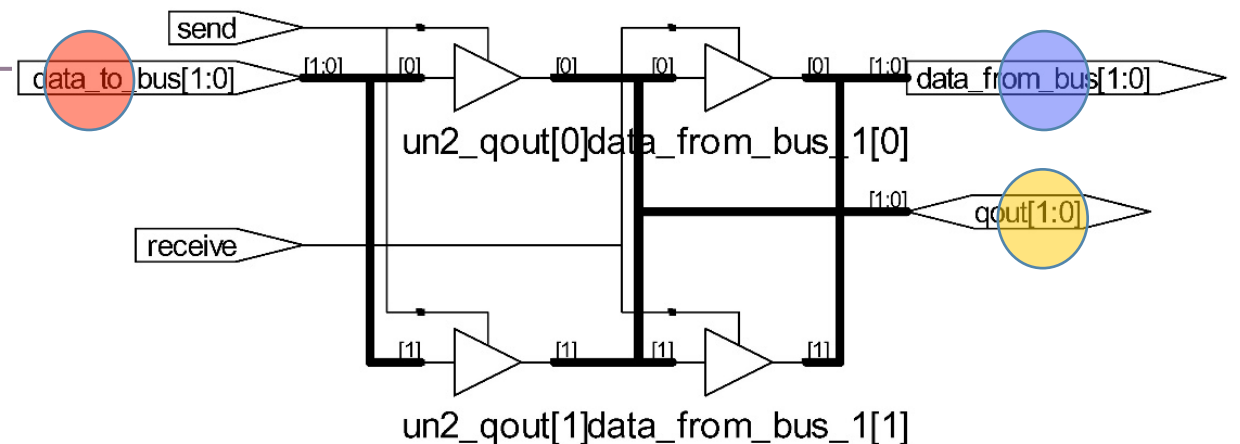 


Bus: A Bidirectional Bus

```
// a bidirectional bus example
module bidirectional_bus (data_to_bus, send, receive, data_from_bus, qout);
parameter          N = 2;          // define bus width
input              send, receive;
input  [N-1:0]     data_to_bus;
output [N-1:0]     data_from_bus;
inout  [N-1:0]     qout;             // bidirectional bus
// the body of tristate bus
assign data_from_bus = receive ? qout : {N{1'bz}};
assign qout = send ? data_to_bus : {N{1'bz}};
endmodule
```

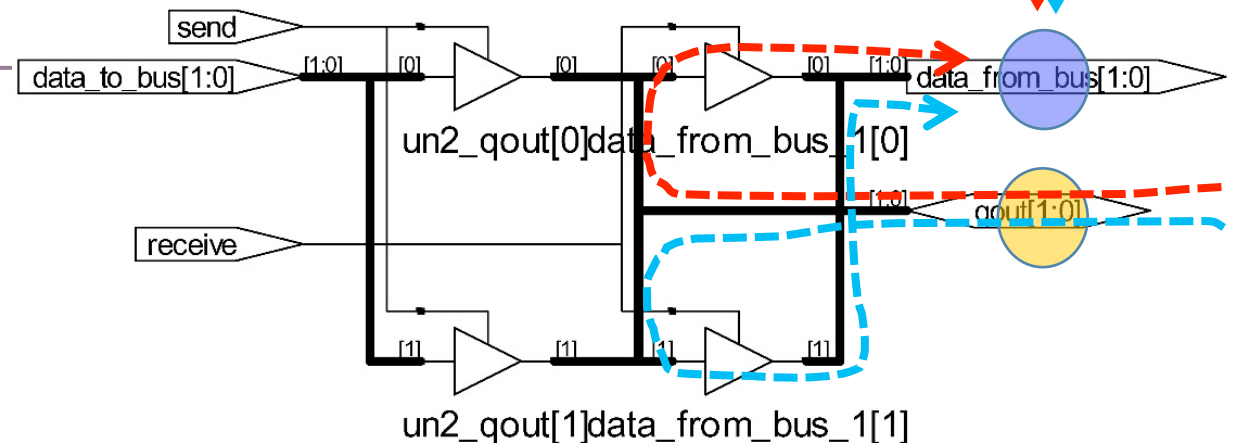


Bus: A Multiplexer-Based Bus

 


The propagation delay is much less than the tristate bus when the modules attached to it are large enough
It can avoid the large amount of capacitive load by the tristate bus

Bus: Arbitration

 - Bus arbitration
 - The operation that chooses one transmitter from multiple ones attempting to transmit data on the bus
- Types of bus arbitration schemes
 - Daisy-chain: fixed priority
 - Radial: fixed, round robin, etc.




(a) Daisy-chain arbitration

 

(b) Radial arbitration

Bus: Simple bus controller example

■ Overview

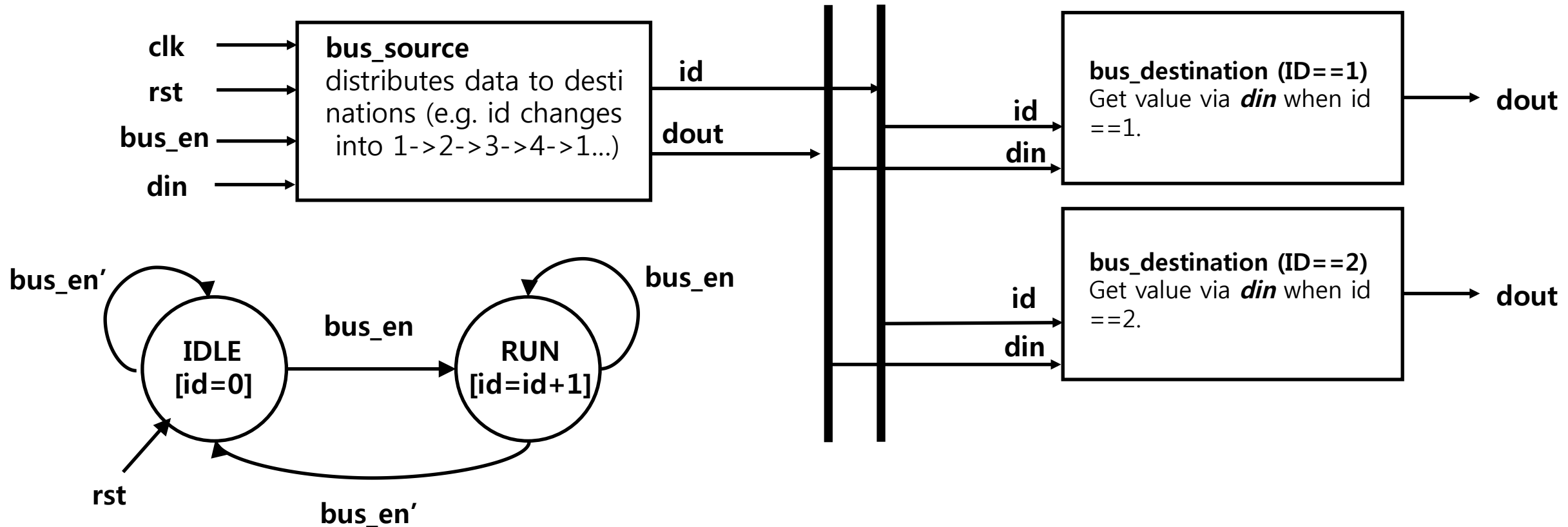


Bus: Simple bus controller example

■ Source

```
module bus_source (clk, rst, bus_en, din, dout, id);
parameter NUM_DESTINATION=2;
input          clk, rst, bus_en;
input [31:0]   din;
output [31:0]  dout;
output reg [2:0] id;
reg [2:0]      sel;
reg           sel_rst;
reg [1:0]      curr_state, next_state;
parameter IDLE=2`d0, RUN=2`d1;
assign dout = din;

//part 1: initialize to state INIT and update current state register
always @(posedge clk or posedge rst)
    if(rst) curr_state <= IDLE; else curr_state <= next_state;

 //part 2: determine next state
always @(*)
    case(curr_state)
        IDLE: if(bus_en) next_state <= RUN; else next_state <= curr_state;
        RUN:  if(bus_en) next_state <= curr_state; else next_state <= IDLE;
    endcase
```



Bus: Simple bus controller example

■ Source (cont'd)

```
//part 3: determine output and internal register
```

```
//Output id is determined
```

```
always @(*)
```

```
case(curr_state)
```

```
  IDLE: id <= 0;
```

```
  RUN: if(bus_en) id <= sel; else id <= 0;
```

```
  default: id <= id;
```

```
endcase
```

```
//If sel_rst == 0, increment id counter (sel)
```

```
always @(posedge clk or posedge sel_rst)
```

```
  if(sel_rst) sel <= 0; else if(sel==NUM_DESTINATION) sel <= 1; else sel <= sel + 1;
```

```
//Setting internal register to control the counter
```

```
always @(*)
```


```
case(curr_state)
```

```
  IDLE: if(bus_en) sel_rst <= 0; else sel_rst <= 1;
```

```
  RUN: if(bus_en) sel_rst <= 0; else sel_rst <= 1;
```

```
  default: sel_rst <= sel_rst;
```

```
endcase
```

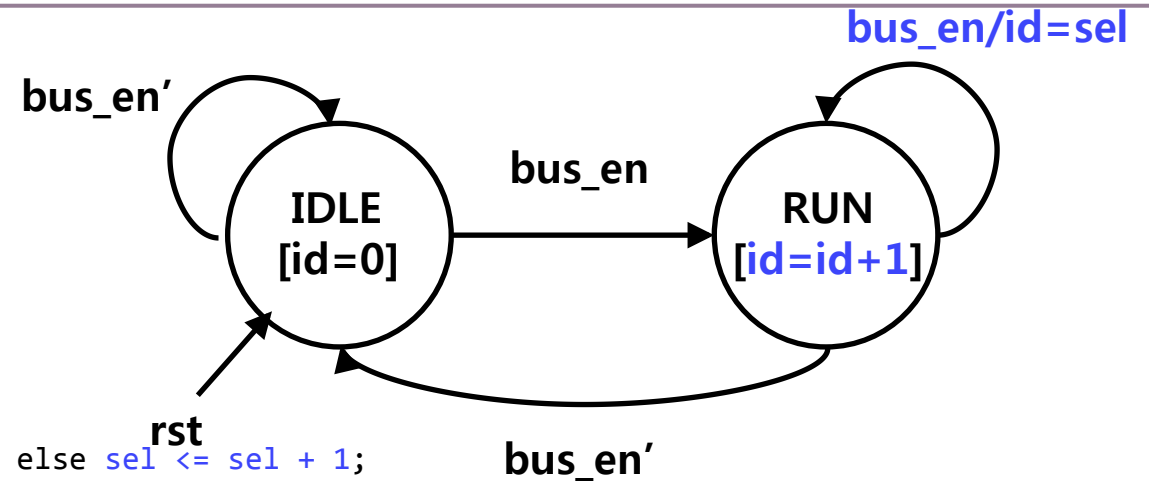

Bus: Simple bus controller example


■ Destination

```
// a bidirectional bus example
module bus_destination (clk, rst, id, din, dout);
parameter ID=1;
input          id;
input  [31:0]  din;
output [31:0]  dout;

wire [31:0] internal_din;
wire en;

assign internal_din = (id==ID) ? din : 0;
assign en = (id==ID) ? 1 : 0;

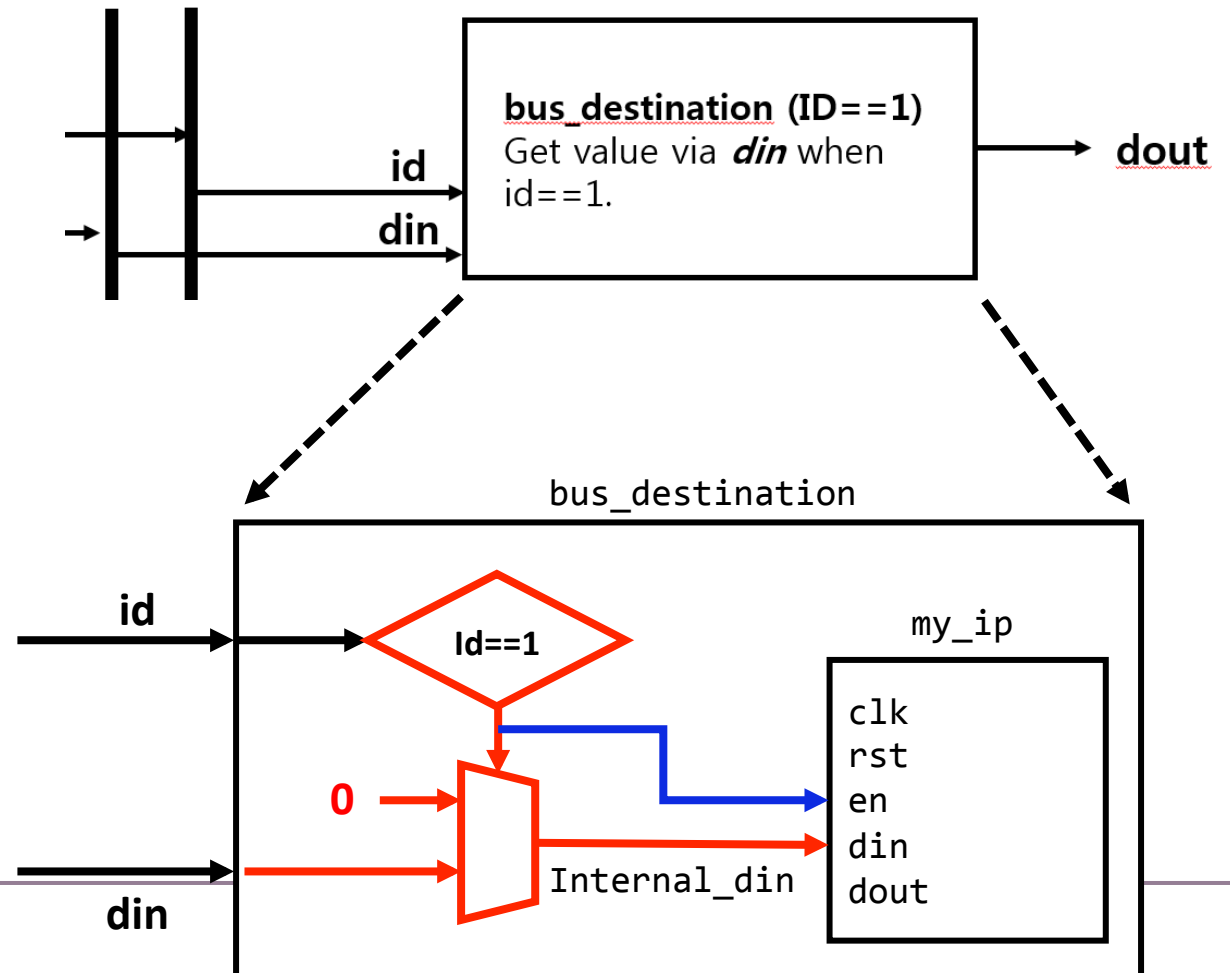
MY_IP my_ip (
    .clk(clk),
    .rst(rst),
    .en(en),
    .din(internal_din),
    .dout(dout)
);
endmodule
```



Outline



- Design example: bus
 - Tri-state based bus
 - Multiplexer-based bus
 - Bus arbitration
 - Simple bus controller example
- Verilog synthesis flow
 - Design environment and constraints
 - Architecture of logic synthesizers
 - Synthesizable operators and constructs
 - Logic optimization

Logic Synthesizer

 


```

module sequence_detector_mealy (clk, reset_n, x, z);
  input      clk, reset_n, x; output reg z;
  reg [1:0]  present_state, next_state; // present state and next state
  parameter A = 2'b00, B = 2'b01, C = 2'b10, D = 2'b11;
  // part 1: initialize to state A and update present state register
  always @(posedge clk or negedge reset_n)
    if(!reset_n) present_state <= A; else present_state <= next_state;
  // part 2: determine next state
  always @(present_state or x)
    case(present_state)
      A: if (x) next_state = A; else next_state = B;
      B: if (x) next_state = C; else next_state = B;
      C: if (x) next_state = A; else next_state = D;
      D: if (x) next_state = C; else next_state = B;
    endcase
  // part 3: evaluate output z
  always @(present_state or x) // mealey machine
    case (present_state)
      A: if (x) z = 1'b0; else z = 1'b0;
      B: if (x) z = 1'b0; else z = 1'b0;
      C: if (x) z = 1'b0; else z = 1'b0;
      D: if (x) z = 1'b1; else z = 1'b0;
    endcase
endmodule
  
```

 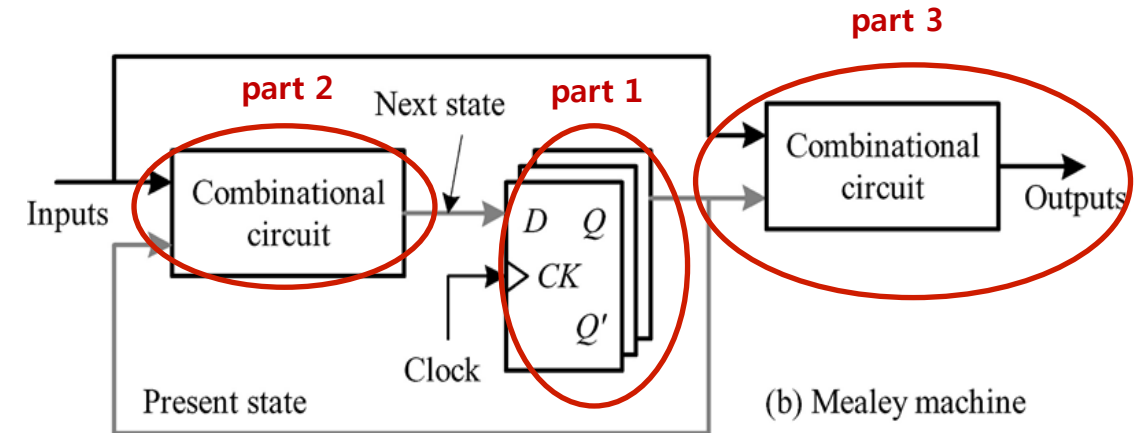


Logic Synthesis Environment

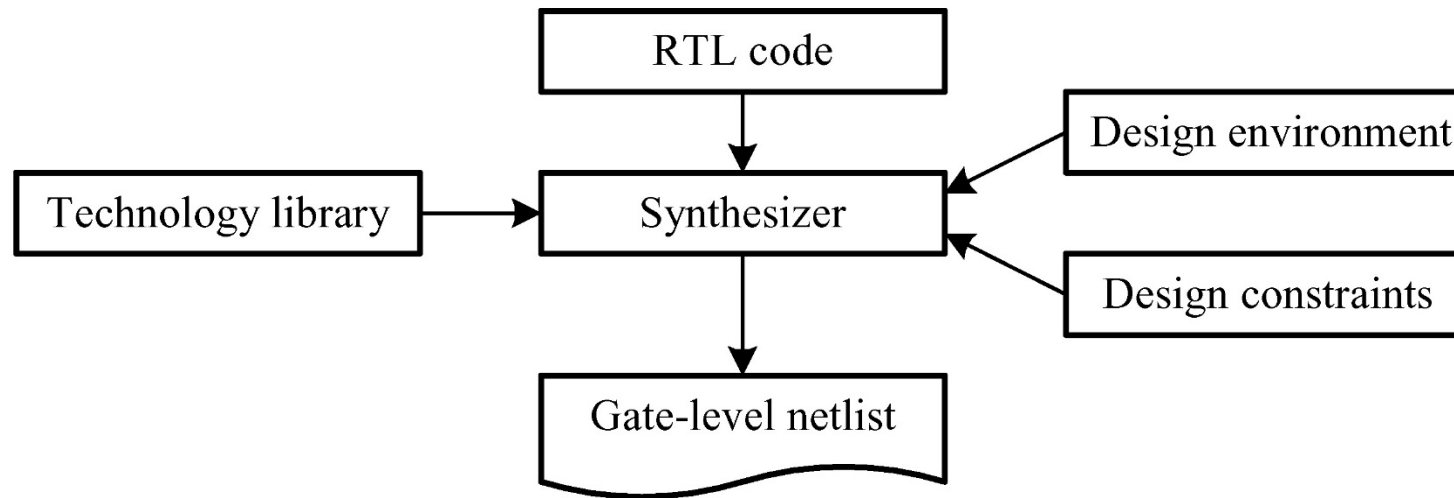- Design environment
- Design constraints
- RTL code
- Technology library



Design Environment

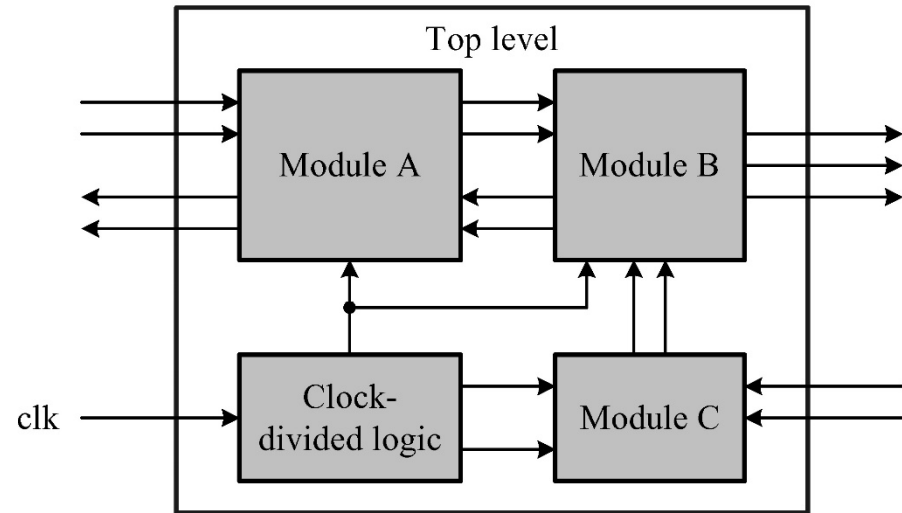
- The process parameters
 - Technology library
 - Operating conditions
 - Process of technology
 - Operating voltage and temperature
- I/O port attributes
 - Drive strength of input port
 - Capacitive loading of output port
 - Design rule constraints
- Statistical wire-load model
 - Pre-layout static timing analysis



Design Constraints


- Include clock, input delay and output delay
 - e.g., 100MHz, every input/output has 0.5ns delay
- Clock signal specification
 - Period : clock period
 - Duty cycle : proportion of time during which a component is operated
 - Transition time : rise time and fall time of the clock
 - Skew : clock network delay
- Delay specifications
 - Maximum
 - Minimum

Architecture of Logic Synthesizers

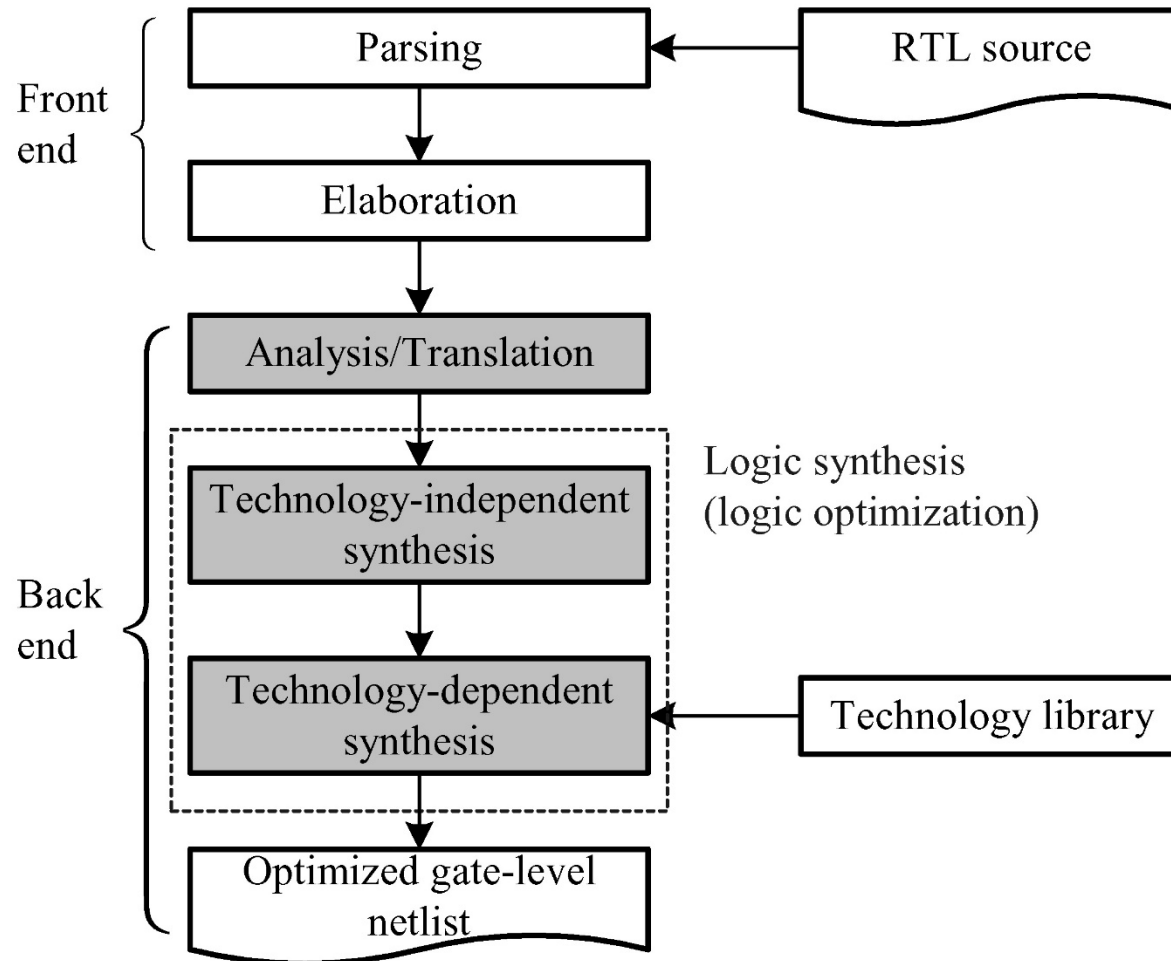

Architecture of Logic Synthesizers

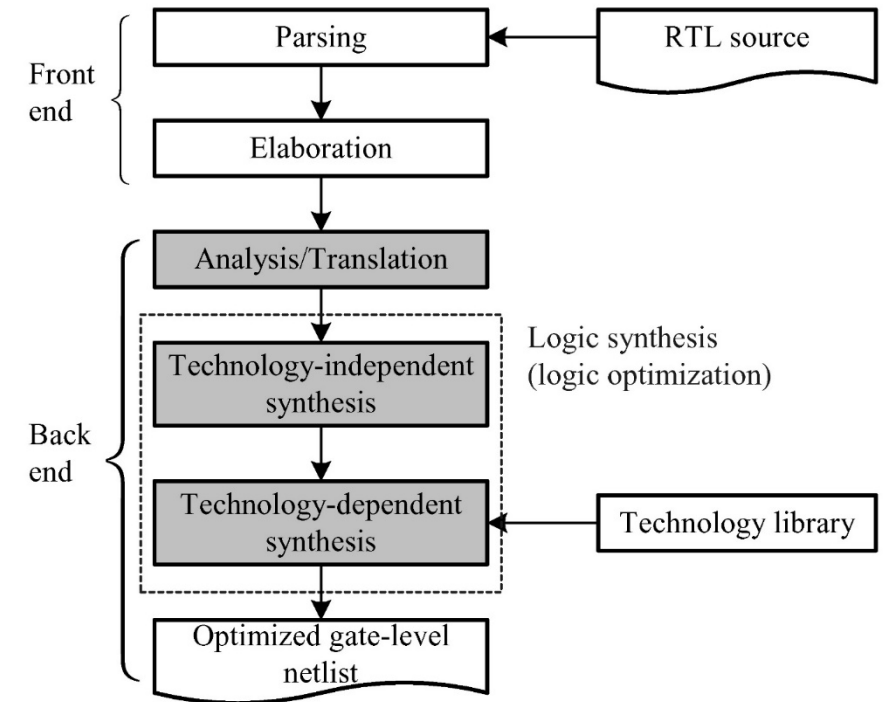- Front end
 - Parsing phase
 - Check the syntax of the source code
 - Create internal components
 - Elaboration phase
 - Connect the internal components
 - Unroll loops & expand generate-loops
 - Set up parameters passing for tasks and functions



→ Complete description of the input circuit

Writing Synthesizable Code

- Synthesizable operators
- Synthesizable constructs
 - assignment statement
 - if .. else statement
 - case statement
 - loop structures
 - always statement

Synthesizable Operators

- Analysis/translation step extracts the logical functions from a language structure

Arithmetic	Bitwise	Reduction	Relational
+: add -: subtract *: multiply /: divide %: modulus **: exponent	~: NOT &: AND : OR ^: XOR ~^, ^~: XNOR	&: AND : OR ~&: NAND ~ : NOR ^: XOR ~^, ^~: XNOR	>: greater than <: less than >=: greater than or equal <=: less than or equal
Shift		Logical	Equality
<<: left shift >>: right shift <<<: arithmetic left shift >>>: arithmetic right shift	case equality ===: equality !==: inequality	&&: AND : OR !: NOT	==: equality !=: inequality
			Miscellaneous
			{ , }: concatenation {const_expr{ }}: replication ? : : conditional

Operators with gray blocks are generally the exceptions for synthesis

Operands can be wire net type, reg variable type and parameter, as well as functions

Synthesizable Constructs: if-else

- Usually synthesize into a 2-to-1 multiplexer
 - Nested if-else → priority-encoded, cascaded combination of multiplexers
- For combinational logic
 - Completely specified?

```
always @(enable or data)
    if (enable) y = data; //infer a latch
```

```
always @(enable or data)
    if (enable) y = data;
    else y = y; //infer a latch
```

```
always @(enable or data)
    if (enable) y = data;
    else y = x; //infer a mux
```

Synthesizable Constructs: if-else

- Latch inference --- Incomplete if-else statements

// creating a latch


```
module latch_infer_if(enable, data, y);
```

```
input          enable, data;
```

```
output reg     y;
```

```
always @(enable or data)
```
 
```
    if (enable) y = data; // infer a latch for y
```



Synthesizable Constructs: if-else

- For sequential logic

- Completely specified?

```
always @(posedge clk)
    if (enable) y <= data;
    else y <= y;      // a redundant expression
```

- Synthesis tool will remove the redundant expression

Synthesizable Constructs: if-else

- Coding style

- Avoid using any latches in a design
- Assign outputs for all input conditions to avoid inferred latches
- Two ways to avoid latch inference:

```
always @(enable or data)
    y = 1'b0;    // initialize y to its initial value.
    if (enable) y = data;
```

```
always @(enable or data)
    if (enable) y = data;
    else y = x;  // complete if-else statement
```


Synthesizable Constructs: case Statement

- A case statement
 - Infers a multiplexer
 - Completely specified?

Synthesizable Constructs: case Statement

- Latch inference --- **Incomplete** case statements
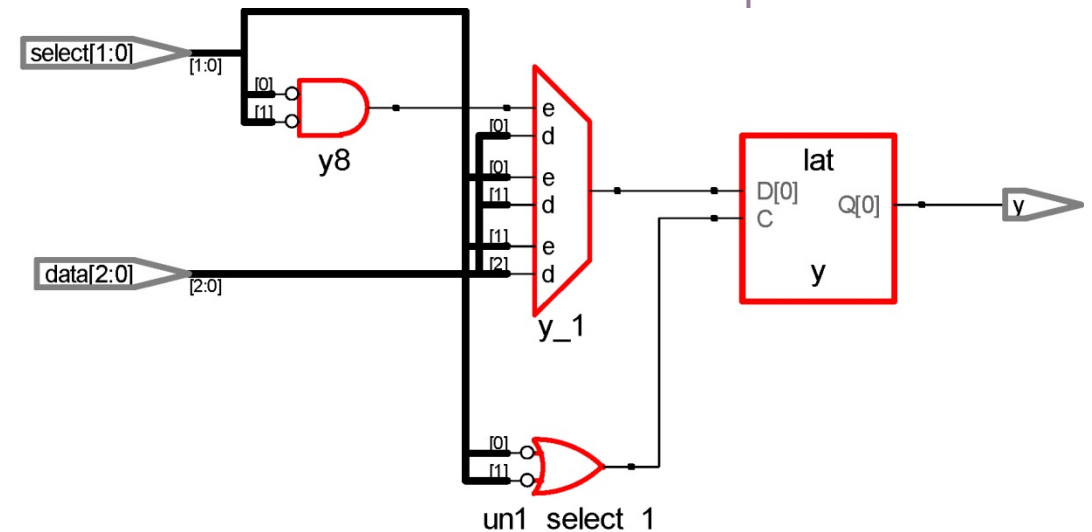
```
// Creating a latch
module latch_infer_case(select, data, y);
...
output reg    y;
always @(select or data)
    case (select)
        2'b00: y = data[select];
        2'b01: y = data[select];
        2'b10: y = data[select];
        // infer a latch
    endcase
```



Synthesizable Constructs: case Statement

- Latch inference --- **Complete** case statements

```
module mux(select, data, y);  
...  
output reg    y;  
always @(select or data)  
    case (select)  
        2'b00: y = data[select];  
        2'b01: y = data[select];  
        2'b10: y = data[select];  
        default: y = 2'b11; // mux  
    endcase
```

Synthesizable Constructs: Pos/Neg signals

- Mixed use of posedge/level signals

```
// the mixed usage of posedge and level signals
// the result cannot be synthesized
module DFF_bad (clk, reset, d, q);
...
// the body of DFF
always @(posedge clk or reset)
begin
    if (reset)      q <= 1'b0;
    else            q <= d;
end
```

Error: Do not mix posedge/negedge use with plain (level) signal references

Synthesizable Constructs: Pos/Neg signals

- Mixed use of posedge/negedge signals

```
// the mixed usage of posedge/negedge signal
```

```
module DFF_good (clk, reset_n, d, q);
```

```
...
```

```
// the body of DFF
```


```
always @(posedge clk or negedge reset_n)
```

```
begin
```

```
    if (!reset_n) q <= 1'b0;
```

```
    else          q <= d;
```

```
end
```

 

Synthesizable Constructs: Loops

- Loop statements *for*, *while*, and *forever* are synthesizable except that *while* and *forever* must contain timing control `@(posedge clk)` or `@(negedge clk)`
- *repeat* is generally not synthesizable

```
// an N-bit adder using for loop.
```

```
module nbit_adder_for( x, y, c_in, sum, c_out);
```

```
parameter          N = 4;      // default size
```

```
...  
integer          i;
```

```
...  
always @(x or y or c_in) begin
```

```
    co = c_in;
```


```
    for (i = 0; i < N; i = i + 1)
```

```
        {co, sum[i]} = x[i] + y[i] + co; // At the elaboration phase, the always
```

```
block is expanded into the following statements
```

```
    c_out = co;
```

```
end
```

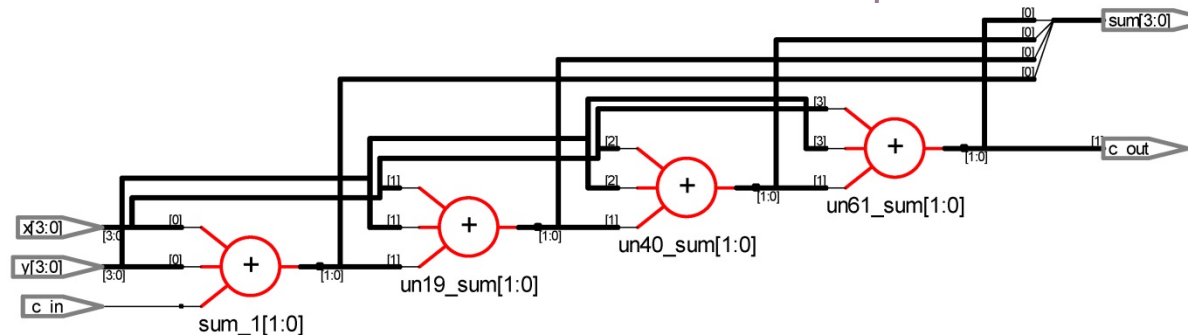


Synthesizable Constructs: Loops

■ Loop structures – **Incorrectly synthesizable** example

// a multiple cycle example --- This is an incorrect version.
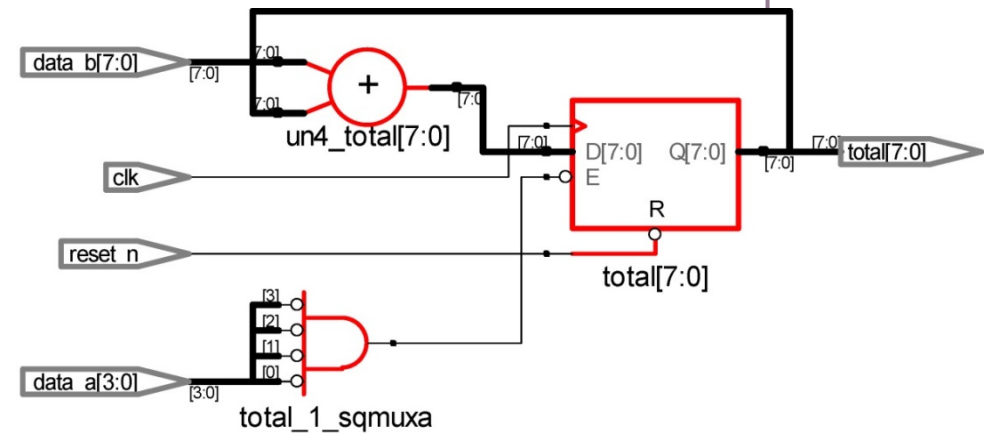
```
...  
parameter      N = 8;  
parameter      M = 4;  
input          clk, reset_n;  
...  
integer i;  
// what does the following statement do?  
always @(posedge clk or negedge reset_n) begin  
    if (!reset_n) total <= 0;  
    else for (i = 0; i < M; i = i + 1)  
        if (data_a[i] == 1) total <= total + data_b;  
end
```




Q: Why the synthesized result is like this?
Due to the blocking statement!

Synthesizable Constructs: Loops


// a multiple cycle example --- This is an incorrect version.

```
...
parameter      N = 8;
parameter      M = 4;
input          clk, reset_n;
...
integer i;
// what does the following statement do?
always @(posedge clk or negedge reset_n) begin
    if (!reset_n) total <= 0;
    else begin
        if (data_a[0] == 1) total <= total + data_b;
        if (data_a[1] == 1) total <= total + data_b;
        if (data_a[2] == 1) total <= total + data_b;
        if (data_a[3] == 1) total <= total + data_b;
    end
end
end
```

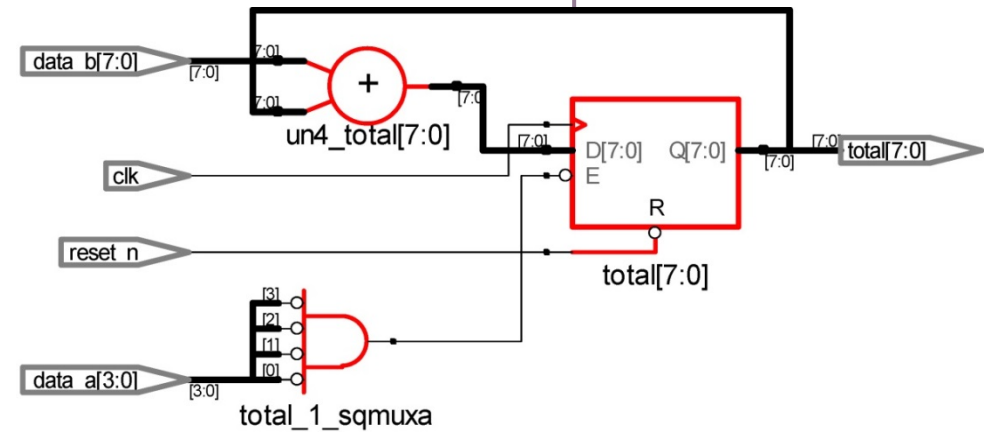

Synthesizable Constructs: Loops

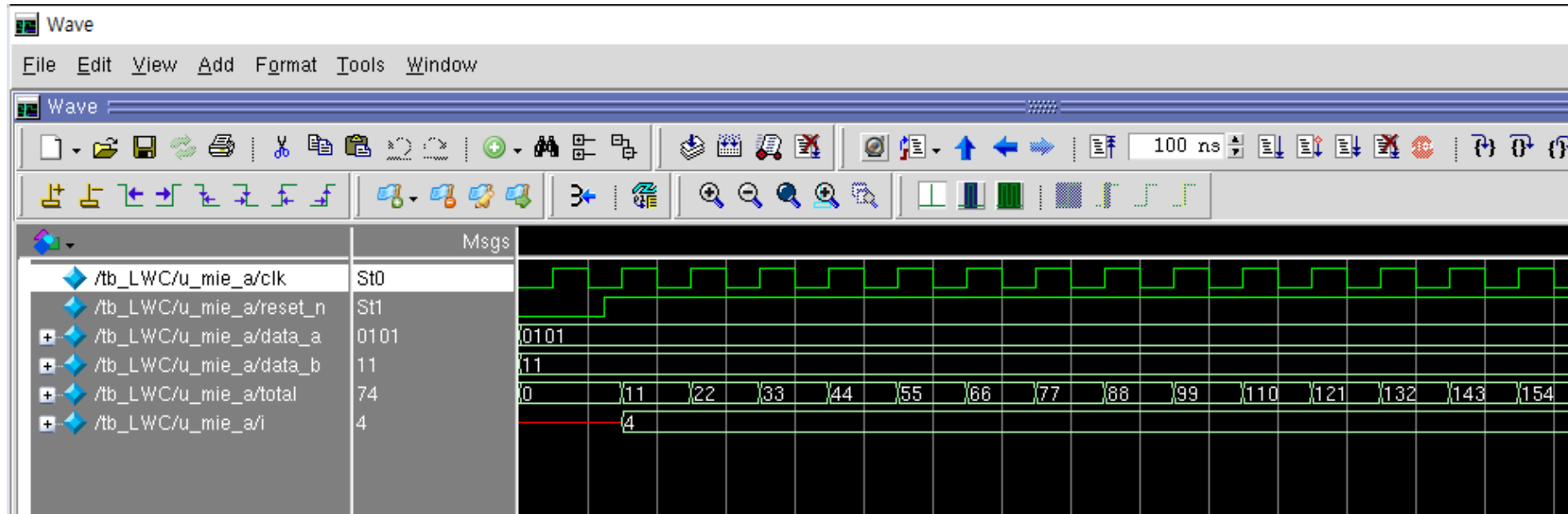- Loop structures – **Incorrectly synthesizable** example



Architecture of Logic Synthesizers

■ Back end


- Analysis/translation

- Include managing the design hierarchy
- Extract the FSM
- Explore resource sharing

- Logic synthesis (**logic optimization**)


- Create a new gate network computing the functions specified by a set of Boolean functions, one per primary output
- Balance a number of concerns : functional metric and non-functional metric (area, power, delay)

- Netlist generation

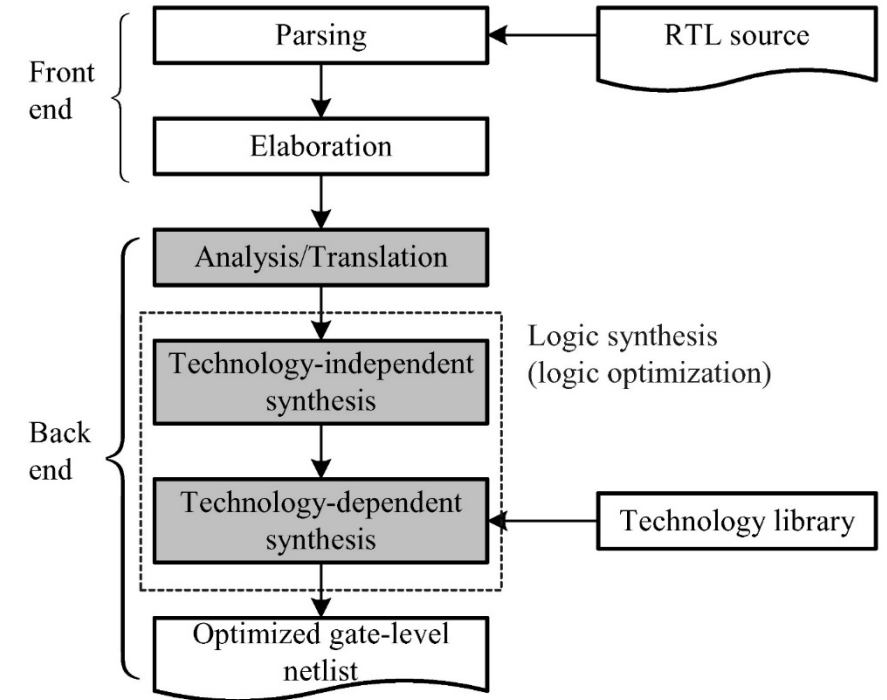

Logic Optimization

 - Combinational circuit
 - e.g., Minimum cover selection on K-map



6 prime implicants:


$A'B'D$, BC' , AC , $A'C'D$, AB , $B'CD$

essential

minimum cover: $AC + BC' + A'B'D$

Logic Optimization

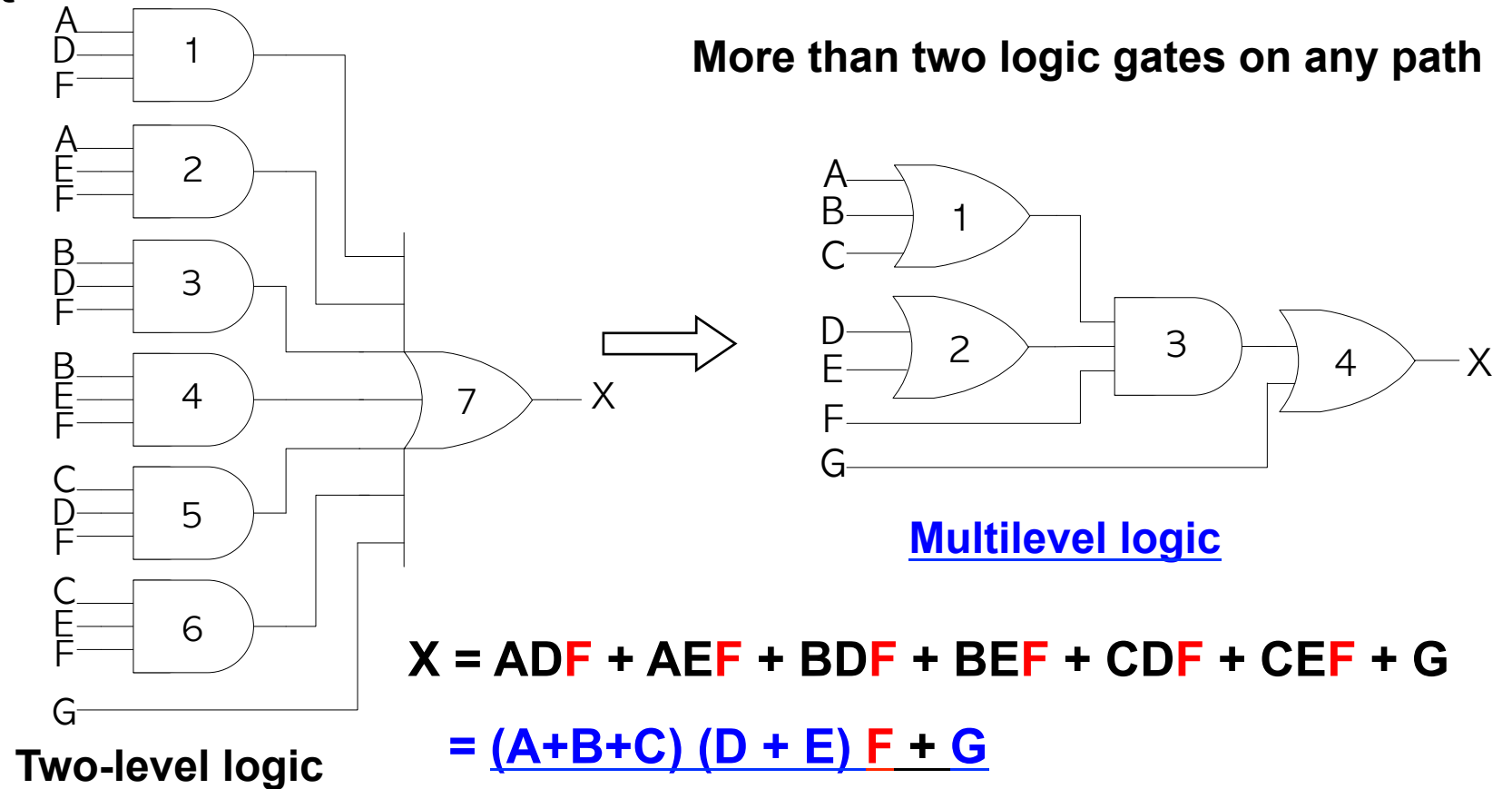- Combinational circuit
 - e.g., multi-level logic




- How can we increase the logic level?
(conversion into multi-level?)


Factoring

Logic Optimization

 - FSM optimization in sequential circuit
 - **State minimization in FSM + input/output/state encoding + combinational circuit optimization**



```
module sequence_detector_mealy (clk, reset_n, x, z);
    input          clk, reset_n, x; output reg z;
    reg            [1:0] present_state, next_state; // present state and next state
    parameter      A = 2'b00, B = 2'b01, C = 2'b10, D = 2'b11;
    // part 1: initialize to state A and update present state register
    always @(posedge clk or negedge reset_n)
        if(!reset_n) present_state <= A; else present_state <= next_state;
    // part 2: determine next state
    always @(present_state or x)
        case(present_state)
            A: if (x) next_state = A; else next_state = B;
            B: if (x) next_state = C; else next_state = B;
            C: if (x) next_state = A; else next_state = D;
            D: if (x) next_state = C; else next_state = B;
        endcase
    // part 3: evaluate output z
    always @(present_state or x) // mealey machine
        case (present_state)
            A: if (x) z = 1'b0; else z = 1'b0;
            B: if (x) z = 1'b0; else z = 1'b0;
            C: if (x) z = 1'b0; else z = 1'b0;
            D: if (x) z = 1'b1; else z = 1'b0;
        endcase
endmodule
```

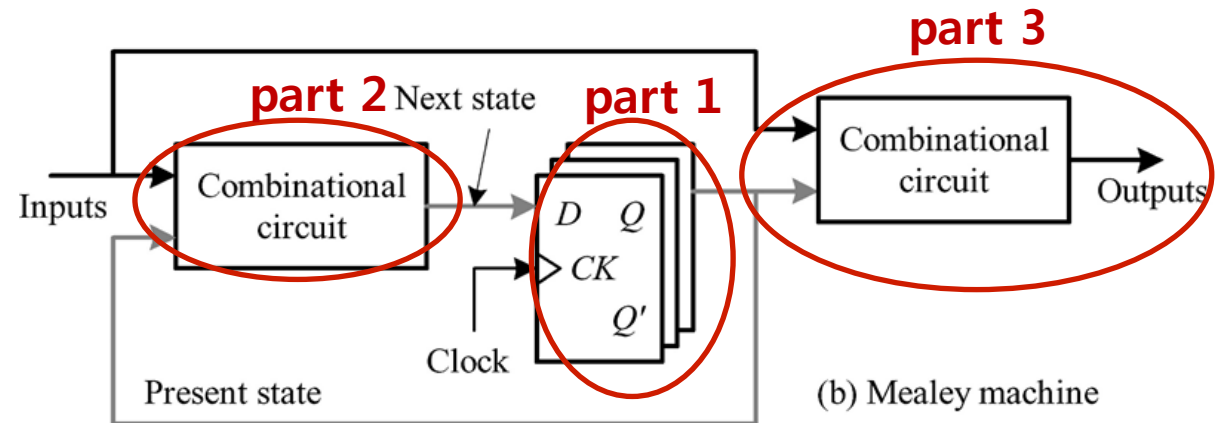

states → # F/Fs

Logic Optimization

- FSM optimization in sequential circuit
 - State Minimization
 - Fewer states require fewer state bits
 - Fewer bits require fewer logic equations
 - Encodings: State, Inputs, Outputs
 - State encoding with fewer bits has fewer equations to implement
 - However, each may be more complex
 - State encoding with more bits (e.g., one-hot) has simpler equations
 - Complexity directly related to complexity of state diagram
 - Input/output encoding may or may not be under designer control