

# Chapter 31

## **Electromagnetic Oscillations and Alternating Current**

Lecture 17,18

Seon-Hee Seo

2016.10.21-26

# 31 Summary

## LC Energy Transfer

- In an oscillating LC circuit, instantaneous values of the two forms of energy are

$$U_E = \frac{q^2}{2C} \quad \text{and} \quad U_B = \frac{Li^2}{2} \quad \text{Eq. 31-1\&2}$$

## LC Charge and Current Oscillations

- The principle of conservation of energy leads to

$$L \frac{d^2q}{dt^2} + \frac{1}{C} q = 0 \quad \text{Eq. 31-11}$$

- The solution of Eq. 31-11 is

$$q = Q \cos(\omega t + \phi) \quad \text{Eq. 31-12}$$

- the angular frequency  $\omega$  of the oscillations is

$$\omega = \frac{1}{\sqrt{LC}}. \quad \text{Eq. 31-4}$$

## Damped Oscillations

- Oscillations in an LC circuit are damped when a dissipative element  $R$  is also present in the circuit. Then

$$L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = 0 \quad \text{Eq. 31-24}$$

- The solution of this differential equation is

$$q = Q e^{-Rt/2L} \cos(\omega' t + \phi), \quad \text{Eq. 31-25}$$

## Alternating Currents; Forced Oscillations

- A series RLC circuit may be set into forced oscillation at a driving angular frequency by an external alternating emf

$$\mathcal{E} = \mathcal{E}_m \sin \omega_d t. \quad \text{Eq. 31-28}$$

- The current driven in the circuit is

$$i = I \sin(\omega_d t - \phi) \quad \text{Eq. 31-29}$$

# 31-1 Electromagnetic Oscillations

## Learning Objectives

**31.01** Sketch an LC oscillator and explain which quantities oscillate and what constitutes one period of the oscillation.

**31.02** For an LC oscillator, sketch graphs of the potential difference across the capacitor and the current through the inductor as functions of time, and indicate the period  $T$  on each graph.

**31.03** Explain the analogy between a block–spring oscillator and an LC oscillator.

**31.04** For an LC oscillator, apply the relationships between the angular frequency  $\omega$  (and the related frequency  $f$  and period  $T$ ) and the values of the inductance and capacitance.

**31.05** Starting with the energy of a block–spring system, explain the derivation of the differential equation for charge  $q$  in an LC oscillator and then identify the solution for  $q(t)$ .

**31.06** For an LC oscillator, calculate the charge  $q$  on the capacitor for any given time and identify the amplitude  $Q$  of the charge oscillations.

# 31-1 Electromagnetic Oscillations

## Learning Objectives

**31.07** Starting from the equation giving the charge  $q(t)$  on the capacitor in an LC oscillator, find the current  $i(t)$  in the inductor as a function of time.

**31.08** For an LC oscillator, calculate the current  $i$  in the inductor for any given time and identify the amplitude  $I$  of the current oscillations.


**31.09** For an LC oscillator, apply the relationship between the charge amplitude  $Q$ , the current amplitude  $I$ , and the angular frequency  $\omega$ .

**31.10** From the expressions for the charge  $q$  and the current  $i$  in an LC oscillator, find the magnetic field energy  $U_B(t)$  and the electric field energy  $U_E(t)$  and the total energy.

**31.11** For an LC oscillator, sketch graphs of the magnetic field energy  $U_B(t)$ , the electric field energy  $U_E(t)$ , and the total energy, all as functions of time


**31.12** Calculate the maximum values of the magnetic field energy  $U_B$  and the electric field energy  $U_E$  and also calculate the total energy..

# 31-1 Electromagnetic Oscillations

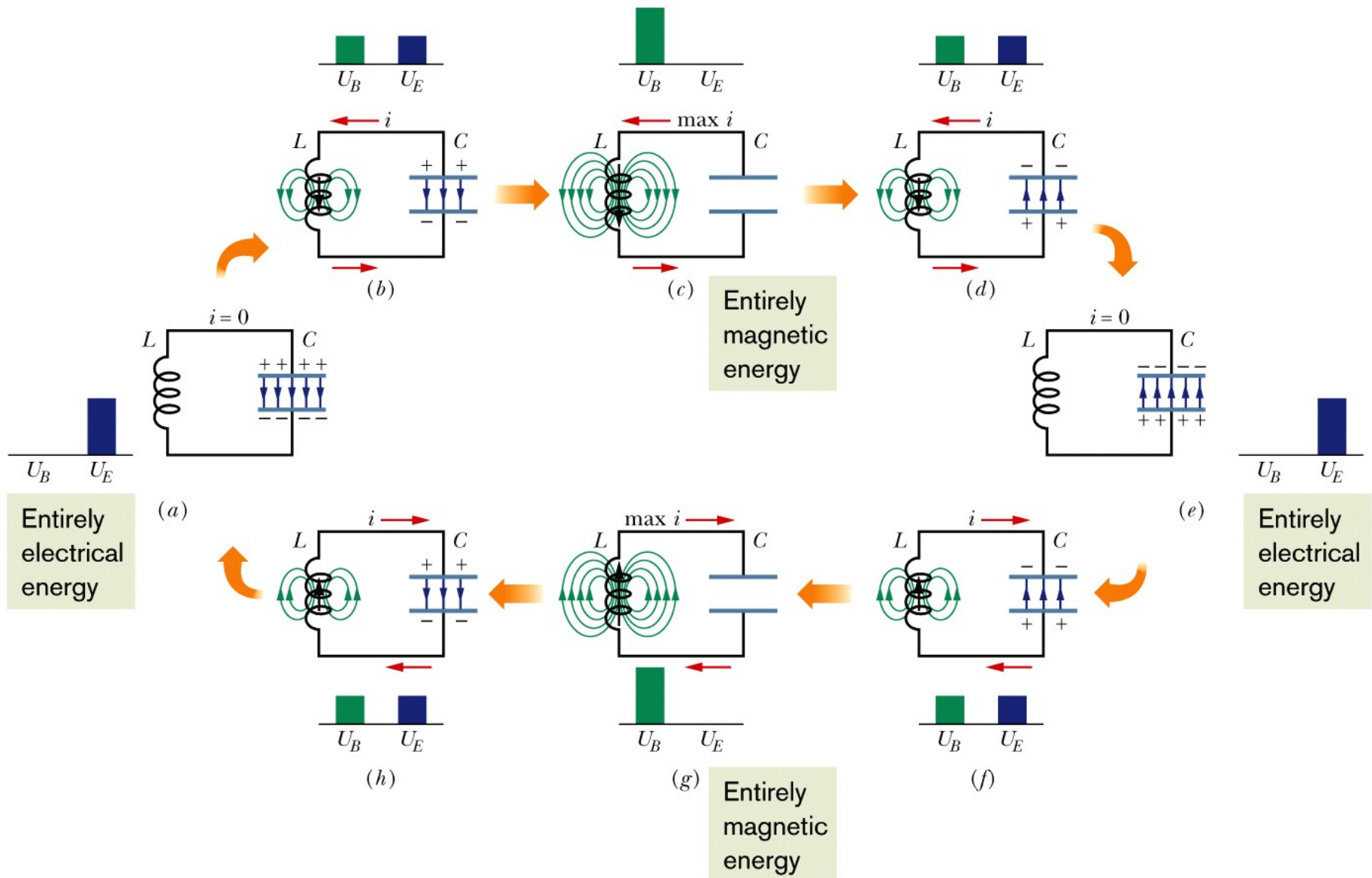
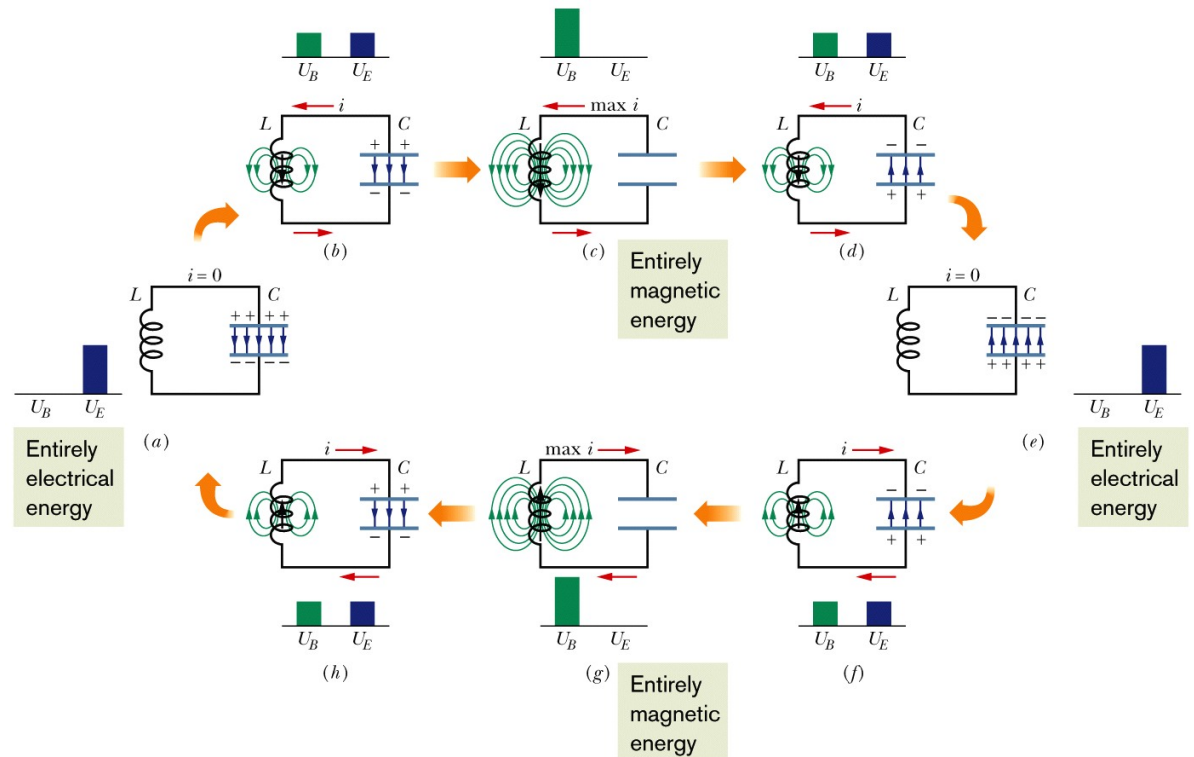
# 31-1 Electromagnetic Oscillations

Eight stages in a single cycle of oscillation of a resistanceless LC circuit. The bar graphs by each figure show the stored magnetic and electrical energies. The magnetic field lines of the inductor and the electric field lines of the capacitor are shown. (a) Capacitor with maximum charge, no current. (b) Capacitor discharging, current increasing. (c) Capacitor fully discharged, current maximum. (d) Capacitor charging but with polarity opposite that in (a), current decreasing. (e) Capacitor with maximum charge having polarity opposite that in (a), no current. (f) Capacitor discharging, current increasing with direction opposite that in (b). (g) Capacitor fully discharged, current maximum. (h) Capacitor charging, current decreasing.



Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

(e) Capacitor with maximum charge having polarity opposite that in (a), no current. (f) Capacitor discharging, current increasing with direction opposite that in (b). (g) Capacitor fully discharged, current maximum. (h) Capacitor charging, current decreasing.



# 31-1 Electromagnetic Oscillations


Parts (a) through (h) of the Figure show succeeding stages of the oscillations in a simple LC circuit. The energy stored in the electric field of the **capacitor** at any time is

$$U_E = \frac{q^2}{2C}$$

where  $q$  is the charge on the capacitor at that time. The energy stored in the magnetic field of the **inductor** at any time is

$$U_B = \frac{Li^2}{2}$$

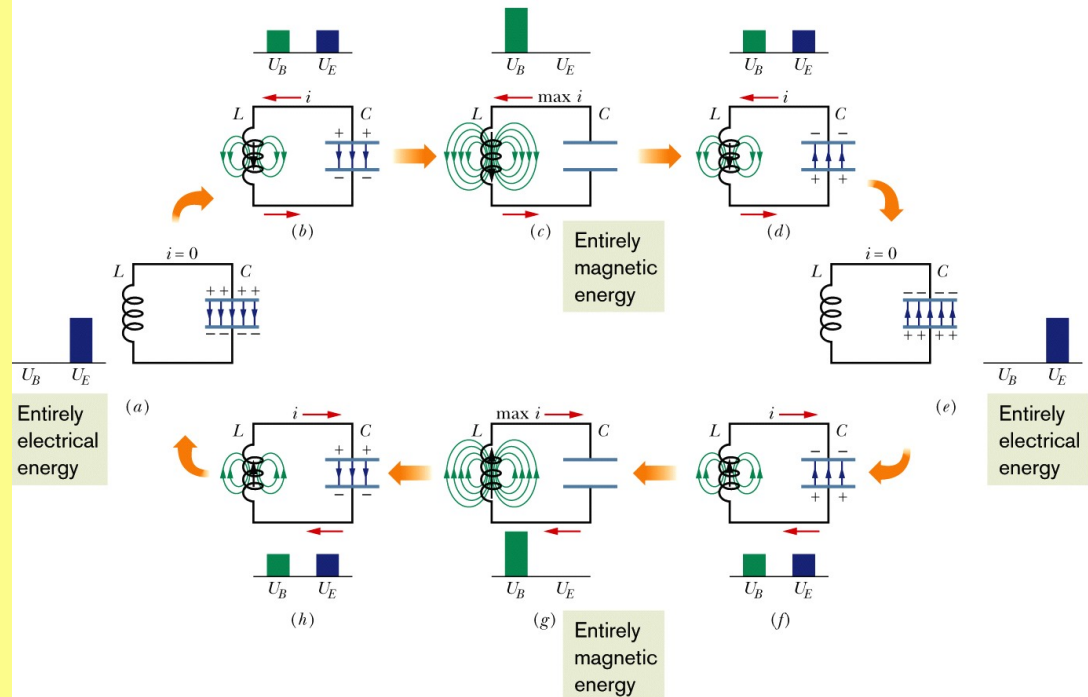where  $i$  is the current through the inductor at that time.



copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

The resulting oscillations of the capacitor's electric field and the inductor's magnetic field are said to be **electromagnetic oscillations**.

# 31-1 Electromagnetic Oscillations

**Table 31-1** Comparison of the Energy in Two Oscillating Systems

Block–Spring System		LC Oscillator	
Element	Energy	Element	Energy
Spring	Potential, $\frac{1}{2}kx^2$	Capacitor	Electrical, $\frac{1}{2}(1/C)q^2$
Block	Kinetic, $\frac{1}{2}mv^2$	Inductor	Magnetic, $\frac{1}{2}Li^2$
$v = dx/dt$		$i = dq/dt$	

Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

From the table we can deduce the correspondence between these systems. Thus,

$q$  corresponds to  $x$ ,  $1/C$  corresponds to  $k$ ,  
 $i$  corresponds to  $v$ , and  $L$  corresponds to  $m$ .

The correspondences listed above suggest that to find the angular frequency of oscillation for an ideal (resistanceless) LC circuit,  $k$  should be replaced by  $1/C$  and  $m$  by  $L$ , yielding


$$\omega = \sqrt{\frac{k}{m}} \quad (\text{block–spring system}).$$

$$\omega = \frac{1}{\sqrt{LC}} \quad (LC \text{ circuit}).$$



# The Block-spring Oscillator

In Ch. 15

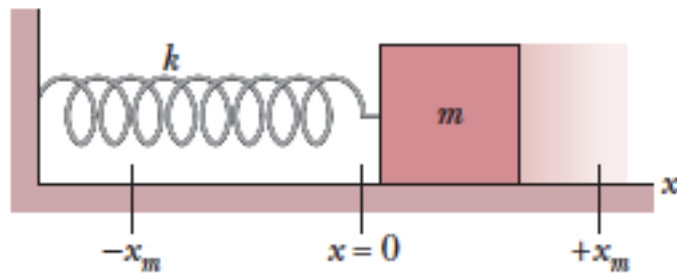

$$U = U_b + U_s = \frac{1}{2}mv^2 + \frac{1}{2}kx^2,$$

$$\frac{dU}{dt} = \frac{d}{dt} \left( \frac{1}{2}mv^2 + \frac{1}{2}kx^2 \right) = mv \frac{dv}{dt} + kx \frac{dx}{dt} = 0.$$

$$m \frac{d^2x}{dt^2} + kx = 0 \quad (\text{block-spring oscillations}).$$

Displacement at time  $t$

$$x(t) = x_m \cos(\omega t + \phi)$$

Amplitude

Angular frequency

Time

Phase constant or phase angle

Phase

$$x = X \cos(\omega t + \phi) \quad (\text{displacement}),$$

Simple Harmonic Motion

# 31-1 Electromagnetic Oscillations

## LC Oscillator

The total energy  $U$  present at any instant in an oscillating LC circuit is given by

$$U = U_B + U_E = \frac{Li^2}{2} + \frac{q^2}{2C}$$

in which  $U_B$  is the energy stored in the magnetic field of the inductor and  $U_E$  is the energy stored in the electric field of the capacitor. Since we have assumed the circuit resistance to be zero, no energy is transferred to thermal energy and  $U$  remains constant with time. In more formal language,  $dU/dt$  must be zero. This leads to

$$\frac{dU}{dt} = \frac{d}{dt} \left( \frac{Li^2}{2} + \frac{q^2}{2C} \right) = Li \frac{di}{dt} + \frac{q}{C} \frac{dq}{dt} = 0.$$

However,  $i = dq/dt$  and  $di/dt = d^2q/dt^2$ . With these substitutions, we get

$$L \frac{d^2q}{dt^2} + \frac{1}{C} q = 0$$

This is the **differential equation** that describes the oscillations of a resistanceless LC circuit.

# 31-1 Electromagnetic Oscillations

## Charge and Current Oscillation

The solution for the differential equation that describes the oscillations of a resistanceless LC circuit is

$$q = Q \cos(\omega t + \phi)$$

where  $Q$  is the amplitude of the charge variations,  $\omega$  is the angular frequency of the electromagnetic oscillations, and  $\phi$  is the phase constant. Taking the first derivative of the above Eq. with respect to time gives us the current:

$$i = \frac{dq}{dt} = -\omega Q \sin(\omega t + \phi)$$



### Checkpoint 2

A capacitor in an LC oscillator has a maximum potential difference of 17 V and a maximum energy of 160  $\mu\text{J}$ . When the capacitor has a potential difference of 5 V and an energy of 10  $\mu\text{J}$ , what are (a) the emf across the inductor and (b) the energy stored in the magnetic field?

Answer:

(a)  $\mathcal{E}_L = 12 \text{ V}$

(b)  $U_B = 150 \mu\text{J}$

# 31-1 Electromagnetic Oscillations

## Electrical and Magnetic Energy Oscillations

The electrical energy stored in the LC circuit at time  $t$  is,

$$U_E = \frac{q^2}{2C} = \frac{Q^2}{2C} \cos^2(\omega t + \phi).$$


The magnetic energy is,

$$U_B = \frac{Q^2}{2C} \sin^2(\omega t + \phi).$$

Figure shows plots of  $U_E(t)$  and  $U_B(t)$  for the case of  $\phi=0$ . Note that

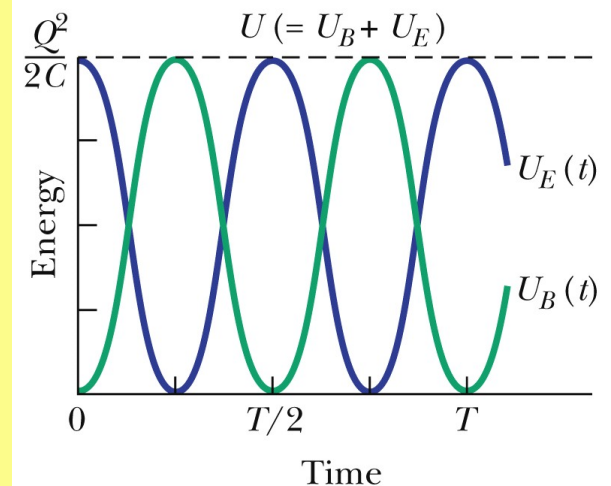1. The maximum values of  $U_E$  and  $U_B$  are both  $Q^2/2C$ .
2. At any instant the sum of  $U_E$  and  $U_B$  is equal to  $Q^2/2C$ , a constant.
3. When  $U_E$  is maximum,  $U_B$  is zero, and conversely.

The electrical and magnetic energies vary but the total is constant.



Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

The stored magnetic energy and electrical energy in the RL circuit as a function of time.

## 31-2 Damped Oscillation in an RLC circuit

### Learning Objectives

**31.13** Draw the schematic of a damped RLC circuit and explain why the oscillations are damped.

**31.14** Starting with the expressions for the field energies and the rate of energy loss in a damped RLC circuit, write the differential equation for the charge  $q$  on the capacitor.

**31.15** For a damped RLC circuit, apply the expression for charge  $q(t)$ .

**31.16** Identify that in a damped RLC circuit, the charge amplitude and the amplitude of the electric field energy decrease exponentially with time.

**31.17** Apply the relationship between the angular frequency  $\omega'$  of a given damped RLC oscillator and the angular frequency  $\omega$  of the circuit if  $R$  is removed.

**31.18** For a damped RLC circuit, apply the expression for the electric field energy  $U_E$  as a function of time.

# 31-2 Damped Oscillation in an RLC circuit

To analyze the oscillations of this circuit, we write an equation for the total electromagnetic energy  $U$  in the circuit at any instant. Because the resistance does not store electromagnetic energy, we can write

$$U = U_B + U_E = \frac{Li^2}{2} + \frac{q^2}{2C}.$$

Now, however, **this total energy decreases as energy is transferred to thermal energy.** The rate of that transfer is,

$$\frac{dU}{dt} = -i^2R,$$

where the minus sign indicates that  $U$  decreases. By differentiating  $U$  with respect to time and then substituting the result we eventually get,

$$L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = 0$$

which is the differential equation for **damped oscillations in an RLC circuit.**


**Charge Decay.** The solution to above Eq. is in which  $\omega' = \sqrt{\omega^2 - (R/2L)^2}$  and

$$\omega = 1/\sqrt{LC},$$

$$q = Qe^{-Rt/2L} \cos(\omega't + \phi)$$

Energy decay
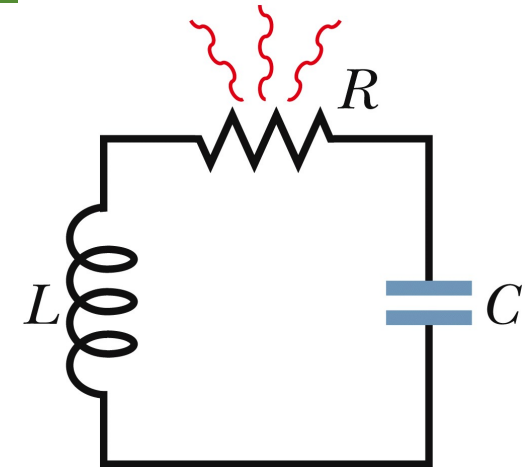
$$U_E = \frac{q^2}{2C} = \frac{[Qe^{-Rt/2L} \cos(\omega't + \phi)]^2}{2C} = \frac{Q^2}{2C} e^{-Rt/L} \cos^2(\omega't + \phi).$$



Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

A series RLC circuit. As the charge contained in the circuit oscillates back and forth through the resistance, electromagnetic energy is dissipated as thermal energy, damping (decreasing the amplitude of) the oscillations.



# 31 Summary

## LC Energy Transfer

- In an oscillating LC circuit, instantaneous values of the two forms of energy are

$$U_E = \frac{q^2}{2C} \quad \text{and} \quad U_B = \frac{Li^2}{2} \quad \text{Eq. 31-1\&2}$$

## LC Charge and Current Oscillations

- The principle of conservation of energy leads to

$$L \frac{d^2q}{dt^2} + \frac{1}{C} q = 0 \quad \text{Eq. 31-11}$$

- The solution of Eq. 31-11 is

$$q = Q \cos(\omega t + \phi) \quad \text{Eq. 31-12}$$

- the angular frequency  $\omega$  of the oscillations is

$$\omega = \frac{1}{\sqrt{LC}}. \quad \text{Eq. 31-4}$$

## Damped Oscillations

- Oscillations in an LC circuit are damped when a dissipative element  $R$  is also present in the circuit. Then

$$L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = 0 \quad \text{Eq. 31-24}$$

- The solution of this differential equation is

$$q = Q e^{-Rt/2L} \cos(\omega' t + \phi), \quad \text{Eq. 31-25}$$

## Alternating Currents; Forced Oscillations

- A series RLC circuit may be set into forced oscillation at a driving angular frequency by an external alternating emf

$$\mathcal{E} = \mathcal{E}_m \sin \omega_d t. \quad \text{Eq. 31-28}$$

- The current driven in the circuit is

$$i = I \sin(\omega_d t - \phi) \quad \text{Eq. 31-29}$$

# 31 Summary

## Series RLC Circuits

- For a series RLC circuit with an alternating external emf and a resulting alternating current,

$$I = \frac{\mathcal{E}_m}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$= \frac{\mathcal{E}_m}{\sqrt{R^2 + (\omega_d L - 1/\omega_d C)^2}}$$

Eq. 31-60&amp;63

- and the phase constant is,

$$\tan \phi = \frac{X_L - X_C}{R}$$

Eq. 31-65

- The impedance is

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Eq. 31-61

## Power

- In a series RLC circuit, the average power of the generator is,

$$P_{\text{avg}} = I_{\text{rms}}^2 R = \mathcal{E}_{\text{rms}} I_{\text{rms}} \cos \phi.$$

Eq. 31-71&amp;76

## Transformers

- Primary and secondary voltage in a transformer is related by

$$V_s = V_p \frac{N_s}{N_p}$$

Eq. 31-79

- The currents through the coils,

$$I_s = I_p \frac{N_p}{N_s}$$

Eq. 31-80

- The equivalent resistance of the secondary circuit, as seen by the generator, is

$$R_{\text{eq}} = \left( \frac{N_p}{N_s} \right)^2 R,$$

Eq. 31-82

## 31-3 Forced Oscillations of Three Simple Circuits

### Learning Objectives

**31.19** Distinguish alternating current from direct current.

**31.20** For an ac generator, write the *emf* as a function of time, identifying the *emf* amplitude and driving angular frequency.

**31.21** For an ac generator, write the current as a function of time, identifying its amplitude and its phase constant with respect to the *emf*.

**31.22** Draw a schematic diagram of a (series) RLC circuit that is driven by a generator.

**31.23** Distinguish driving angular frequency  $\omega_d$  from natural angular frequency  $\omega$ .

**31.24** In a driven (series) RLC circuit, identify the conditions for resonance and the effect of resonance on the current amplitude.

**31.25** For each of the three basic circuits (purely resistive load, purely capacitive load, and purely inductive load), draw the circuit and sketch graphs and **phasor diagrams** for voltage  $v(t)$  and current  $i(t)$ .

## 31-3 Forced Oscillations of Three Simple Circuits

### Learning Objectives

**31.26** For the three basic circuits, apply equations for voltage  $v(t)$  and current  $i(t)$ .

**31.27** On a phasor diagram for each of the basic circuits, identify angular speed, amplitude, projection on the vertical axis, and rotation angle.

**31.28** For each basic circuit, identify the phase constant, and interpret it in terms of the relative orientations of the current phasor and voltage phasor and also in terms of leading and lagging.

**31.29** Apply the mnemonic “ELI positively is the ICE man.”

**31.30** For each basic circuit, apply the relationships between the voltage amplitude  $V$  and the current amplitude  $I$ .

**31.31** Calculate capacitive reactance  $X_C$  and inductive reactance  $X_L$ .

## 31-3 Forced Oscillations of Three Simple Circuits


**AC (Alternating Current)**

**DC (Direct Current)**




The direction of motion is unimportant as long as the electrons do move so as to transfer energy to the device via collisions with atoms in the device.

DIRECT CURRENT  
(DC)

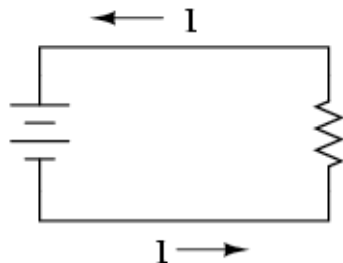

ALTERNATING CURRENT  
(AC)

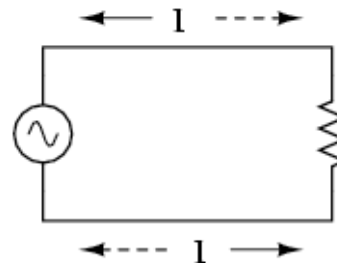


AC frequency in Korea: 60 Hz

### Why AC ?

- It is possible the use of Faraday's law of induction.
- We can step up (increase) or step down (decrease) the magnitude of an alternating potential difference at will, using a device called a transformer.
- Alternating current is more readily adaptable to rotating machinery such as generators and motors.

# 31-3 Forced Oscillations of Three Simple Circuits

## Principle of AC

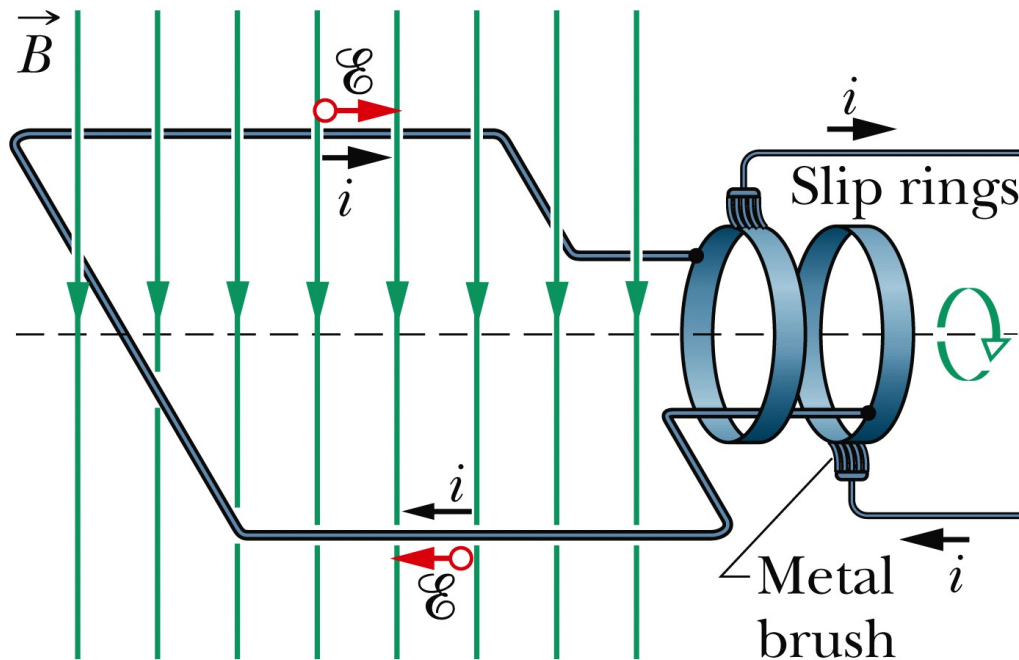

The basic mechanism of an alternating-current generator is a conducting loop rotated in an external magnetic field. In practice, the alternating emf induced in a coil of many turns of wire is made accessible by means of slip rings attached to the rotating loop. Each ring is connected to one end of the loop wire and is electrically connected to the rest of the generator circuit by a conducting brush against which the ring slips as the loop (and ring) rotates.







# Principle of AC

## AC Generator


A wire loop is rotated between the poles of a magnet, inducing a current in the wire. The current is transmitted through slip rings and brushes. ▶

### Key

-  Electric Current
-  Magnetic Field

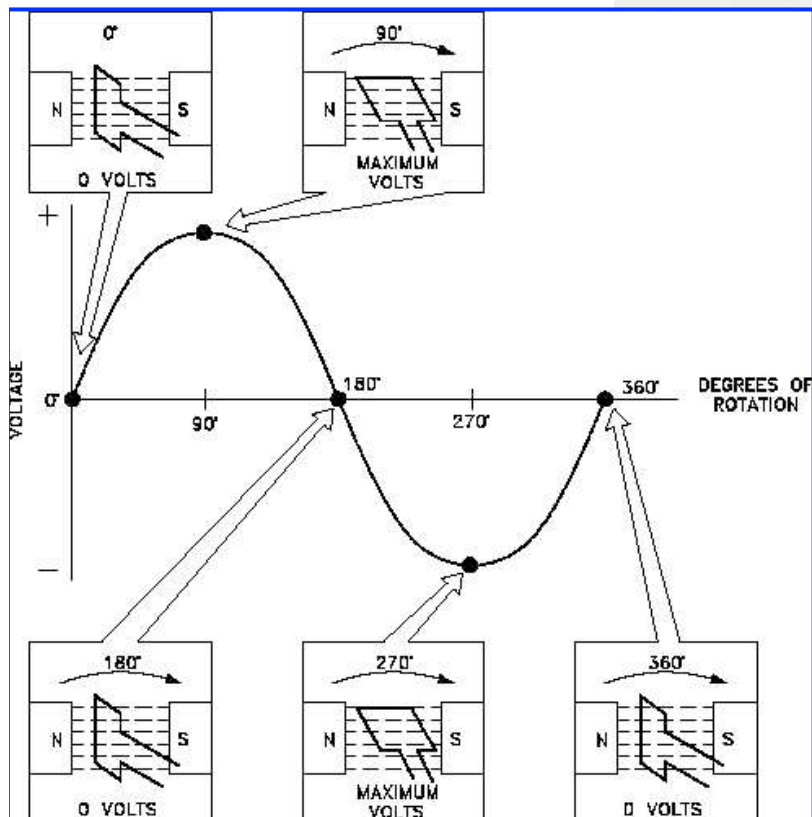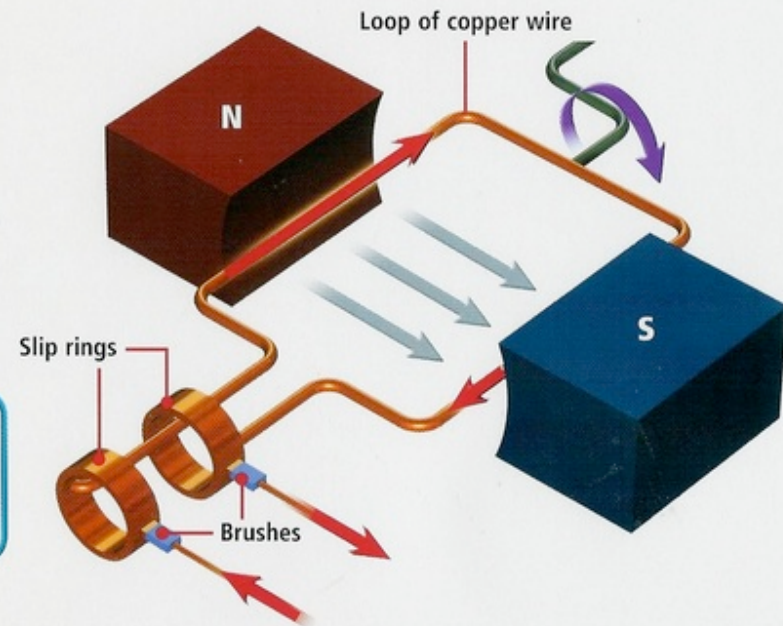
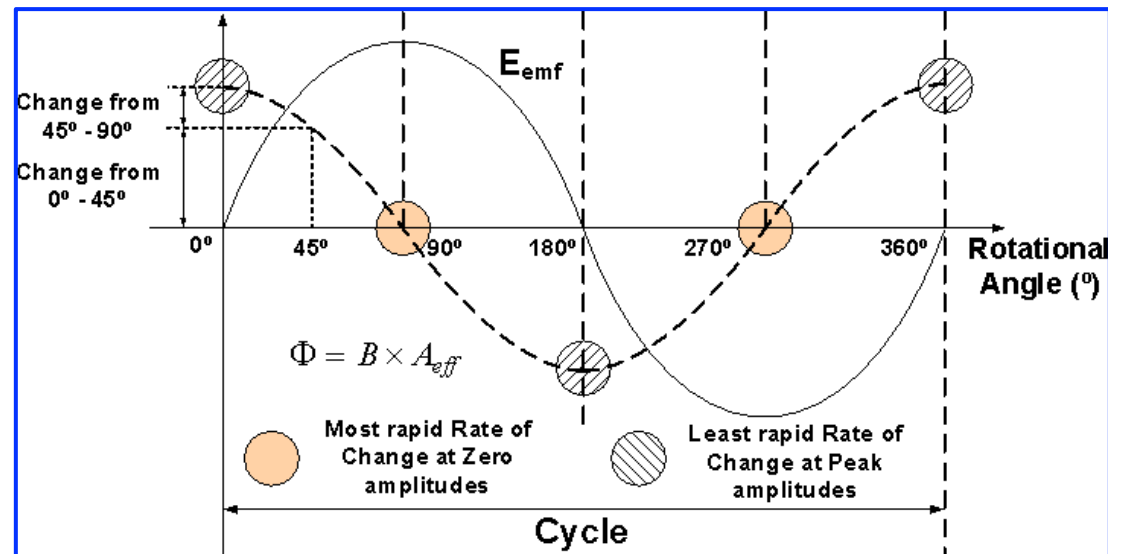
$$\mathcal{E} = \mathcal{E}_m \sin \omega_d t.$$




# 31-3 Forced Oscillations of Three Simple Circuits

## Forced Oscillations

$$\mathcal{E} = \mathcal{E}_m \sin \omega_d t.$$

$$i = I \sin(\omega_d t - \phi)$$

driving angular frequency

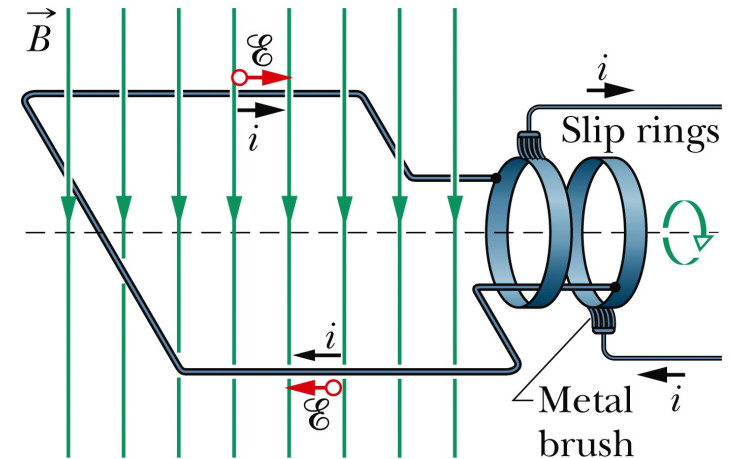

Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.



Whatever the natural angular frequency  $\omega$  of a circuit may be, forced oscillations of charge, current, and potential difference in the circuit always occur at the driving angular frequency  $\omega_d$ .

$$\omega = 1/\sqrt{LC}$$



Natural frequency in LC circuit

The amplitudes of the oscillations very much depend on how close  $\omega_d$  is to  $\omega$ . When the two angular frequencies match—a condition known as **resonance**—the amplitude  $I$  of the current in the circuit is maximum.


# 31-3 Forced Oscillations of Three Simple Circuits

## Resistive Load

The alternating potential difference across a resistor has amplitude

$$V_R = I_R R \quad (\text{resistor}).$$


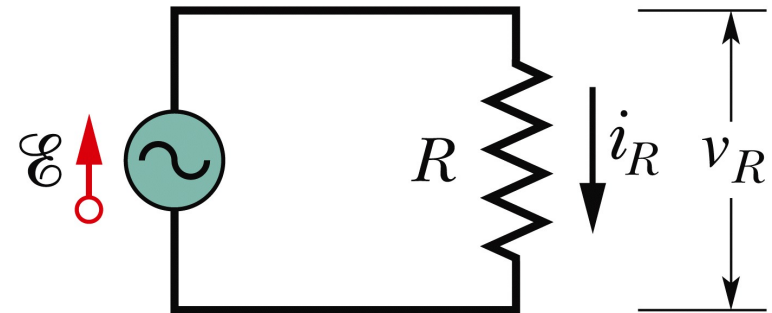
where  $V_R$  and  $I_R$  are the amplitudes of alternating current  $i_R$  and alternating potential difference  $v_R$  across the resistance in the circuit.



Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

A resistor is connected across an alternating-current generator.

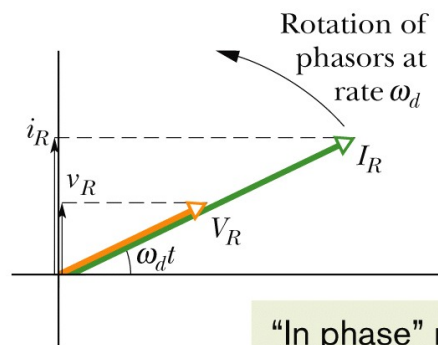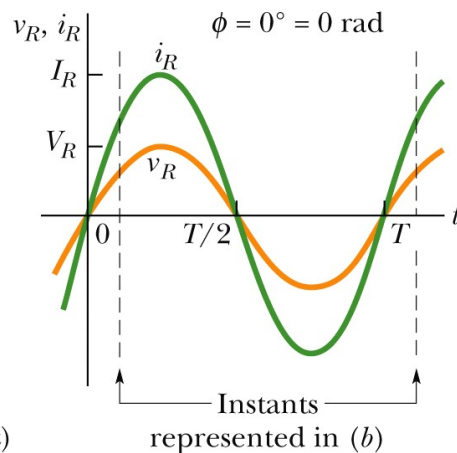For a resistive load, the current and potential difference are in phase.



“In phase” means that they peak at the same time.

$$v_R = V_R \sin \omega_d t.$$

$$i_R = \frac{v_R}{R} = \frac{V_R}{R} \sin \omega_d t.$$

(a) The current  $i_R$  and the potential difference  $v_R$  across the resistor are plotted on the same graph, both versus time  $t$ . They are in phase and complete one cycle in one period  $T$ . (b) A phasor diagram shows the same thing as (a).

# WILEY 31-3 Forced Oscillations of Three Simple Circuits

## Capacitive Load

The **capacitive reactance** of a capacitor, defined as

$$X_C = \frac{1}{\omega_d C}$$

Its value depends not only on the capacitance but also on the driving angular frequency  $\omega_d$ .


The voltage amplitude and current amplitude are related by

$$V_C = I_C X_C$$


$$q_C = C v_C = C V_C \sin \omega_d t.$$

$$i_C = \frac{dq_C}{dt} = \omega_d C V_C \cos \omega_d t.$$

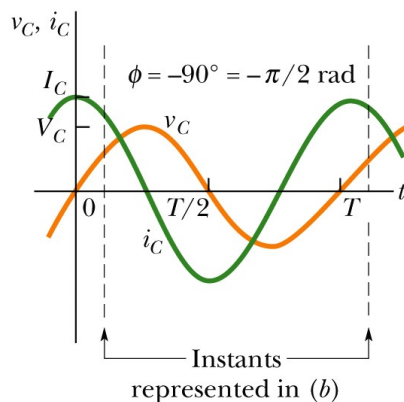For a capacitive load, the current leads the potential difference by  $90^\circ$ .




(a)

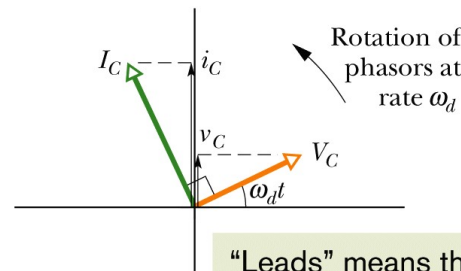

"Leads" means that the current peaks at an earlier time than the potential difference.

(b)

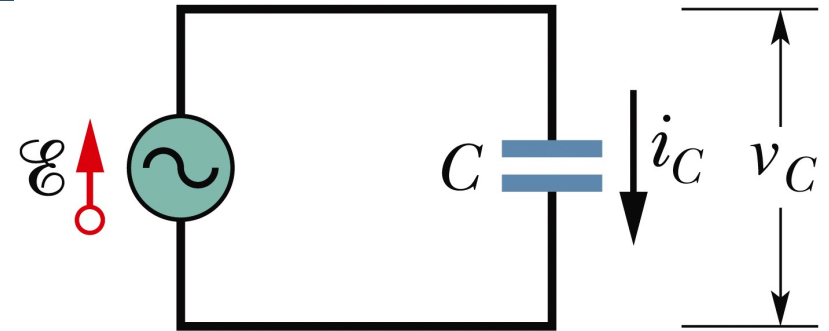

Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

A capacitor is connected across an alternating-current generator.

In the phasor diagram we see that  $i_C$  leads  $v_C$ , which means that, if you monitored the current  $i_C$  and the potential difference  $v_C$  in the circuit above, you would find that  $i_C$  reaches its maximum before  $v_C$  does, by one-quarter cycle.

(a) The current in the capacitor lags the voltage by  $90^\circ$  ( $= \pi/2$  rad). (b) A phasor diagram shows the same thing.

# 31-3 Forced Oscillations of Three Simple Circuits

## Inductive Load




The **inductive reactance** of an inductor is defined as

$$X_L = \omega_d L$$

Its value depends not only on the inductance but also on the driving angular frequency  $\omega_d$ . The voltage amplitude and current amplitude are related by

$$V_L = I_L X_L$$

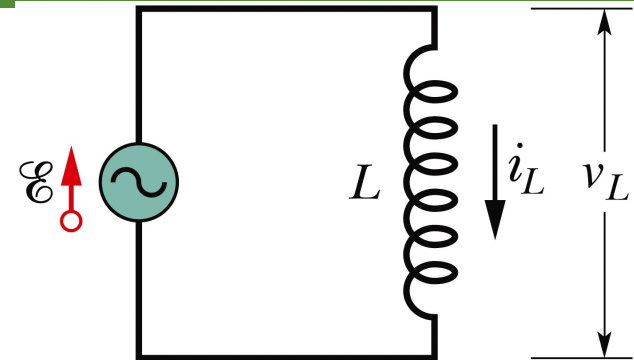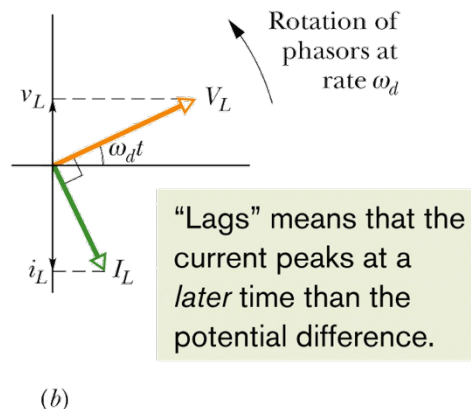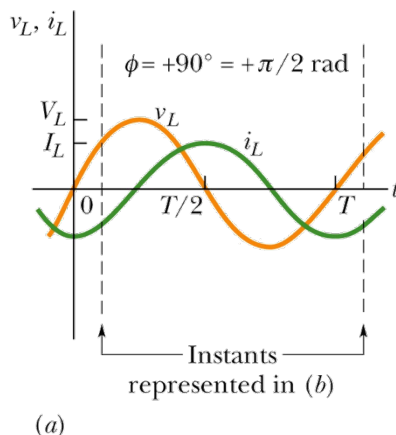For an inductive load, the current lags the potential difference by  $90^\circ$ .



Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

An inductor is connected across an alternating-current generator.

Fig. (left), shows that the quantities  $i_L$  and  $v_L$  are  $90^\circ$  out of phase. In this case, however,  $i_L$  lags  $v_L$ ; that is, monitoring the current  $i_L$  and the potential difference  $v_L$  in the circuit of Fig. (right) shows that  $i_L$  reaches its maximum value after  $v_L$  does, by one-quarter cycle.

(a) The current in the capacitor leads the voltage by  $90^\circ$  ( $= \pi/2$  rad). (b) A phasor diagram shows the same thing.



$$\mathcal{E}_L = -L \frac{di}{dt}.$$

$$v_L = L \frac{di_L}{dt}.$$

$$\longrightarrow \frac{di_L}{dt} = \frac{V_L}{L} \sin \omega_d t.$$

$$\longrightarrow i_L = \int di_L = \frac{V_L}{L} \int \sin \omega_d t \, dt = -\left( \frac{V_L}{\omega_d L} \right) \cos \omega_d t.$$

$$\longrightarrow i_L = \left( \frac{V_L}{X_L} \right) \sin(\omega_d t - 90^\circ).$$


$$X_L = \omega_d L$$



## 31-4 The Series RLC Circuits

### Learning Objectives

**31.32** Draw the schematic diagram of a series RLC circuit.

**31.33** Identify the conditions for a mainly inductive circuit, a mainly capacitive circuit, and a resonant circuit.

**31.34** For a mainly inductive circuit, a mainly capacitive circuit, and a resonant circuit, sketch graphs for voltage  $v(t)$  and current  $i(t)$  and sketch phasor diagrams, indicating leading, lagging, or resonance.

**31.35** Calculate impedance  $Z$ .

**31.36** Apply the relationship between current amplitude  $I$ , impedance  $Z$ , and emf amplitude.

**31.37** Apply the relationships between phase constant  $\phi$  and voltage amplitudes  $V_L$  and  $V_C$ , and also between phase constant  $\phi$ , resistance  $R$ , and reactances  $X_L$  and  $X_C$ .

**31.38** Identify the values of the phase constant  $\phi$  corresponding to a mainly inductive circuit, a mainly capacitive circuit, and a resonant circuit.

## 31-4 The Series RLC Circuits

### Learning Objectives

**31.39** For resonance, apply the relationship between the driving angular frequency  $\omega_d$ , the natural angular frequency  $\omega$ , the inductance  $L$ , and the capacitance  $C$ .

**31.40** Sketch a graph of current amplitude versus the ratio  $\omega_d/\omega$ , identifying the portions corresponding to a mainly inductive circuit, a mainly capacitive circuit, and a resonant circuit and indicating what happens to the curve for an increase in the resistance.

## 31-4 The Series RLC Circuit

For a series RLC circuit with an external emf given by


$$\mathcal{E} = \mathcal{E}_m \sin \omega_d t$$

The current is given by

$$i = I \sin(\omega_d t - \phi)$$

the current amplitude is given by
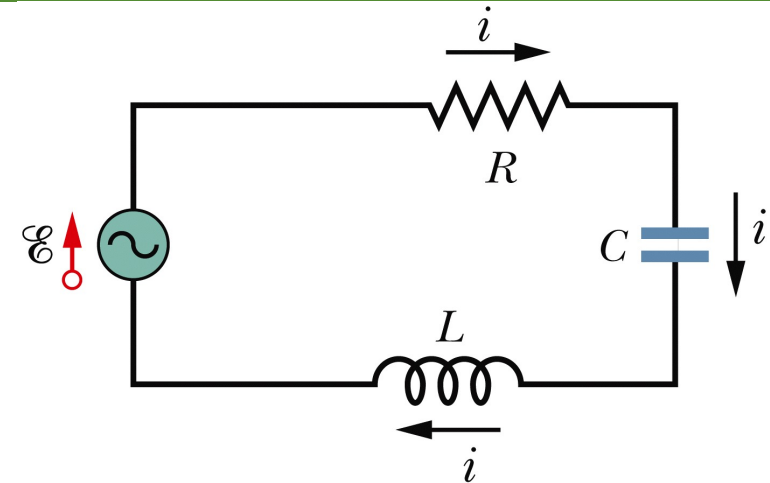
$$I = \frac{\mathcal{E}_m}{\sqrt{R^2 + (X_L - X_C)^2}}$$



Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

Series RLC circuit with an external emf


The denominator in the above equation is called the **impedance  $Z$**  of the circuit for the driving angular frequency  $\omega_d$ .

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

If we substitute the value of  $X_L$  and  $X_C$  in the equation for current ( $I$ ), the equation becomes:

$$I = \frac{\mathcal{E}_m}{\sqrt{R^2 + (\omega_d L - 1/\omega_d C)^2}}$$

## 31-4 The Series RLC Circuit

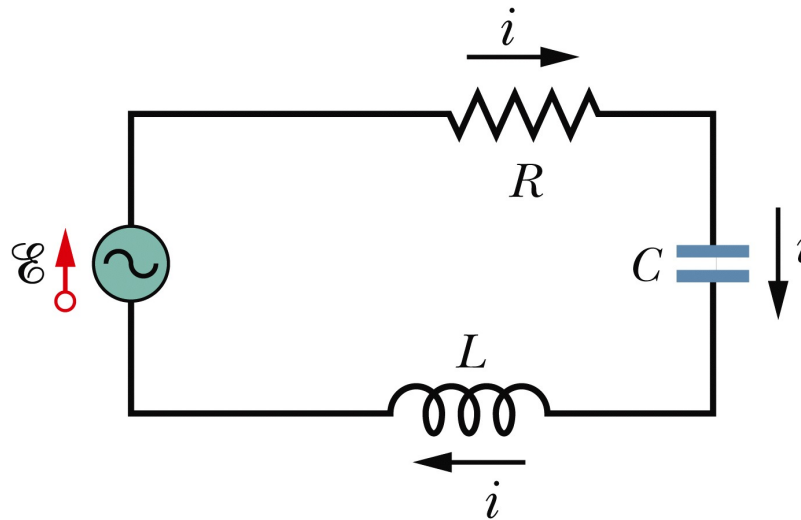

Series RLC circuit with an external emf




Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

**Resistor:** Here current and voltage are in phase; so the angle of rotation of voltage phasor  $V_R$  is the same as that of phasor  $I$ .

**Capacitor:** Here **current leads** voltage by  $90^\circ$ ; so the angle of rotation of voltage phasor  $V_C$  is  $90$  less than that of phasor  $I$ .



**Inductor:** Here **current lags** voltage by  $90^\circ$ ; so the angle of rotation of voltage phasor  $V_L$  is  $90$  greater than that of phasor  $I$ .

# 31-4 The Series RLC Circuits

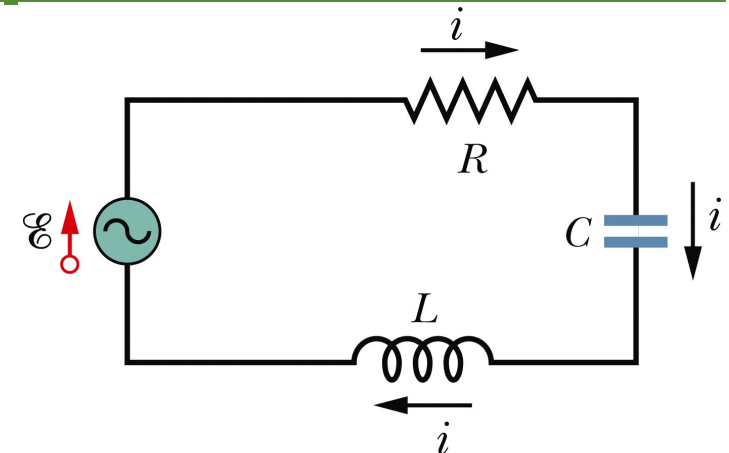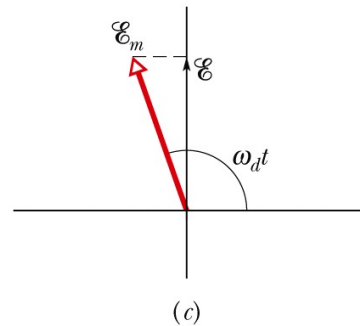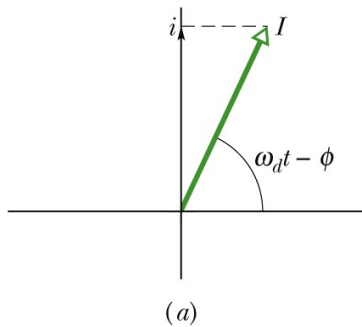

Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

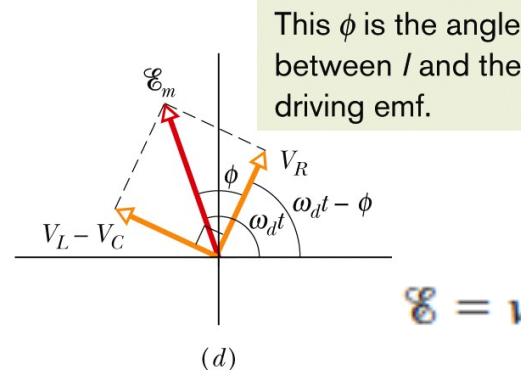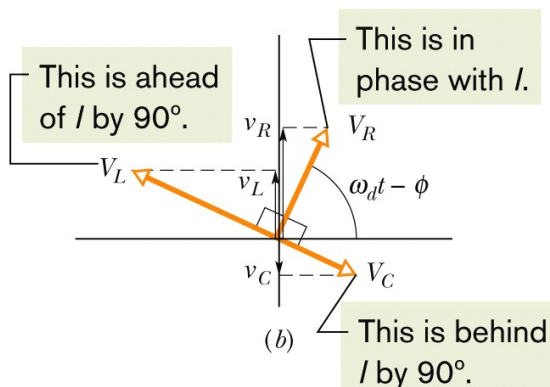Series RLC circuit  
with an external emf



$$\mathcal{E} = v_R + v_C + v_L.$$

Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

From the right-hand phasor triangle in Fig.(d) we can write

$$\tan \phi = \frac{V_L - V_C}{V_R} = \frac{IX_L - IX_C}{IR},$$



$$\tan \phi = \frac{X_L - X_C}{R}$$

**Phase Constant**


## 31-4 The Series RLC Circuits

From the right-hand phasor triangle in Fig.(d) we can write:

$$\mathcal{E}_m^2 = V_R^2 + (V_L - V_C)^2.$$

$$\rightarrow \mathcal{E}_m^2 = (IR)^2 + (IX_L - IX_C)^2,$$
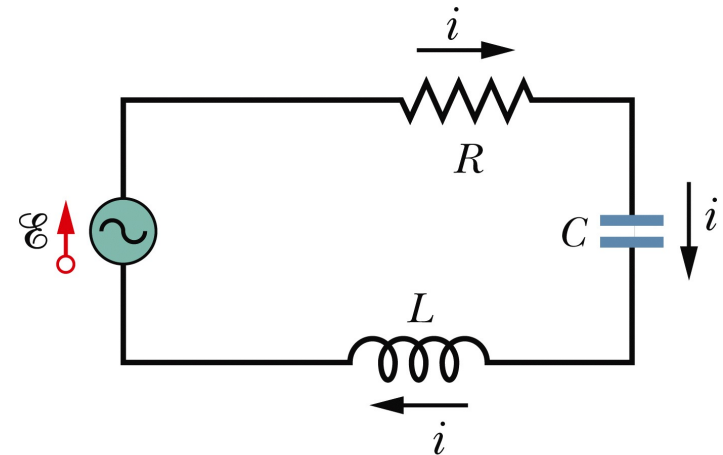
$$\rightarrow I = \frac{\mathcal{E}_m}{\sqrt{R^2 + (X_L - X_C)^2}}.$$



Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

Series RLC circuit  
with an external emf

The current amplitude  $I$  is maximum when the driving angular frequency  $\omega_d$  equals the natural angular frequency  $\omega$  of the circuit, a condition known as **resonance**. Then  $X_C = X_L$ ,  $\phi = 0$ , and the current is in phase with the emf.

$$\omega_d = \omega = \frac{1}{\sqrt{LC}} \quad (\text{resonance}).$$



## 31-5 Power in Alternating-Current Circuits

### Learning Objectives

**31.41** For the current, voltage, and emf in an ac circuit, apply the relationship between the rms values and the amplitudes.

**31.42** For an alternating emf connected across a capacitor, an inductor, or a resistor, sketch graphs of the sinusoidal variation of the current and voltage and indicate the peak and rms values.

**31.43** Apply the relationship between average power  $P_{avg}$ , rms current  $I_{rms}$ , and resistance  $R$ .

**31.44** In a driven RLC circuit, calculate the power dissipated by each element.

**31.45** For a driven RLC circuit in steady state, explain what happens to (a) the value of the average stored energy with time and (b) the energy that the generator puts into the circuit.

**31.46** Apply the relationship between the power factor  $\cos \phi$ , the resistance  $R$ , and the impedance  $Z$ .

## 31-5 Power in Alternating-Current Circuits

The instantaneous rate at which energy is dissipated in the resistor can be written as


$$P = i^2 R = [I \sin(\omega_d t - \phi)]^2 R = I^2 R \sin^2(\omega_d t - \phi).$$

Over one complete cycle, the average value of  $\sin \theta$ , where  $\theta$  is any variable, is zero (Fig.a) but the average value of  $\sin^2 \theta$  is  $1/2$  (Fig.b). Thus the power is,

$$P_{\text{avg}} = \frac{I^2 R}{2} = \left( \frac{I}{\sqrt{2}} \right)^2 R.$$

The quantity  $I/\sqrt{2}$  is called the **root-mean-square**, or rms, value of the current  $i$ :

$$I_{\text{rms}} = \frac{I}{\sqrt{2}}$$

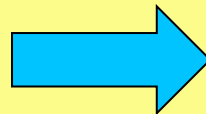


$$P_{\text{avg}} = I_{\text{rms}}^2 R$$

We can also define rms values of voltages and emfs for alternating-current circuits:


$$V_{\text{rms}} = \frac{V}{\sqrt{2}} \quad \text{and} \quad \mathcal{E}_{\text{rms}} = \frac{\mathcal{E}_m}{\sqrt{2}}$$

In a series RLC circuit, the average power  $P_{\text{avg}}$  of the generator is equal to the production rate of thermal energy in the resistor:
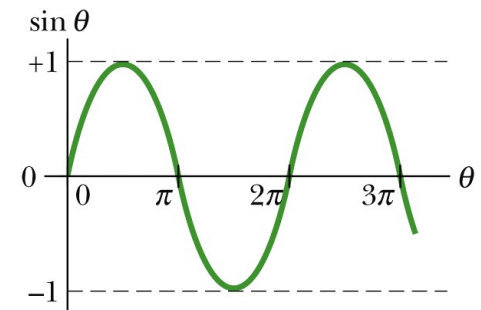
$$P_{\text{avg}} = \mathcal{E}_{\text{rms}} I_{\text{rms}} \cos \phi$$



(a)

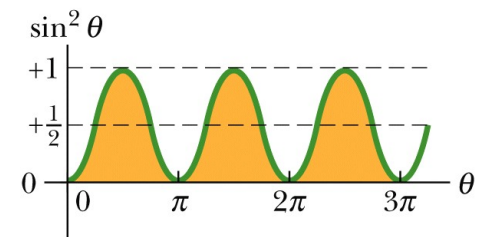

(b)

Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.


- (a) A plot of  $\sin \theta$  versus  $\theta$ . The average value over one cycle is zero.
- (b) A plot of  $\sin^2 \theta$  versus  $\theta$ . The average value over one cycle is  $1/2$ .

$$P_{\text{avg}} = \mathcal{E}_{\text{rms}} I_{\text{rms}} \cos \phi$$

$$I_{\text{rms}} = \frac{\mathcal{E}_{\text{rms}}}{Z} = \frac{\mathcal{E}_{\text{rms}}}{\sqrt{R^2 + (X_L - X_C)^2}},$$

$$P_{\text{avg}} = \frac{\mathcal{E}_{\text{rms}}}{Z} I_{\text{rms}} R = \mathcal{E}_{\text{rms}} I_{\text{rms}} \frac{R}{Z}.$$
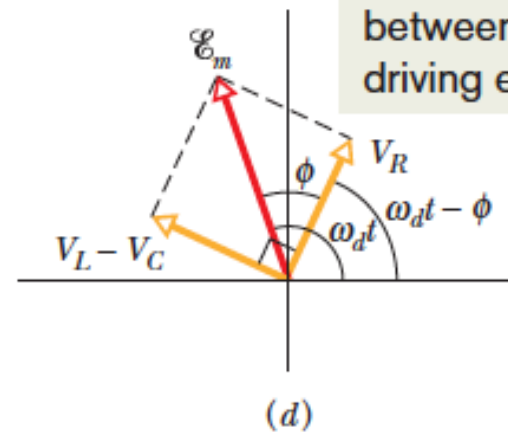
$$\cos \phi = \frac{V_R}{\mathcal{E}_m} = \frac{IR}{IZ} = \frac{R}{Z}.$$



This  $\phi$  is the angle between  $I$  and the driving emf.

## 31-6 Transformers

### Learning Objectives

**31.49** For power transmission lines, identify why the transmission should be at low current and high voltage.

**31.50** Identify the role of transformers at the two ends of a transmission line.

**31.51** Calculate the energy dissipation in a transmission line.

**31.52** Identify a transformer's primary and secondary.

**31.53** Apply the relationship between the voltage and number of turns on the two sides of a transformer.

**31.54** Distinguish between a step-down transformer and a step-up transformer.

**31.55** Apply the relationship between the current and number of turns on the two sides of a transformer.

**31.56** Apply the relationship between the power into and out of an ideal transformer.

# 31-6 Transformers

## Learning Objectives

**31.57** Identify the equivalent resistance as seen from the primary side of a transformer.

**31.58** Apply the relationship between the equivalent resistance and the actual resistance.

**31.59** Explain the role of a transformer in impedance matching.

## 31-6 Transformers

A **transformer** (assumed to be ideal) is an **iron core** on which are wound a **primary coil of  $N_p$  turns** and a **secondary coil of  $N_s$  turns**. If the primary coil is connected across an alternating-current generator, the primary and secondary voltages are related by


$$V_s = V_p \frac{N_s}{N_p}$$

**Energy Transfers.** The rate at which the generator transfers energy to the primary is equal to  $I_p V_p$ . The rate at which the primary then transfers energy to the secondary (via the alternating magnetic field linking the two coils) is  $I_s V_s$ . Because we assume that no energy is lost along the way, conservation of energy requires that

$$I_p V_p = I_s V_s \quad \longrightarrow \quad I_s = I_p \frac{N_p}{N_s}$$

The equivalent resistance of the secondary circuit, as seen by the generator, is
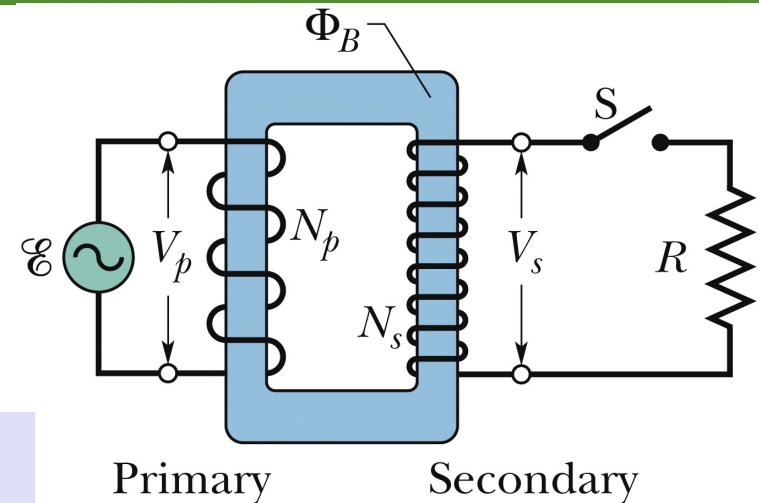
$$R_{\text{eq}} = \left( \frac{N_p}{N_s} \right)^2 R.$$



Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

An ideal transformer (two coils wound on an iron core) in a basic transformer circuit. An ac generator produces current in the coil at the left (the primary). The coil at the right (the secondary) is connected to the resistive load  $R$  when switch  $S$  is closed.

$$V_s = V_p \frac{N_s}{N_p}$$

Faraday's law of induction

$$\mathcal{E} = -N \frac{d\Phi_B}{dt}$$


$$\varepsilon_p (= V_p) = -N_p \frac{d\Phi}{dt} \quad \varepsilon_s (= V_s) = -N_s \frac{d\Phi}{dt}$$



$$V_s = V_p \frac{N_s}{N_p}$$

Transformation of voltage

## Transformer

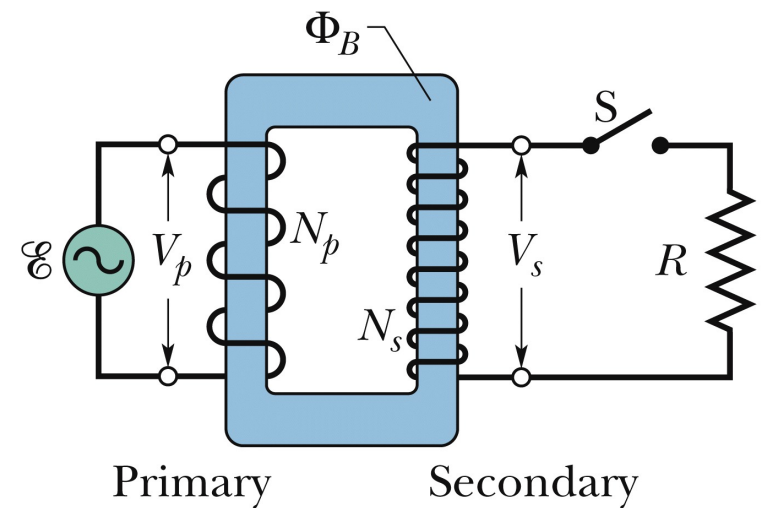

Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

220 V

110 V



# 31 Summary

## LC Energy Transfer

- In an oscillating LC circuit, instantaneous values of the two forms of energy are

$$U_E = \frac{q^2}{2C} \quad \text{and} \quad U_B = \frac{Li^2}{2} \quad \text{Eq. 31-1\&2}$$

## LC Charge and Current Oscillations

- The principle of conservation of energy leads to

$$L \frac{d^2q}{dt^2} + \frac{1}{C} q = 0 \quad \text{Eq. 31-11}$$

- The solution of Eq. 31-11 is

$$q = Q \cos(\omega t + \phi) \quad \text{Eq. 31-12}$$

- the angular frequency  $\omega$  of the oscillations is

$$\omega = \frac{1}{\sqrt{LC}}. \quad \text{Eq. 31-4}$$

## Damped Oscillations

- Oscillations in an LC circuit are damped when a dissipative element  $R$  is also present in the circuit. Then

$$L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = 0 \quad \text{Eq. 31-24}$$

- The solution of this differential equation is

$$q = Q e^{-Rt/2L} \cos(\omega' t + \phi), \quad \text{Eq. 31-25}$$

## Alternating Currents; Forced Oscillations

- A series RLC circuit may be set into forced oscillation at a driving angular frequency by an external alternating emf

$$\mathcal{E} = \mathcal{E}_m \sin \omega_d t. \quad \text{Eq. 31-28}$$

- The current driven in the circuit is

$$i = I \sin(\omega_d t - \phi) \quad \text{Eq. 31-29}$$

# 31 Summary

## Series RLC Circuits

- For a series RLC circuit with an alternating external emf and a resulting alternating current,

$$I = \frac{\mathcal{E}_m}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$= \frac{\mathcal{E}_m}{\sqrt{R^2 + (\omega_d L - 1/\omega_d C)^2}}$$

Eq. 31-60&amp;63

- and the phase constant is,

$$\tan \phi = \frac{X_L - X_C}{R}$$

Eq. 31-65

- The impedance is

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Eq. 31-61

## Power

- In a series RLC circuit, the average power of the generator is,

$$P_{\text{avg}} = I_{\text{rms}}^2 R = \mathcal{E}_{\text{rms}} I_{\text{rms}} \cos \phi.$$

Eq. 31-71&amp;76

## Transformers

- Primary and secondary voltage in a transformer is related by

$$V_s = V_p \frac{N_s}{N_p}$$

Eq. 31-79

- The currents through the coils,

$$I_s = I_p \frac{N_p}{N_s}$$

Eq. 31-80

- The equivalent resistance of the secondary circuit, as seen by the generator, is

$$R_{\text{eq}} = \left( \frac{N_p}{N_s} \right)^2 R,$$

Eq. 31-82