

# Logic Design with Verilog II: Basic Syntax and Combinational Logic

Jae W. Lee (jaewlee@snu.ac.kr)

Department of Computer Science and Engineering  
Seoul National University

Slide credits: Prof. Ming-Bo Lin (Digital System Designs and Practices Using Verilog HDL and FPGAs)


# Outline

---

- Modules
  - Concept
  - Definitions
  - Parameters
  - Module instantiation
  - Parameter values
- Generate statements
- Module modeling styles
- Simulation
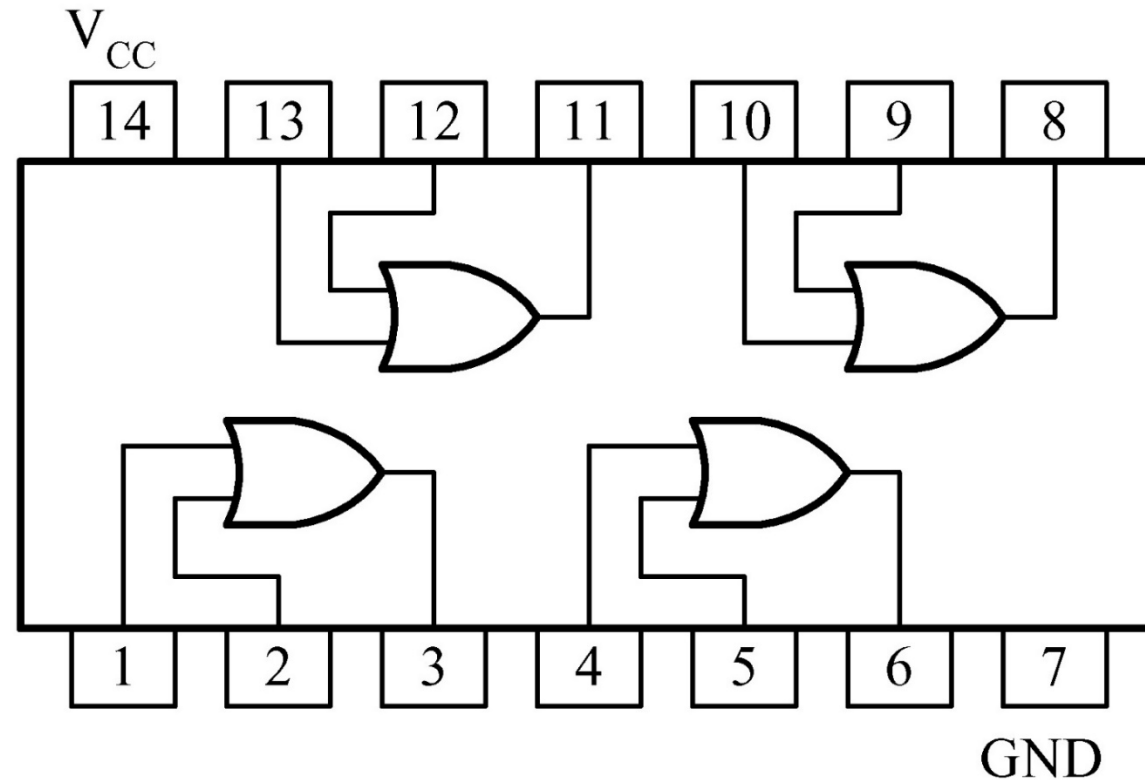
# Modules: Concept

- Concept of module
  - A core circuit (called internal or body)
  - An interface (called ports)



# Modules: Concept

---

- Module in Verilog: basic building block

*module* Module name

Port List, Port Declarations (if any)

Parameters (if any)

Declarations of *wires*, *regs*, and other variables

Instantiation of lower level modules or primitives

Dataflow statements (*assign*)

*always* and *initial* blocks. (all behavioral statements go into these blocks).

Tasks and functions.

*endmodule* statement

# Modules: Definitions

---

- Module definitions

```
// port list style
module module_name [#(parameter_declarations)][port_list];
parameter_declarations; // if no parameter ports are used
port_declarations;
other_declaration;
statements;
endmodule
```

```
// port list declaration style
module module_name [#(parameter_declarations)][port_declarations];
parameter_declarations; // if no parameter ports are used
other_declarations;
statements;
endmodule
```

# Modules: Definitions

- Example: module definitions

```
module FIND_PMV_QME (
    CLK,
    RSTn,
    en,
    mv_a,
    mv_b,
    mv_c,
    pred_type,
    x_pmv,
    y_pmv
);
    parameter MEDIAN = 2'b00, LEFT = 2'b01, UPPER = 2'b10, UPLEFT = 2'b11;
    input          CLK, RSTn, en;
    input  [31:0]  mv_a, mv_b, mv_c;
    input  [ 1:0]  pred_type;
    output [ 8:0]  x_pmv, y_pmv;
    reg     [ 8:0]  x_pmv, y_pmv;

    reg  [ 1:0]  x_median, y_median;
    wire      x_ab, x_ac, x_bc;
    wire      y_ab, y_ac, y_bc;
endmodule
```

Port list style

```
module MC_BLOCK_ASSIGN(
    input          CLK, RSTn,
    input          mc_block_assign_start,
    input  [40:0]  do_mc_block, mc_done_block,

    input  [17:0]  vect_00_i, vect_01_i, vect_02_i, vect_03_i, vect_04_i,
                    vect_05_i, vect_06_i, vect_07_i, vect_08_i, vect_09_i,
                    vect_10_i, vect_11_i, vect_12_i, vect_13_i, vect_14_i,
                    vect_15_i, vect_16_i, vect_17_i, vect_18_i, vect_19_i,
                    vect_20_i, vect_21_i, vect_22_i, vect_23_i, vect_24_i,
                    vect_25_i, vect_26_i, vect_27_i, vect_28_i, vect_29_i,
                    vect_30_i, vect_31_i, vect_32_i, vect_33_i, vect_34_i,
                    vect_35_i, vect_36_i, vect_37_i, vect_38_i, vect_39_i,
                    vect_40_i,

    output reg [ 5:0]  mc_block,
    output reg [ 5:0]  bx_init_mc, bx_end_mc, by_init_mc, by_end_mc,
    output reg          mc_last_block,
    output reg          mc_block_assign_done
);
    reg  [6:0]  ivect_x, ivect_y;
    reg  [4:0]  x_size, y_size;
    reg          mc_block_assign_start_d, mc_block_assign_start_d2;
    reg  [40:0]  mc_next_block_inverted;
endmodule
```

Port list declaration style

# Modules: Definitions

- Example: module definitions
  - Variable names
    - All undeclared variables are wires and are one bit wide.
    - Good Practice: **Declare all variables!!**

```
3 module mux2 (out, in1, in2, sel);
4
5     // Port declaration
6     output out;
7     input  in1, in2, sel;
8
9     // Variable declaration
10    reg     out;
11
12    // Mux2
13    always @(in1 or in2 or sel) begin
14        if (sel)    out = in1;
15        else        out = in2;
16    end
17
18 endmodule
```

```
3 module mux2 (out, in1, in2, sel);
4
5     // Port declaration
6     output out;
7     input  in1, in2, sel;
8
9     // Mux2
10    wire    out = sel ? in1 : in2;
11
12 endmodule
```

# Modules: Definitions

## ■ Port declaration: Types of ports

- input
- output
- inout



```
module adder(x, y, c_in, sum, c_out);  
input [3:0] x, y;  
input c_in;  
output reg [3:0] sum;  
output reg c_out;
```



# Modules: Parameters

---

## ■ Types of Parameters

- Module parameters
  - parameter
  - localparam
- Specify parameters

```
parameter SIZE = 7;  
parameter WIDTH_BUSA = 24, WIDTH_BUSB = 8;  
parameter signed [3:0] mux_selector = 4'b0;
```

# Modules: Parameters

---

- Options for constant specification
  - ``define` compiler directive  
``define BUS_WIDTH 8`  
defined at outside of module (applied to entire code)
  - `parameter`  
`parameter BUS_WIDTH = 8;`  
cannot defined at outside of module
  - `localparam`  
`localparam BUS_WIDTH = 8;`  
cannot defined at outside of module

# Modules: Parameters

---

- Parameter ports

```
module module_name
#(parameter SIZE = 7,
    parameter WIDTH_BUSA = 24, WIDTH_BUSB = 8,
    parameter signed [3:0] mux_selector = 4'b0
) //parameter ports
(port list or port list declarations)
...
endmodule
```

# Modules: Module Instantiation

---

- **Syntax**

`module_name` [#(parameters)] `instance_name` ([ports]);

- **Port Connection Rules**

- Named association  
(`.port_id1(port_expr1), ..., .port_idn(port_exprn)`)
- Positional association  
(`port_expr1, ..., port_exprn`)

# Modules: Module Instantiation

---

- Port connection rules

- Named association

```
shift_reg shift_reg_1(    //module name and instance of the module
    .clk      (clk_50),    //the pin clk is connected to the wire clk_50
    .reset_n   (reset_n),  //the "." denotes the pin
    .data_ena  (data_ena), //the value in the parens is the wire
    .serial_data (serial_data),
    .parallel_data (shift_reg_out)); //wires and pins do not have to match
[show with arrows and such the various parts]
```

- Positional association

```
shift_reg shift_reg_1(clk_50,reset_n,data_ena,serial_data,shift_reg_out);
```

How do you know its connected correctly?

What if the module had 50 pins on it?

What if you wanted to add wire in the middle of the list?

*Do not use Positional Association!*

It saves time once, and costs you dearly afterwards

# Modules: Module Instantiation

## ■ Example: Port Connection

```
module half_adder (x, y, s, c);  
input x, y;  
output s, c;  
// -- half adder body-- //  
// instantiate primitive gates  
xor xor1 (s, x, y);  
and and1 (c, x, y);  
endmodule
```

Can only be connected by using positional association

Instance name is optional.

```
module full_adder (x, y, cin, s, cout);  
input x, y, cin;  
output s, cout;  
wire s1, c1, c2; // outputs of both half adders  
// -- full adder body-- //  
// instantiate the half adder  
half_adder ha_1 (x, y, s1, c1);  
half_adder ha_2 (.x(cin), .y(s1), .s(s), .c(c2));  
or (cout, c1, c2);  
endmodule
```

Connecting by using positional association

Connecting by using named association

Instance name is necessary.

# Modules: Parameter Values

---

- Parameterized modules

```
module adder_nbit(x, y, c_in, sum, c_out);  
parameter N = 4;    // set default value  
input [N-1:0] x, y;  
input c_in;  
output [N-1:0] sum;  
output c_out;  
  
assign {c_out, sum} = x + y + c_in;  
endmodule
```

# Modules: Parameter Values

- Overriding parameters: Using defparam statement

```
module counter_nbits (clock, clear, qout);  
parameter N = 4; // define counter size  
always @(negedge clock or posedge clear)  
begin // qout <= (qout + 1) % 2^n  
    if (clear) qout <= {N{1'b0}};  
    else      qout <= (qout + 1) ;  
end
```

```
// define top level module  
...  
output [3:0] qout4b;  
output [7:0] qout8b;  
// instantiate two counter modules  
defparam cnt_4b.N = 4, cnt_8b.N = 8;  
counter_nbits cnt_4b (clock, clear, qout4b);  
counter_nbits cnt_8b (clock, clear, qout8b);
```



# Modules: Parameter Values

- Overriding parameters: Using module instance parameter value as signment - one parameter

```
module counter_nbits (clock, clear, qout);  
parameter N = 4; // define counter size  
...  
always @(negedge clock or posedge clear)  
begin // qout <= (qout + 1) % 2^n;  
    if (clear) qout <= {N{1'b0}};  
    else      qout <= (qout + 1) ;  
end
```

```
// define top level module  
...  
output [3:0] qout4b;  
output [7:0] qout8b;  
// instantiate two counter modules  
counter_nbits #(4) cnt_4b (clock, clear, qout4b);  
counter_nbits #(8) cnt_8b (clock, clear, qout8b);
```

# Modules: Parameter Values


- Overriding parameters: Using module instance parameter value as signment - two parameters

```
module hazard_static (x, y, z, f);  
parameter delay1 = 2, delay2 = 5;  
...  
    and #delay2 a1 (b, x, y);  
    not #delay1 n1 (a, x);  
    and #delay2 a2 (c, a, z);  
    or #delay2 o2 (f, b, c);  
endmodule
```

```
// define top level module  
module ...  
...  
hazard_static #(4, 8) example (x, y, z, f);
```

```
hazard_static #(.delay2(4), .delay1(6))  
example (x, y, z, f);
```

 - parameter value assignment by name ---  
**minimize the chance of error!**



# Outline

---

- Module
- **Generate statements**
  - Generate-loop statements
  - Generate-conditional statements
- Module modeling styles
- Simulation

# Generate-loop Statements

---

- generate block structures
  - Keywords: `generate` and `endgenerate`

```
// convert Gray code into binary code
parameter SIZE = 8;
input  [SIZE-1:0] gray;
output [SIZE-1:0] bin;
genvar i;
generate for (i = 0; i < SIZE; i = i + 1)
begin: bit
    assign bin[i] = ^gray[SIZE-1:i];
end endgenerate
```

# Generate-loop Statements

---

- generate loop construct

```
// convert Gray code into binary code
parameter SIZE = 8;
input  [SIZE-1:0] gray;
output [SIZE-1:0] bin;
reg     [SIZE-1:0] bin;

genvar i;
generate for (i = 0; i < SIZE; i = i + 1)
begin:bit
    always @(*)
        bin[i] = ^gray[SIZE - 1: i];
end endgenerate
```

# Generate-Conditional Statements

---

- Full adder

```
// define a full adder at dataflow level.  
module full_adder(x, y, c_in, sum, c_out);  
// I/O port declarations  
input  x, y, c_in;  
output sum, c_out;  
// Specify the function of a full adder.  
    assign {c_out, sum} = x + y + c_in;  
endmodule
```

# Generate-Conditional Statements

- $n$ -bit adder

```
module adder_nbit(x, y, c_in, sum, c_out);
...
genvar i;
wire [N-2:0] c;           // internal carries declared as nets.
generate for (i = 0; i < N; i = i + 1) begin: adder
    if (i == 0)            // specify LSB
        full_adder fa (_____);
    else if (i == N-1)     // specify MSB
        full_adder fa (_____);
    else                   // specify other bits
        full_adder fa (_____);
end endgenerate
```

# Generate-Conditional Statements

- $n$ -bit adder: An alternative

```
module adder_nbit(x, y, c_in, sum, c_out);
...
genvar i;
wire [N-2:0] c;           // internal carries declared as nets.
generate for (i = 0; i < N; i = i + 1) begin: adder
    if (i == 0)            // specify LSB
        assign {_____} = x[i] + y[i] + c_in;
    else if (i == N-1)     // specify MSB
        assign {_____} = x[i] + y[i] + c[i-1];
    else                   // specify other bits
        assign {_____} = x[i] + y[i] + c[i-1];
end endgenerate
```



# Generate-Conditional Statements

- $n$ -bit adder: Yet another alternative

```
module adder_nbit(x, y, c_in, sum, c_out);
...
genvar i;
reg      [N-2:0] c;           // internal carries declared as nets.
generate for (i = 0; i < N; i = i + 1) begin: adder
    if (i == 0)               // specify LSB
        always @(*) {_____} = x[i] + y[i] + c_in;
    else if (i == N-1)        // specify MSB
        always @(*) {_____} = x[i] + y[i] + c[i-1];
    else                       // specify other bits
        always @(*) {_____} = x[i] + y[i] + c[i-1];
end endgenerate
```

# Outline

---

- Module
- Generate statements
- **Module modeling styles**
- Simulation


# Module Modeling Styles

---

- **Structural style**
  - Gate level
  - Hierarchical design
- Dataflow style
- Behavioral or algorithmic style
- Mixed style


# Structural Style: and/nand Gates

- Verilog primitive

 

and		i2			
		0	1	x	z
i1	0	0	0	0	0
	1	0	1	x	x
	x	0	x	x	x
	z	0	x	x	x

(a) and gate

 


nand		i2			
		0	1	x	z
i1	0	1	1	1	1
	1	1	0	x	x
	x	1	x	x	x
	z	1	x	x	x

(b) nand gate


# Structural Style: or/nor Gates

- Verilog primitive

 

or		i2			
		0	1	x	z
i1	0	0	1	x	x
	1	1	1	1	1
	x	x	1	x	x
	z	x	1	x	x

(c) or gate

 


nor		i2			
		0	1	x	z
i1	0	1	0	x	x
	1	0	0	0	0
	x	x	0	x	x
	z	x	0	x	x

(d) nor gate


# Structural Style: xor/xnor Gates

- Verilog primitive

 

xor		i2			
		0	1	x	z
i1	0	0	1	x	x
	1	1	0	x	x
	x	x	x	x	x
	z	x	x	x	x

(e) xor gate

 


xnor		i2			
		0	1	x	z
i1	0	1	0	x	x
	1	0	1	x	x
	x	x	x	x	x
	z	x	x	x	x

(f) xnor gate


# Structural Style: buf/not Gates

- Verilog primitive

 

in	out
0	0
1	1
x	x
z	x

(a) buffer

 

in	out
0	1
1	0
x	x
z	x

(b) not gate


# Structural Style: Instantiation of Basic Gates

- To instantiate and/or gates

gatename [instance\_name](**output**, input1, input2, ..., inputn);

- instance\_name is **optional**
 
```
module basic_gates (x, y, z, f) ;  
input  x, y, z;  
output f ;  
wire a, b, c;  
// Structural modeling  
    nor g1  (b, x, y);  
    not  g2  (a, x);  
    and  g3  (c, a, z);  
    nor  g4  (f, b, c);  
endmodule
```



**Optional**



# Structural Style: Array of Instances

---

- **Array instantiations** may be a synthesizer dependent!
  - **Suggestion: check this feature before using the synthesizer**


```
wire [3:0] out, in1, in2;  
// basic array instantiations of nand gate.  
nand n_gate[3:0] (out, in1, in2);  
  
// this is equivalent to the following, this is better  
nand n_gate0 (out[0], in1[0], in2[0]);  
nand n_gate1 (out[1], in1[1], in2[1]);  
nand n_gate2 (out[2], in1[2], in2[2]);  
nand n_gate3 (out[3], in1[3], in2[3]);
```

# Structural Style: An Example

```
module full_adder_structural(x, y,
c_in, sum, c_out);
// I/O port declarations
input  x, y, c_in;
output sum, c_out;
wire  s1, c1, c2;
// Structural modeling of the 1-bit
full adder.
    xor  xor_s1(s1, x, y); // compute
sum.
    xor  xor_s2(sum, s1, c_in);
    and  and_c1(c1, x, y); // compute
carry out.
    and  and_c2(c2, s1, c_in);
    or   or_cout(c_out, c1, c2); // can
be xor
endmodule
```

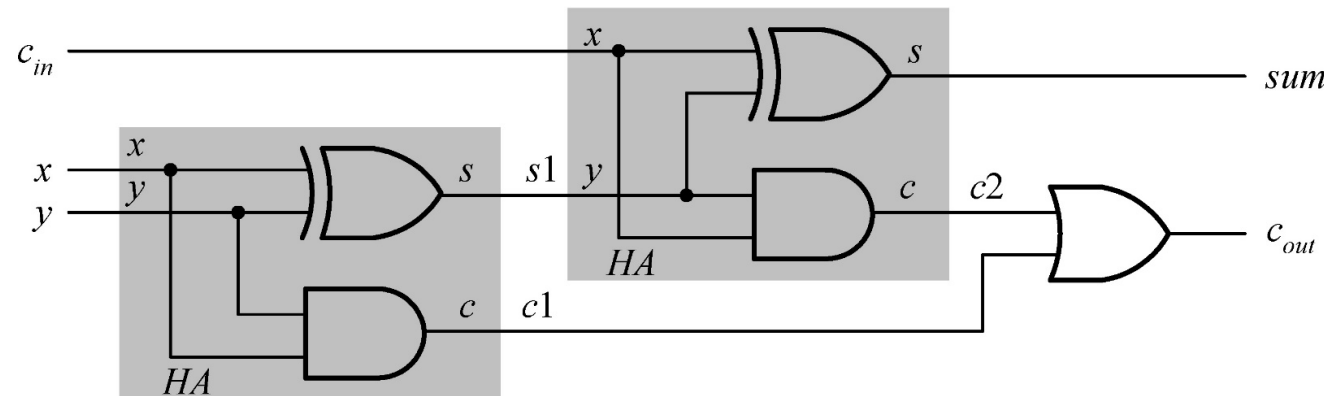
## ■ 1-bit full adder

$$\begin{aligned} \text{sum} &= (a \oplus b \oplus c_{in}) \\ c_{out} &= (a \cdot b) + c_{in} \cdot (a \oplus b) \end{aligned}$$



# Structural Style: Hierarchical Design

- Example: 4-bit adder

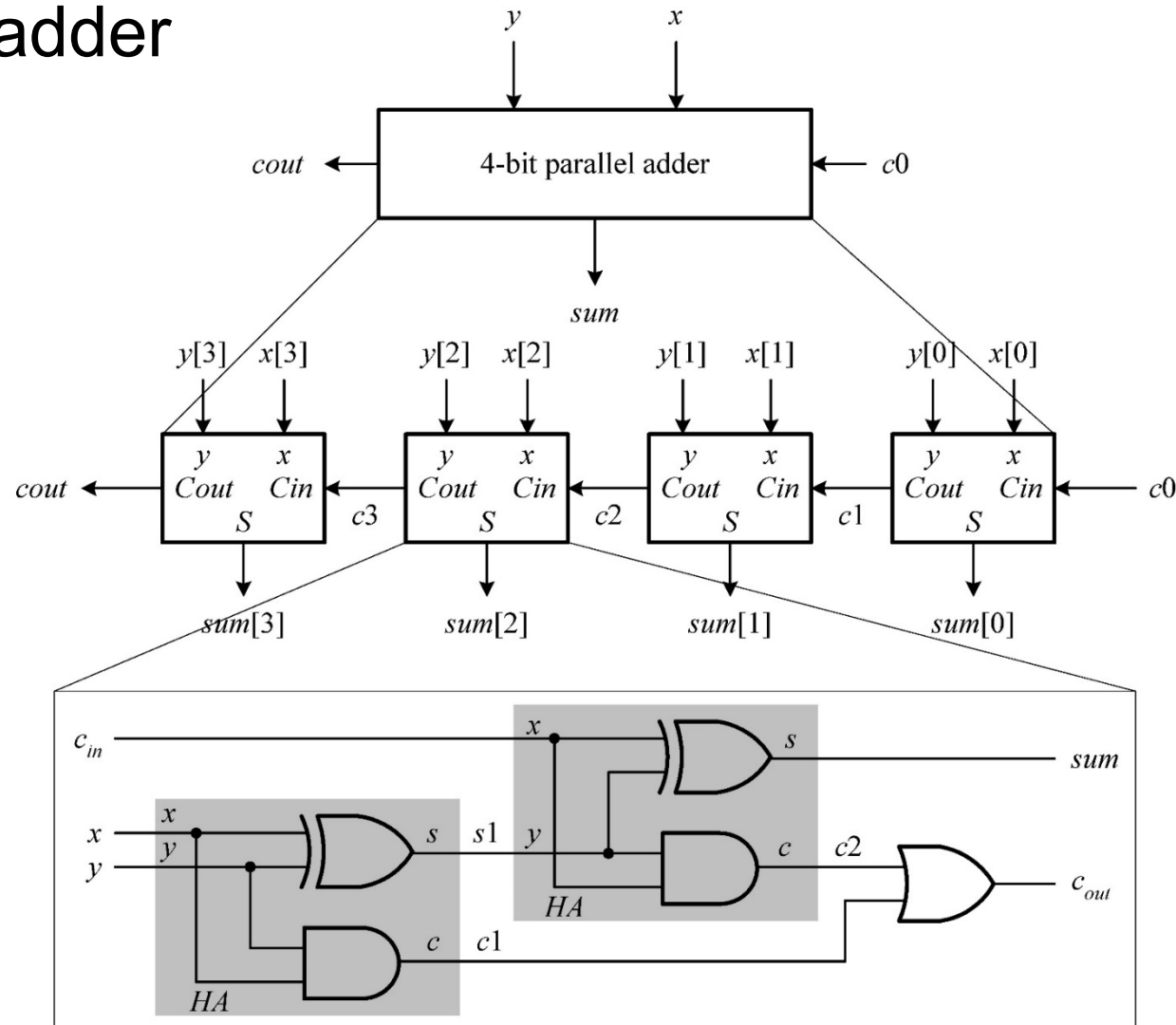

# Structural Style: Hierarchical Design

- Example: 4-bit adder

```
// gate-level description of 4-bit adder
module four_bit_adder (x, y, c_in, sum, c_out);
input [3:0] x, y;
input c_in;
output [3:0] sum;
output c_out;
wire c1, c2, c3; // intermediate carries
// four_bit adder body
// instantiate the full adder
full_adder fa_1 (x[0], y[0], c_in, sum[0], c1);
full_adder fa_2 (x[1], y[1], c1, sum[1], c2);
full_adder fa_3 (x[2], y[2], c2, sum[2], c3);
full_adder fa_4 (x[3], y[3], c3, sum[3], c_out);
endmodule
```

# Module Modeling Styles

---

- Structural style
- **Dataflow style**
- Behavioral or algorithmic style
- Mixed style

# Dataflow Style

```
module full_adder_dataflow(x, y, c_in, sum, c_out);  
  // I/O port declarations  
  input x, y, c_in;  
  output sum, c_out;  
  // specify the function of a full adder  
  assign {c_out, sum} = x + y + c_in;  
endmodule
```



# Module Modeling Styles

---

- Structural style
  - Gate level
- Dataflow style
- **Behavioral or algorithmic style**
- Mixed style

# Behavioral Style

---


- Similar with a C-code
- Flip-Flop implementation

```
module full_adder_behavioral(x, y, c_in, sum, c_out);  
  // I/O port declarations  
  input x, y, c_in;  
  output sum, c_out;  
  reg sum, c_out;  // need to be declared as reg types, output reg  
  
  // specify the function of a full adder  
  always @(x, y, c_in) // always @(*) or always@(x or y or c_in)  
    {c_out, sum} = x + y + c_in;  
endmodule
```




# Behavioral Style: Example #1

- 2-to-4 decoder

 

$E$	$x_1$	$x_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
1	$\phi$	$\phi$	1	1	1	1
0	0	0	1	1	1	0
0	0	1	1	1	0	1
0	1	0	1	0	1	1
0	1	1	0	1	1	1

(b) Function table

 

(c) Logic circuit



# Behavioral Style: Example #1'

- 2-to-4 decoder with enable control

```
// a 2-to-4 decoder with active-high output
```

```
always @ (x or enable)
```

```
    if (!enable) y = 4'b0000;
```

```
    else
```

```
        case (x)
```

```
            2'b00 : y = 4'b0001;
```


```
            2'b01 : y = 4'b0010;
```

```
            2'b10 : y = 4'b0100;
```

```
            2'b11 : y = 4'b1000;
```

```
        default : y = 4'b0000;
```

```
    endcase
```

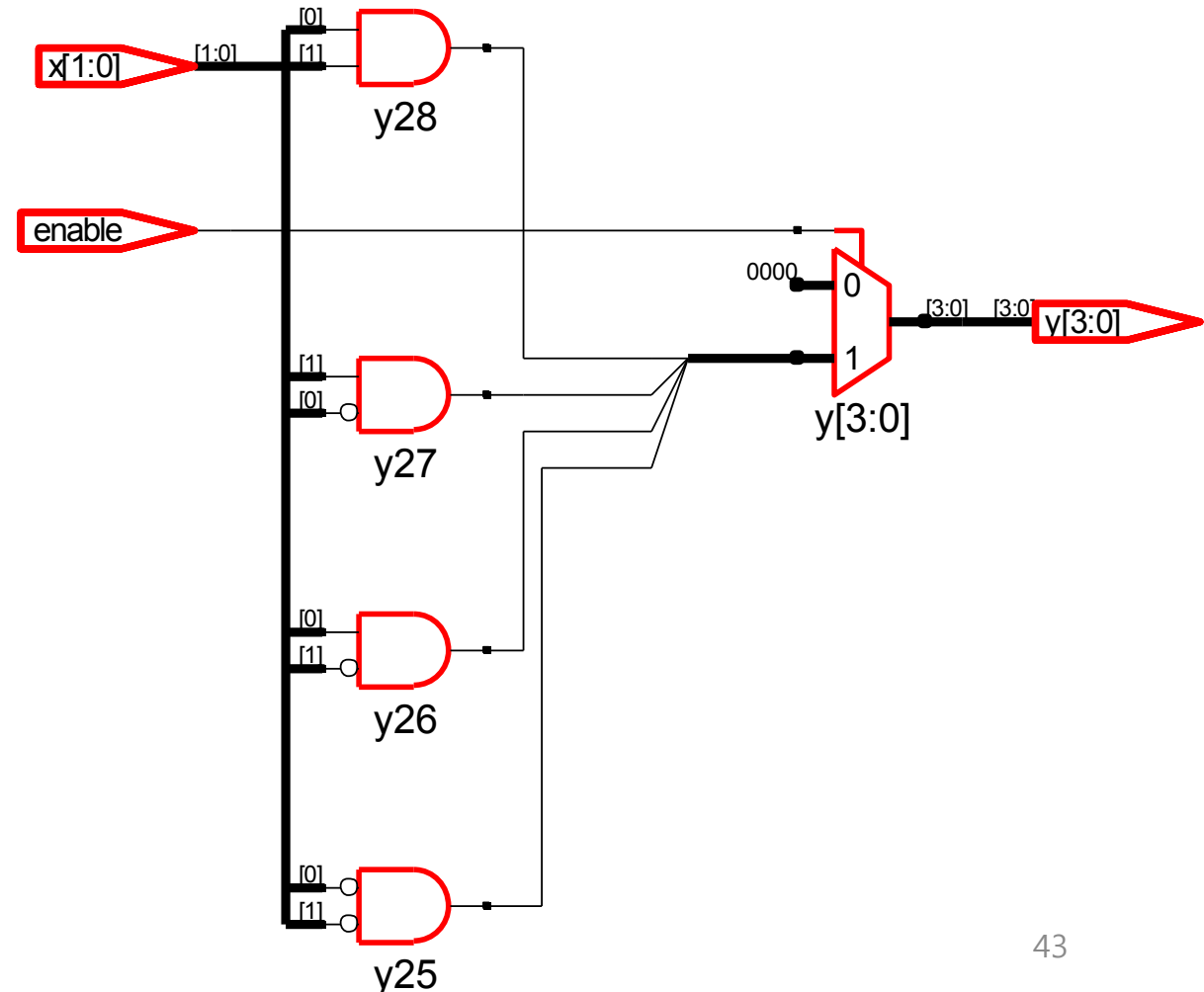


# Behavioral Style: Example #2

- 4-to-2 encoder

$I_3$	$I_2$	$I_1$	$I_0$	$Y_1$	$Y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

(a) Function table

 


(b) Logic circuit

# Behavioral Style: Example #2

- 4-to-2 encoder: if ... else

```
// a 4-to-2 encoder using if ... else  
structure
```

 
```
always @ (in) begin  
    if (in == 4'b0001) y = 0;  
    else if (in == 4'b0010) y = 1;  
    else if (in == 4'b0100) y = 2;  
    else if (in == 4'b1000) y = 3;  
    else y = 2'bx;  
end
```


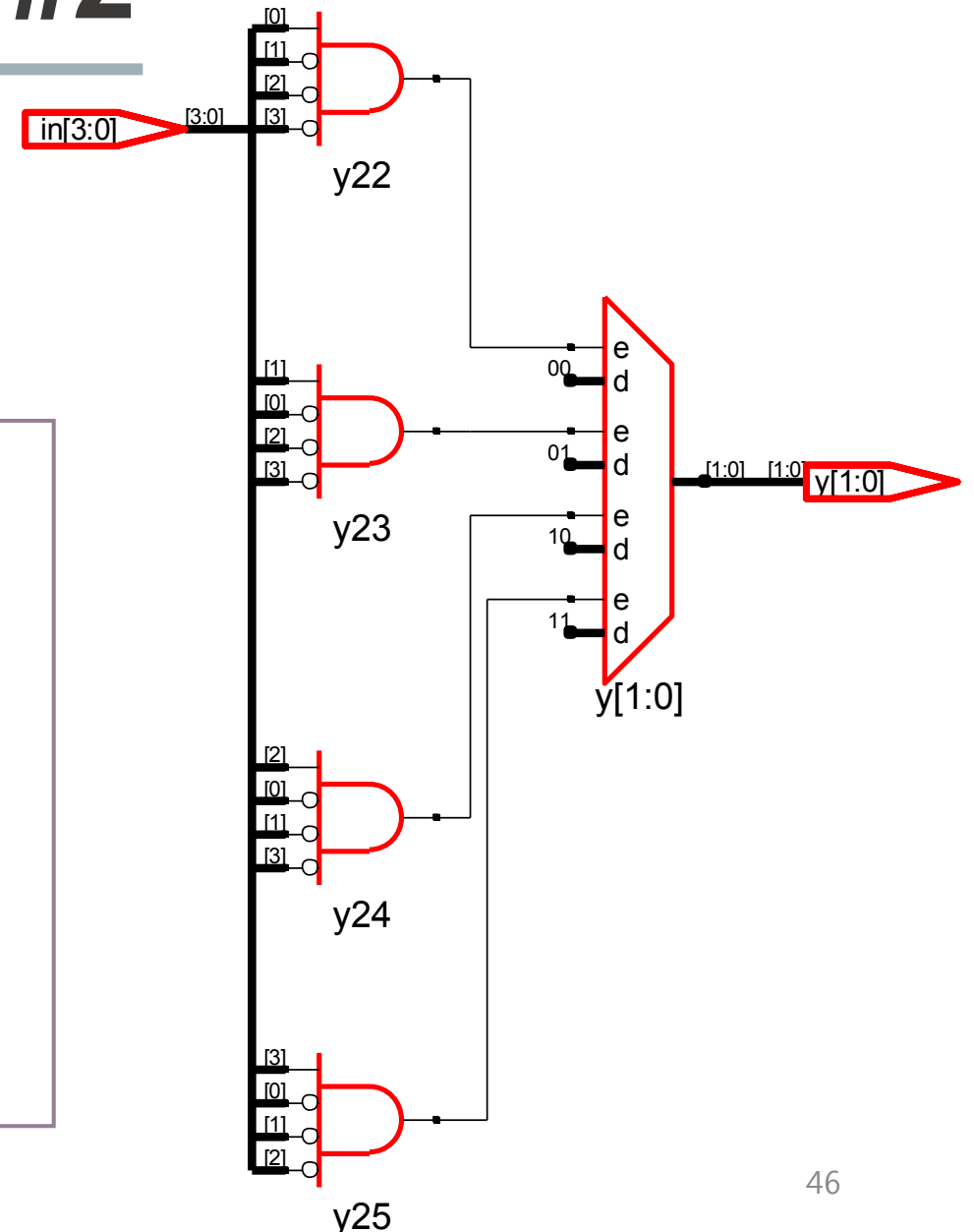
# Behavioral Style: Example #2


- 4-to-2 encoder: case statement

```
// a 4-to-2 encoder using case structure
always @ (in)
  case (in)
    4'b0001 : y = 0;
    4'b0010 : y = 1;
    4'b0100 : y = 2;
    4'b1000 : y = 3;
    default : y = 2'bx;
  endcase
```



# Behavioral Style: Example #3

- 4-to-2 priority encoder

 

(a) Block diagram


Input				Output	
$I_3$	$I_2$	$I_1$	$I_0$	$A_1$	$A_0$
0	0	0	1	0	0
0	0	1	$\phi$	0	1
0	1	$\phi$	$\phi$	1	0
1	$\phi$	$\phi$	$\phi$	1	1

(b) Function table

# Behavioral Style: Example #3

- 4-to-2 priority encoder: if ... else

```
// using if ... else structure
assign valid_in = |in;
always @(in) begin
    if (in[3]) y = 3;
    else if (in[2]) y = 2;
    else if (in[1]) y = 1;
    else if (in[0]) y = 0;
    else y = 2'bx;
end
```

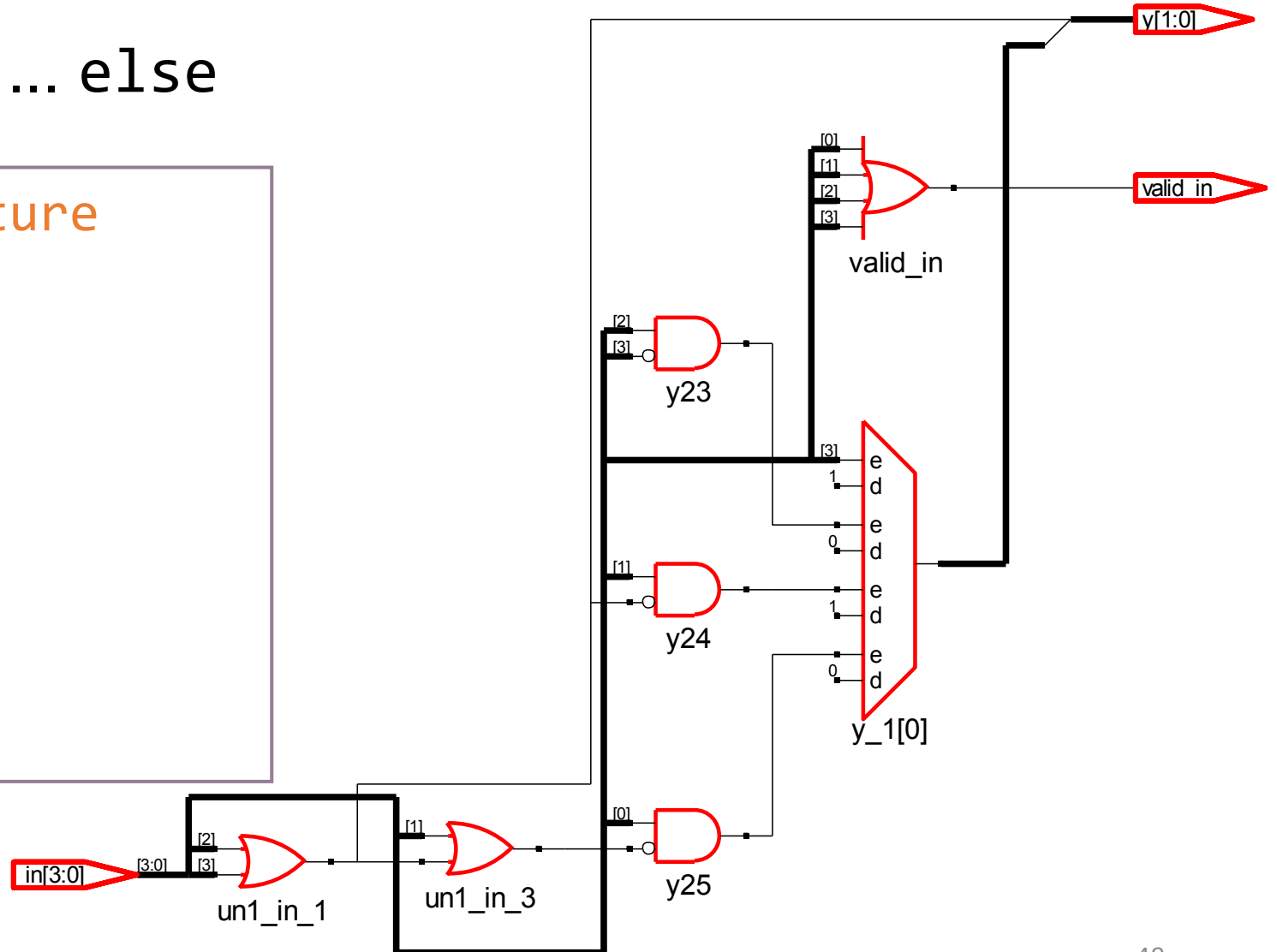




# Behavioral Style: Example #3


- 4-to-2 priority encoder: case statement

```
// using casex structure
assign valid_in = |in;
always @ (in)
  casex (in)
    4'b1xxx: y = 3;
    4'b01xx: y = 2;
    4'b001x: y = 1;
    4'b0001: y = 0;
    default: y = 2'bx;
  endcase
```

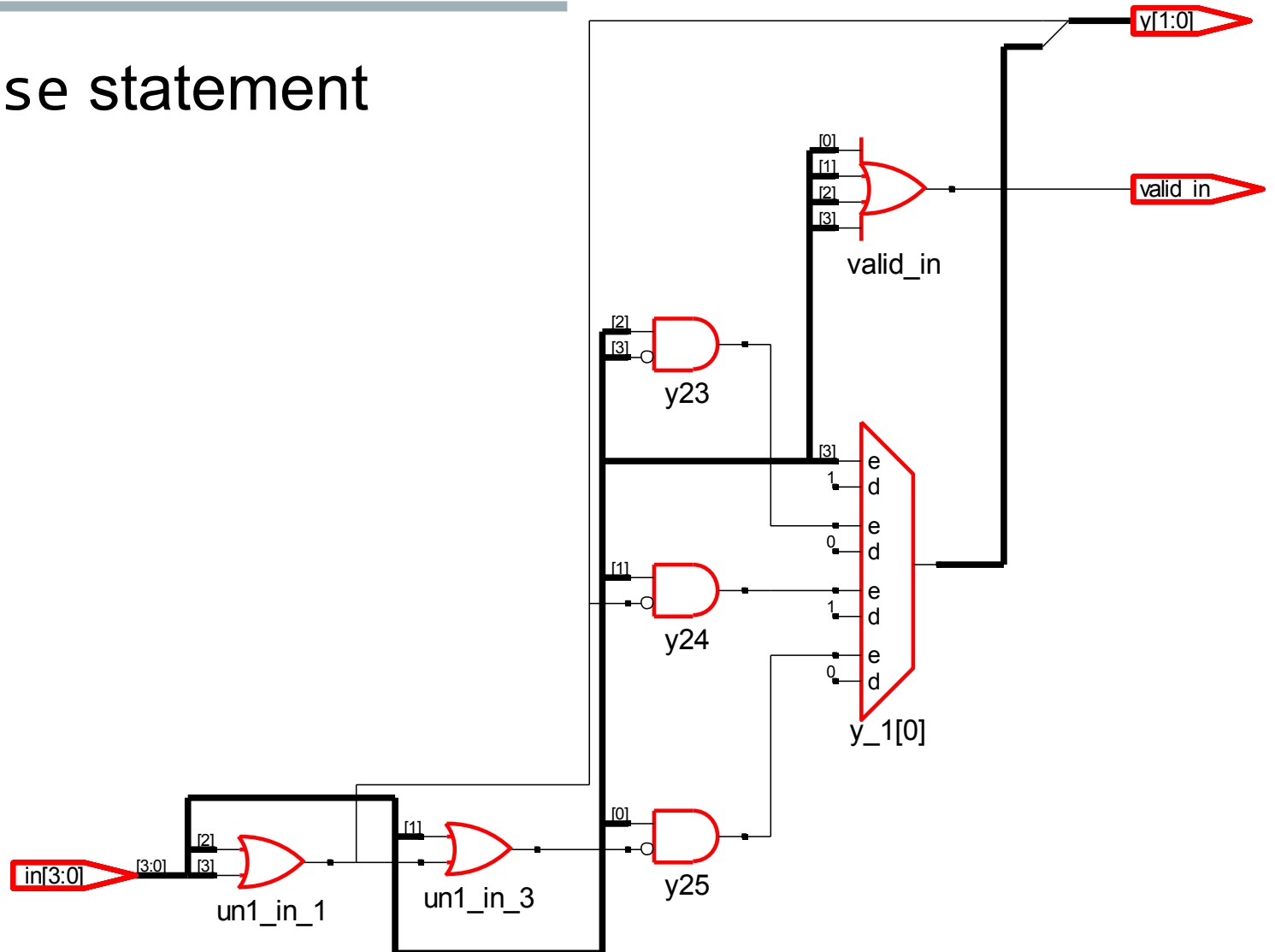

# Behavioral Style: Example #4


## ■ 4-to-1 multiplexer

 

(a) Logic symbol

$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

(b) Function table

 


(c) Logic circuit

# Behavioral Style: Example #4'

- *n*-bit 4-to-1 Multiplexer

```
// an N-bit 4-to-1 multiplexer using  
conditional operator
```
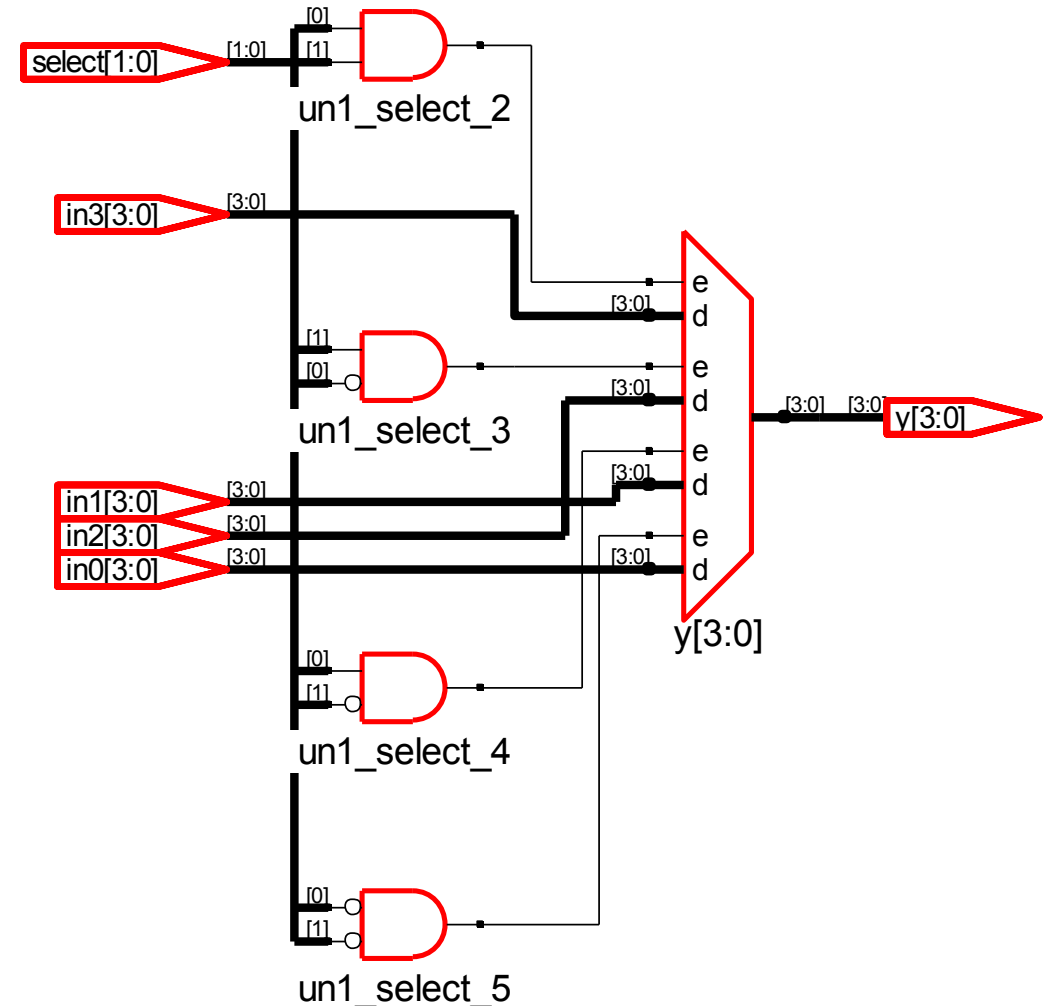
```
parameter N = 4;  
input [1:0] select;  
input [N-1:0] in3, in2, in1, in0;  
output [N-1:0] y;  
assign y = select[1] ?  
    (select[0] ? in3 : in2) :  
    (select[0] ? in1 : in0) ;
```




# Behavioral Style: Example #4"

- $n$ -bit 4-to-1 multiplexer with enable

```
// an N-bit 4-to-1 multiplexer with enable  
control
```

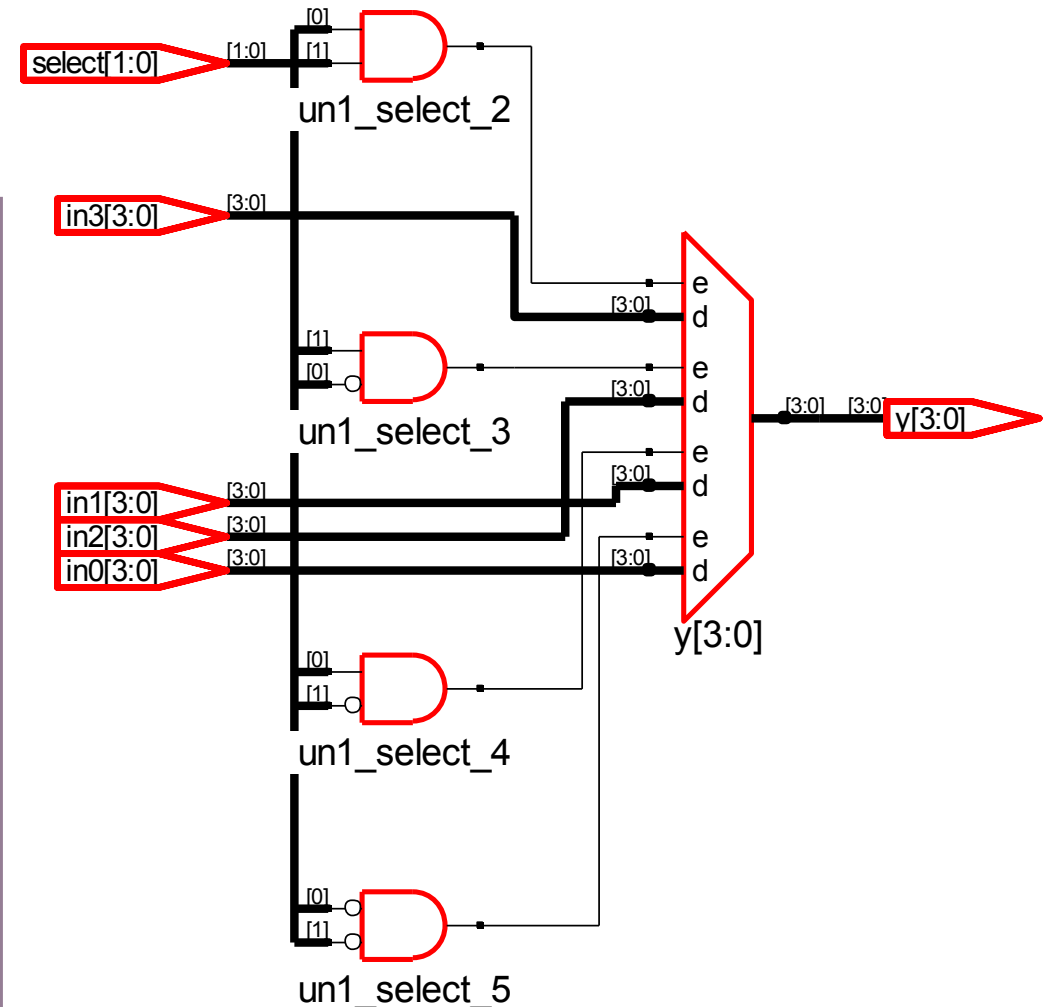
```
parameter N = 4;  
input [1:0] select;  
input enable;  
input [N-1:0] in3, in2, in1, in0;  
output reg [N-1:0] y;  
  
always @(select or enable or in0 or in1 or in2  
or in3)  
    if (!enable) y = {N{1'b0}};  
    else y = select[1] ?  
        (select[0] ? in3 : in2) :  
        (select[0] ? in1 : in0) ;
```


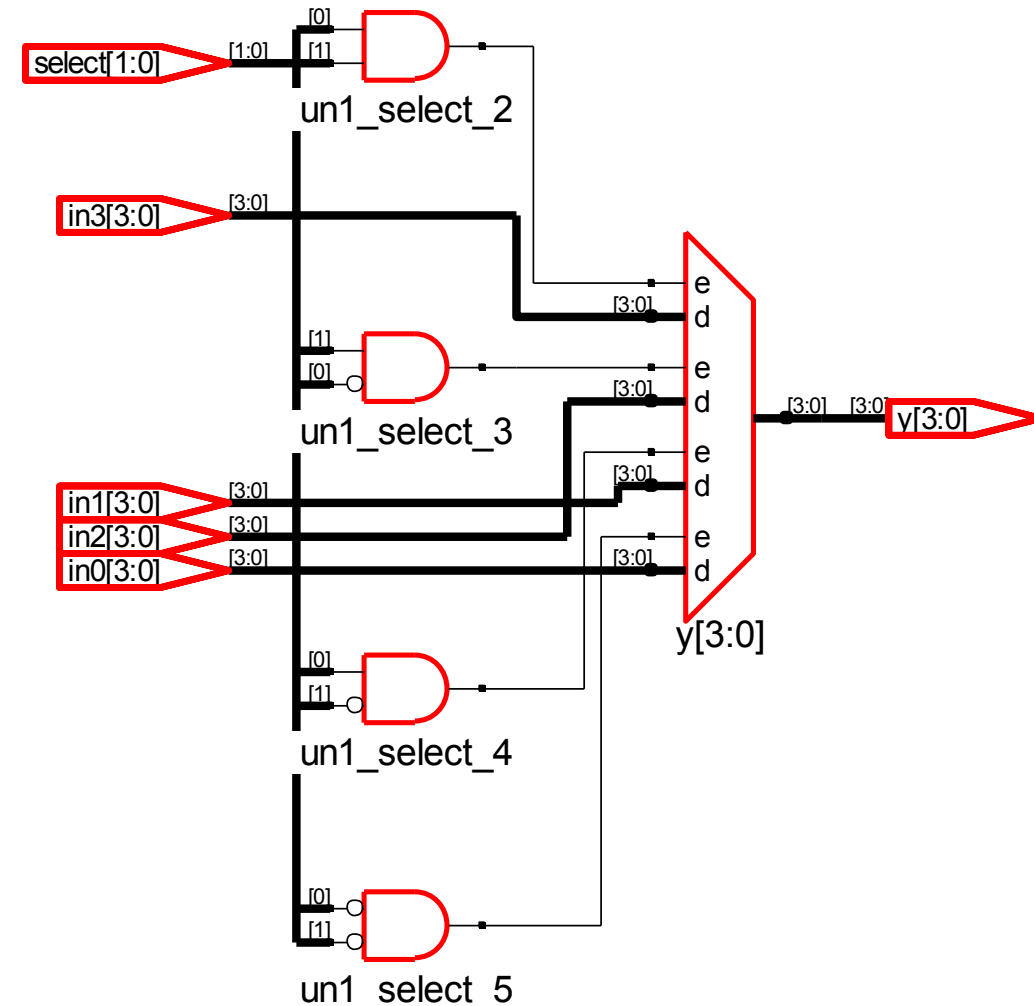
# Behavioral Style: Example #4"


- $n$ -bit 4-to-1 multiplexer with enable:  
An alternative using case

```
// an N-bit 4-to-1 multiplexer using case
parameter N = 8;
input [1:0] select;
input [N-1:0] in3, in2, in1, in0;
output reg [N-1:0] y;
always @(*)
    case (select)
        2'b11: y = in3 ;
        2'b10: y = in2 ;
        2'b01: y = in1 ;
        2'b00: y = in0 ;
        default: y = N{1'b0};
    endcase
```



# Behavioral Style: Example #5


- 1-to-4 demultiplexer (DEMUX)

 

(a) Logic symbol

$E$	$S_1$	$S_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
1	$\phi$	$\phi$	0	0	0	0
0	0	0	0	0	0	$D$
0	0	1	0	0	$D$	0
0	1	0	0	$D$	0	0
0	1	1	$D$	0	0	0

(b) Function table

 


(c) Logic circuit

# Behavioral Style: Example #5
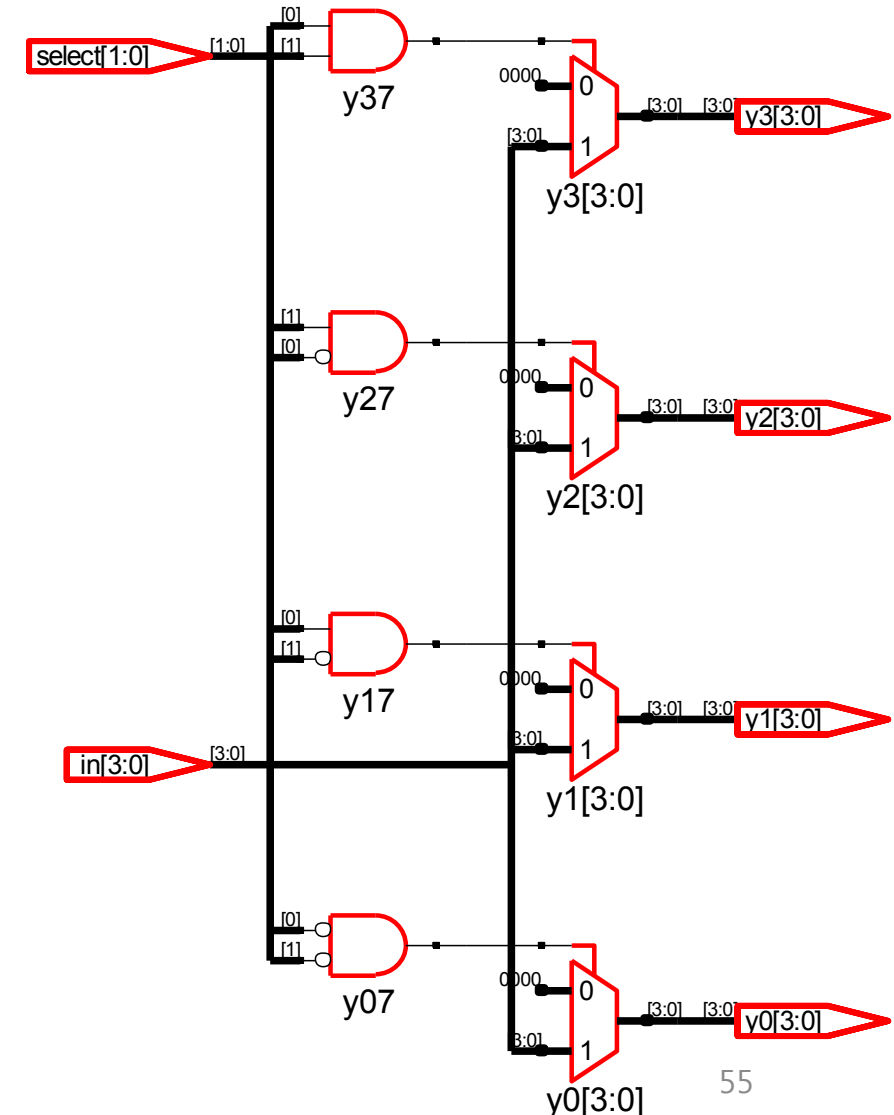
## ■ 1-to-4 DEMUX: if ... else

```
// an N-bit 1-to-4 demultiplexer using if ...  
else structure  
parameter N = 4; // default width  
input      [1:0] select;  
input      [N-1:0] in;  
output reg [N-1:0] y3, y2, y1, y0;  
  
always @(select or in) begin  
    if (select == 3) y3 = in; else y3 = {N{1'b0}};  
    if (select == 2) y2 = in; else y2 = {N{1'b0}};  
    if (select == 1) y1 = in; else y1 = {N{1'b0}};  
    if (select == 0) y0 = in; else y0 = {N{1'b0}};  
end
```



# Behavioral Style: Example #5

```
// an N-bit 1-to-4 demultiplexer with enable control  
parameter N = 4; // Default width
```

```
...
```

```
output reg [N-1:0] y3, y2, y1, y0;  
always @(select or in or enable) begin
```

```
    if (enable) begin
```

```
        if (select == 3) y3 = in; else y3 = {N{1'b0}};
```

```
        if (select == 2) y2 = in; else y2 = {N{1'b0}};
```

```
        if (select == 1) y1 = in; else y1 = {N{1'b0}};
```

```
        if (select == 0) y0 = in; else y0 = {N{1'b0}};
```

```
    end
```

```
    else begin
```


```
        y3 = {N{1'b0}};
```

```
        y2 = {N{1'b0}};
```

```
        y1 = {N{1'b0}};
```

```
        y0 = {N{1'b0}}; end
```

```
end
```

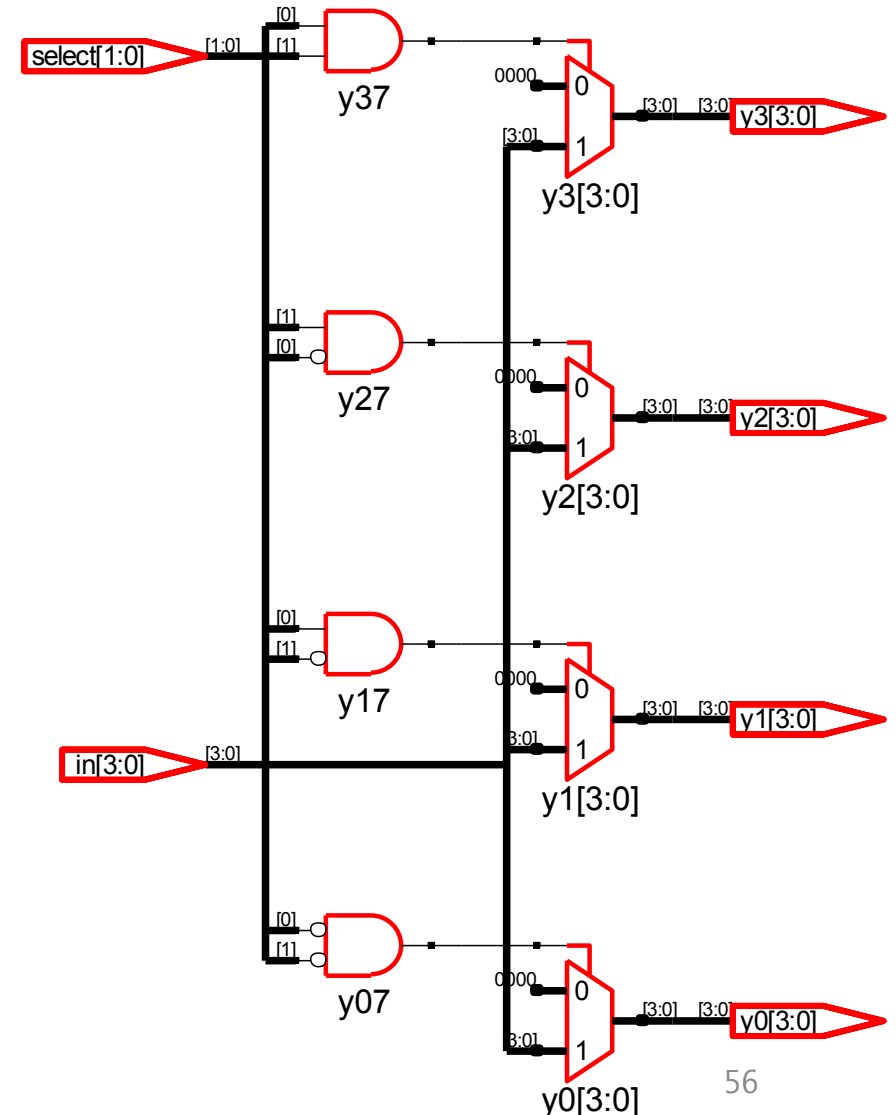




# Behavioral Style: Example #6

- Simple comparator


```
// an N-bit comparator module example
parameter N = 4;    // default size
input  [N-1:0] a, b;
output cgt, clt, ceq;
```
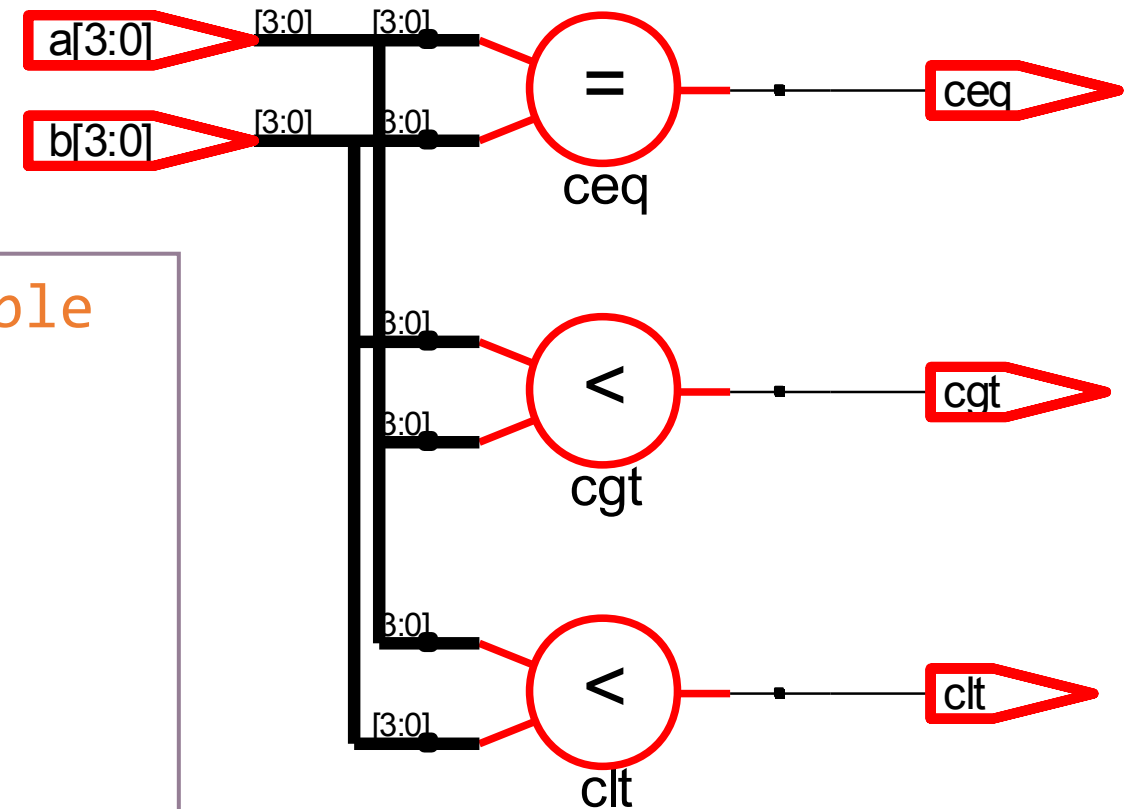
```
assign cgt = _____;
assign clt = _____;
assign ceq = _____;
```



# Behavioral Style: Example #6'

- Cascadable comparator

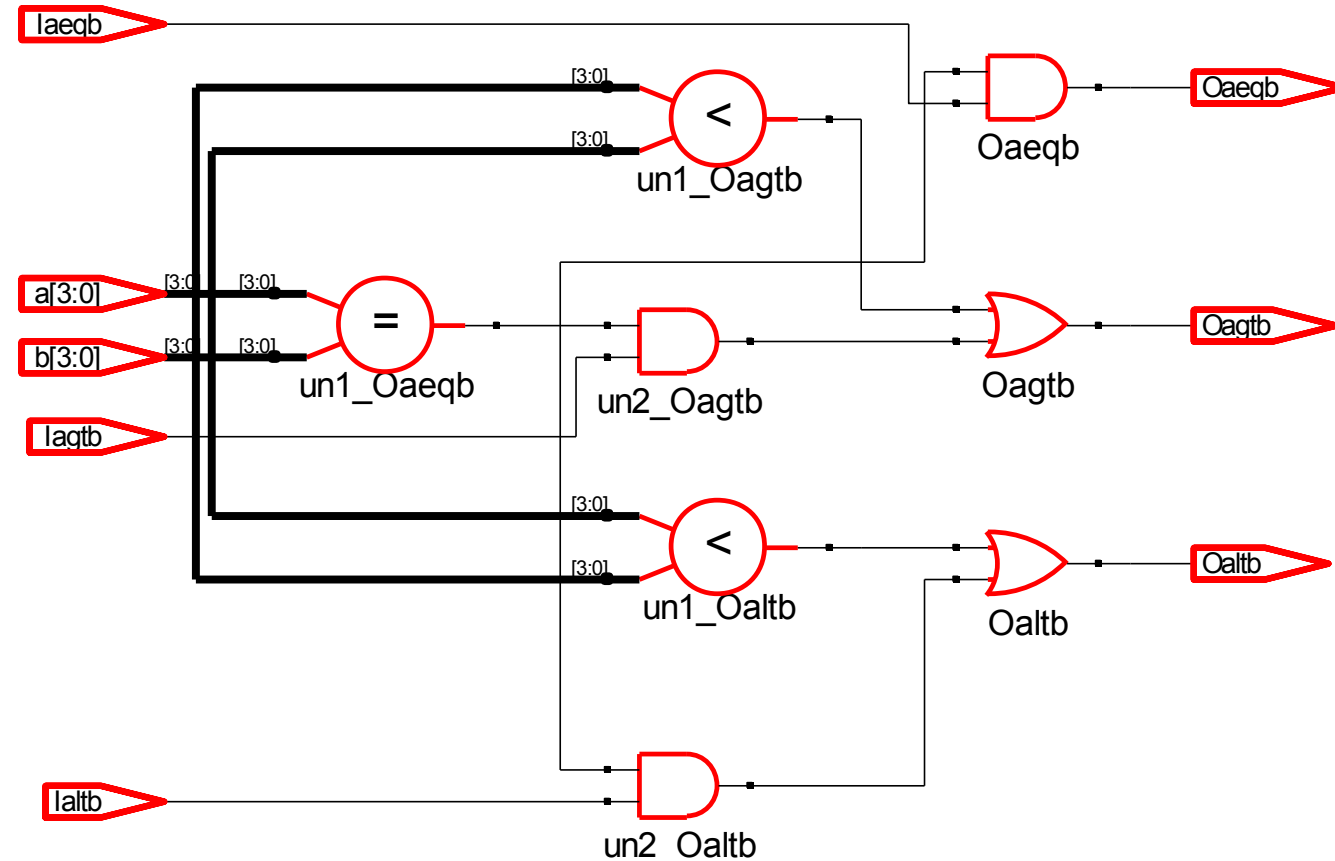

# Behavioral Style: Example #6'

- Cascadable comparator

```
parameter N = 4;
// I/O port declarations
input      Iagtb, Iaeqb, Ialtb;
input      [N-1:0] a, b;
output     Oagtb, Oaeqb, Oaltb;

// dataflow modeling using relation operators
assign Oaeqb = _____; // =
assign Oagtb = _____; // >
assign Oaltb = _____; // <
```

# Module Modeling Styles


---

- Structural style
  - Gate level
- Dataflow style
- Behavioral or algorithmic style
- **Mixed style**

# Mixed Style

## ■ Example: Full adder

```
module full_adder_mixed_style(x, y, c_in, s, c_out); // I/O port declarations
input x, y, c_in;
output s, c_out;
reg c_out;
wire s1, c1, c2;
// structural modeling of HA 1
xor xor_ha1 (s1, x, y);
and and_ha1(c1, x, y);
// dataflow modeling of HA 2
assign s = c_in ^ s1;
assign c2 = c_in & s1;
// behavioral modeling of output OR gate
always @(c1, c2) // always @(*)
c_out = c1 | c2;
endmodule
```

 

# Mixed Style

---

- Mixed style modeling
  - Using two or more different styles of description
  - Common mixed style: Register Transfer-Level (RTL)
    - RTL = synthesizable behavioral + dataflow constructs
    - Synthesized into gate-level design for chip design or FPGA emulation


# Outline

---


- Module
- Generate statements
- Module modeling styles
- **Simulation**
 
# Simulation

- Basic simulation constructs
  - Stimulus Block = Test Bench



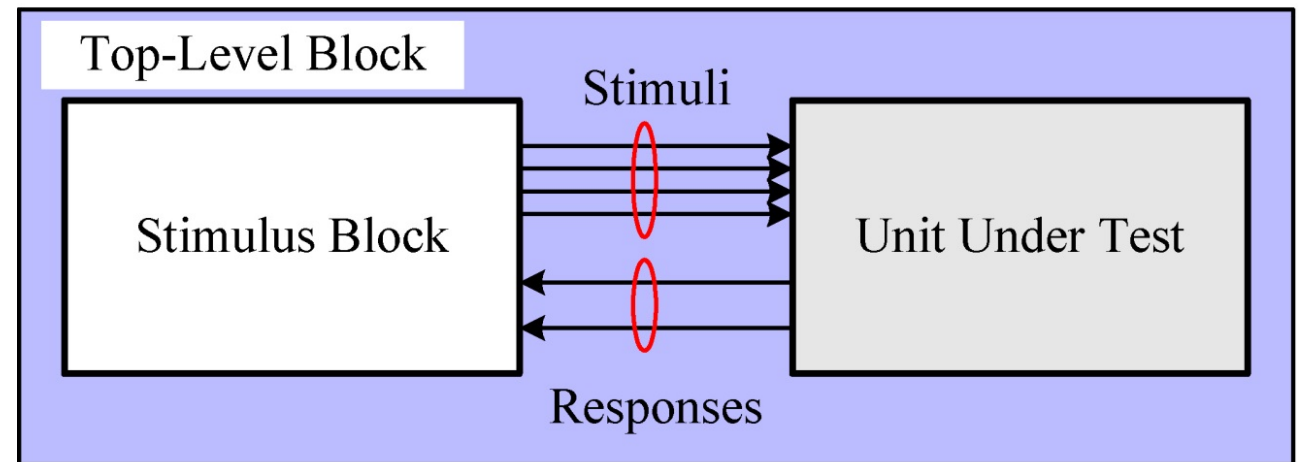(a) Stimulus block at the top-level module.



(b) Stimulus block is considered as a separate module.



# Simulation: Example

---

- Unit Under Test (UUT): 4-bit adder

```
// Gate-level description of 4-bit adder
module four_bit_adder (x, y, c_in, sum, c_out);
input  [3:0] x, y;
input  c_in;
output [3:0] sum;
output c_out;
wire    C1,C2,C3; // Intermediate carries
// -- four_bit adder body--
// Instantiate the full adder
    full_adder fa_1 (x[0],y[0],c_in,sum[0],C1);
    full_adder fa_2 (x[1],y[1],C1,sum[1],C2);
    full_adder fa_3 (x[2],y[2],C2,sum[2],C3);
    full_adder fa_4 (x[3],y[3],C3,sum[3],c_out);
endmodule
```

# Simulation: Example

---

## ■ Test bench of 4-bit adder

```
`timescale 1ns / 100ps // time unit is in ns.
module four_bit_adder_tb;
// internal signals declarations:
reg [3:0] x;
reg [3:0] y;
reg c_in;
wire [3:0] sum;
wire c_out;
// Unit Under Test port map
four_bit_adder UUT (.x(x), .y(y), .c_in(c_in), .sum(sum), .c_out(c_out));
reg [7:0] i;

initial
    for (i = 0; i <= 255; i = i + 1) begin
        x[3:0] = i[7:4]; y[3:0] = i[3:0]; c_in = 1'b0;
        #20 ;    end
```

# Simulation: Example

## ■ Simulation results

[illegible]