

# Logic Design with Verilog III: Sequential Logic and FSM

Jae W. Lee (jaewlee@snu.ac.kr)

Department of Computer Science and Engineering  
Seoul National University

Slide credits: Prof. Ming-Bo Lin (Digital System Designs and Practices Using Verilog HDL and FPGAs)

# Objectives

---

After completing this lecture, you will be able to:




- Describe how to model **asynchronous and synchronous *D*-type flip-flops**
- Describe how to model registers (**data register, register file, and synchronous RAM**)
- Describe how to model **shift registers**
- Describe how to model **counters** (ripple/synchronous counters and modulo  $r$  counters)
- Describe how to model **sequence generators**

# Outline

---

- Flip-Flops
- Memory elements
- Shift registers
- Counters
- Finite-state machine (FSM)
   
# Comparison of Latches and Flip-Flops (FFs)




Again, in FFs, the data value only at the rising edge (or falling edge) is critical (see blue dots). Meanwhile, most latches are sensitive to D value changes as long as the clock is high. Typically, the clock input of a FF is depicted by a triangle.
 
# D-Type Flip-Flops

```
// D-type flip-flop
module DFF (clk, d, q);
input      clk, d;
output reg q;


    always @(posedge clk)    q <= d;
endmodule
```


 
# Asynchronous Reset D-Type Flip-Flops

```
// asynchronous reset D-type flip-flop
module DFF_async_reset (clk, reset_n, d, q);
input      clk, reset_n, d;
output reg q;


always @(posedge clk or negedge reset_n)
    if (!reset_n) q <= 0;
    else        q <= d;
endmodule
```


 
# Synchronous Reset D-Type Flip-Flops

```
// synchronous reset D-type flip-flop
module DFF_sync_reset (clk, reset_n, d, q);
input      clk, reset_n, d;
output reg q;

always @(posedge clk)
    if (!reset_n) q <= 0;
    else         q <= d;
endmodule
```



# Outline

---

- Flip-Flops
- **Memory elements**
- Shift registers
- Counters
- Finite-state machine (FSM)




# Memory Elements: Types

---

- Data registers
- Register files
- Synchronous RAMs


# Memory Elements: Data Registers

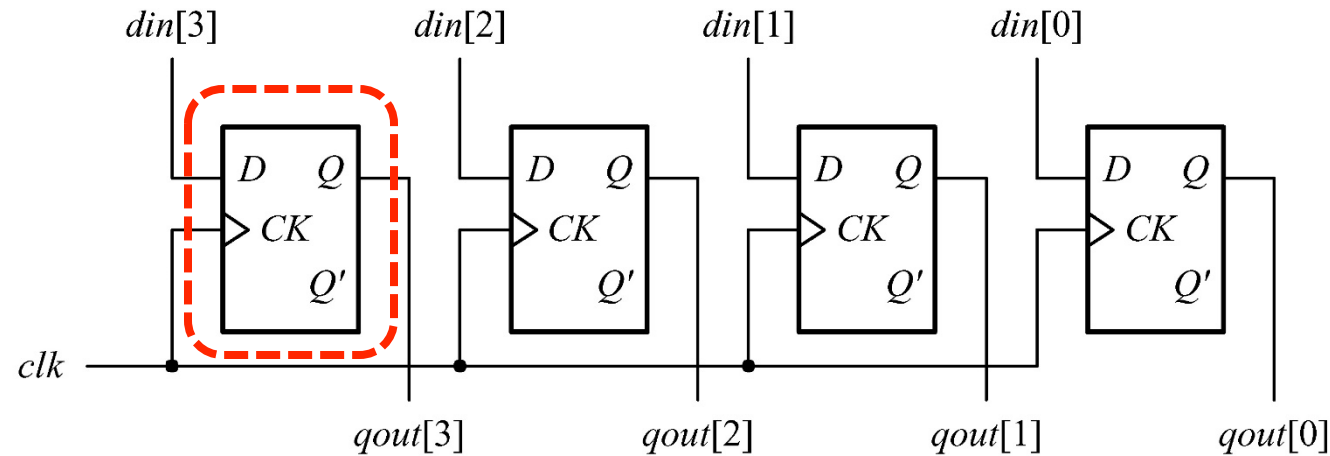

```
// D-type flip-flop
module DFF (clk, din, qout);
input      clk, din;
output reg qout;

    always @(posedge clk)    qout <= din;
endmodule
```

# Memory Elements: Data Registers

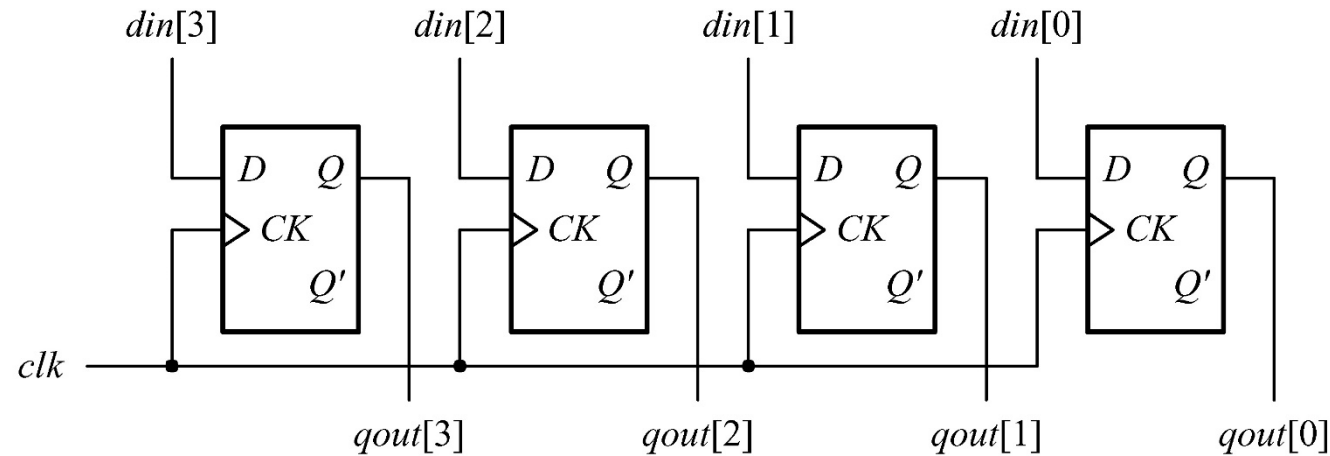

// an n-bit data register

```
module register(clk, din, qout);
```

```
parameter          N = 4;    // number of bits
```

```
...
```

```
input      [N-1:0]    din;
```

```
output reg [N-1:0]    qout;
```

```
    always @(posedge clk) qout <= din;
```

```
endmodule
```

# Memory Elements: Data Registers

---

```
// an N-bit data register with asynchronous reset
module register_reset (clk, reset_n, din, qout);
parameter                N = 4;    // number of bits
...
input                    [N-1:0]    din;
output reg               [N-1:0]    qout;
always @(posedge clk or negedge reset_n)
    if (!reset_n)    qout <= {N{1'b0}};
    else            qout <= din;
endmodule
```

# Memory Elements: Data Registers

---


```
// an N-bit data register with synchronous load and asynchronous reset
module register_load_reset (clk, load, reset_n, din, qout);
parameter                N = 4;    // number of bits
input                    clk, load, reset_n;
input [N-1:0]            din;
output reg [N-1:0]        qout;

always @(posedge clk or negedge reset_n)
    if (!reset_n)    qout <= {N{1'b0}};
    else if (load)    qout <= din;
endmodule
```

# Memory Elements: Register File

 - Example: A register file having 16 8-bit words


```
// an N-word register file with one-write and two-read ports
parameter          M = 4;    // number of address bits
parameter          N = 16;   // number of words, N = 2^M
parameter          W = 8;    // number of bits in a word
input              clk, wr_enable;
input              [W-1:0] din;
output             [W-1:0] douta, doutb;
input              [M-1:0] rd_addra, rd_addrb, wr_addr;
reg                [W-1:0] reg_file [N-1:0];
...
assign douta = reg_file[rd_addra];
assign doutb = reg_file[rd_addrb];
always @(posedge clk)
    if (wr_enable) reg_file[wr_addr] <= din;
```



# Memory Elements: Register File

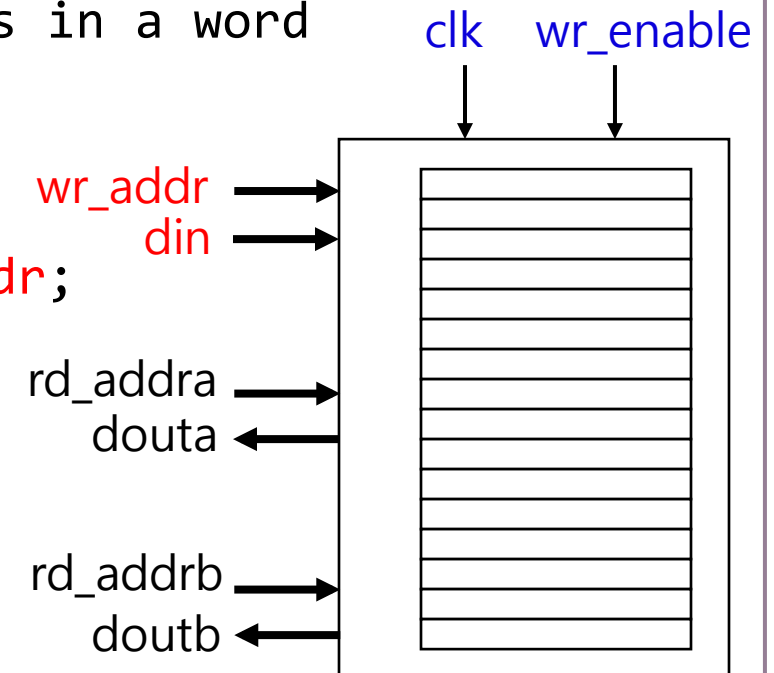- Example: A register file having 16 8-bit words

```
// an N-word register file with one-write and two-read ports
parameter          M = 4;    // number of address bits
parameter          N = 16;   // number of words, N = 2^M
parameter          W = 8;    // number of bits in a word
input              clk, wr_enable;
input              [W-1:0] din;
output             [W-1:0] douta, doutb;
input              [M-1:0] rd_addra, rd_addrb, wr_addr;
reg                [W-1:0] reg_file [N-1:0];
...
assign douta = reg_file[rd_addra];
assign doutb = reg_file[rd_addrb];
always @(posedge clk)
    if (wr_enable) reg_file[wr_addr] <= din;
```



# Memory Elements: Register File

- Example: A register file having 16 8-bit words

```
// an N-word register file with one-write and two-read ports with read_en
parameter          M = 4;    // number of address bits
parameter          N = 16;   // number of words, N = 2^M
parameter          W = 8;    // number of bits in a word
input              clk, wr_enable, read_en_a, read_en_b;
input              [W-1:0] din;
output             [W-1:0] douta, doutb;
input              [M-1:0] rd_addra, rd_addrb, wr_addr;
reg                [W-1:0] reg_file [N-1:0];
...
assign douta = read_en_a ? _____;
assign doutb = read_en_b ? _____;
always @(posedge clk)
    if (wr_enable) reg_file[wr_addr] <= din;
```



# Memory Elements: Synchronous RAM

- RAM = Random Access Memory

```
// a synchronous RAM module example
```

```
parameter          N = 16;          // number of words
parameter          A = 4;          // number of address bits
parameter          W = 8;          // number of wordsize in bits
input              [A-1:0]          addr;
input              [W-1:0]          din;
input              cs, wr, clk;      //chip select, read-write control, and clock signals
output reg         [W-1:0]          dout;
reg                [W-1:0]          ram[N-1:0]; // declare an N * W memory array

always @(posedge clk)
    if (cs) begin
        if (wr)      ram[addr] <= din;
        else         dout <= ram[addr];
    end
end
```

# Outline

---


- Flip-Flops
- Memory elements
- **Shift registers**
- Counters
- Finite-state machine (FSM)

# Shift Registers


- Parallel/serial format conversion

- SISO (serial in serial out)
- SIPO (serial in parallel out)
- PISO (parallel in serial out)
- PIPO (parallel in parallel out)

- Example: SISO shift register

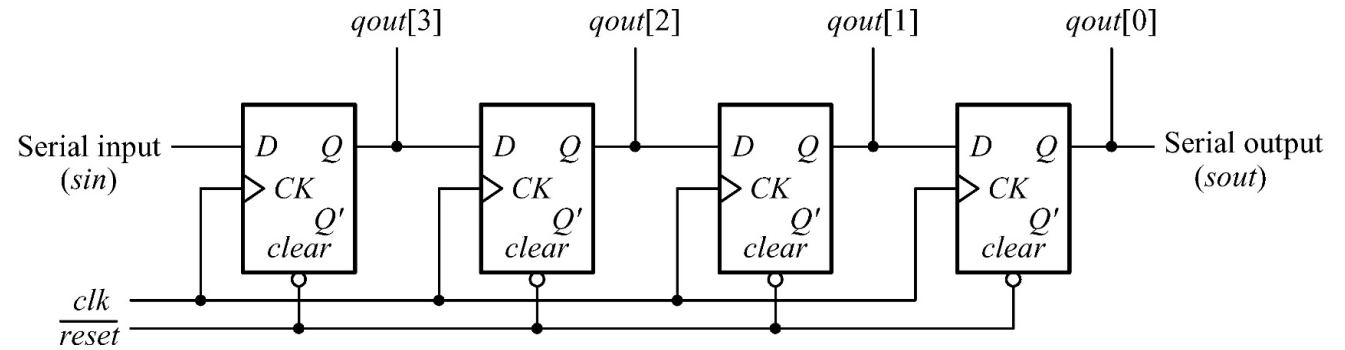

(a) Logic circuit

 


(b) Timing
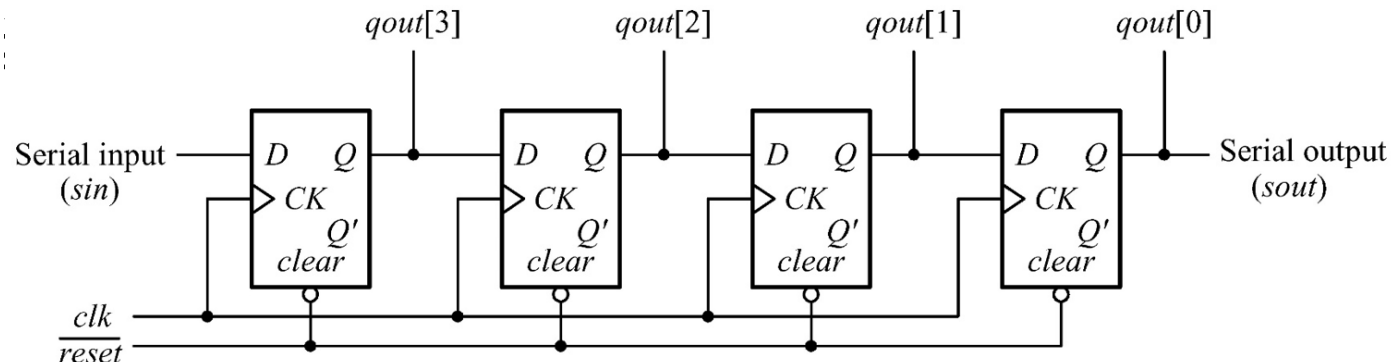
# Shift Registers: Verilog Code

```
// a shift register module example
module shift_register(clk, reset_n, sin, qout);
parameter                N = 4;    // number of bits
input                    clk, reset_n, sin;
output reg [N-1:0]      qout;

always @(posedge clk or negedge reset_n)
    if (!reset_n)    qout <= {N{1'b0}};
    else             qout <= {sin, qout[N-1:1]};
endmodule
```



# Shift Registers: With Parallel Load

---

```
// a shift register with parallel load module example
module shift_register_parallel_load (clk, load, reset_n, sin, din, qout);
parameter                                N = 8; // number of bits
input                                    clk, load, reset_n, sin;
input [N-1:0]                            din;
output reg [N-1:0]                        qout;


always @(posedge clk or negedge reset_n)
    if (!reset_n)    qout <= {N{1'b0}};
    else if (load)   qout <= din;
    else            qout <= {sin, qout[N-1:1]};
```

# Universal Shift Registers


---

- A universal shift register can carry out
  - SISO
  - SIPO
  - PISO
  - PIPO
- The register must have the following capabilities
  - Parallel load
  - Serial in and serial out
  - Shift left and shift right

# Universal Shift Registers

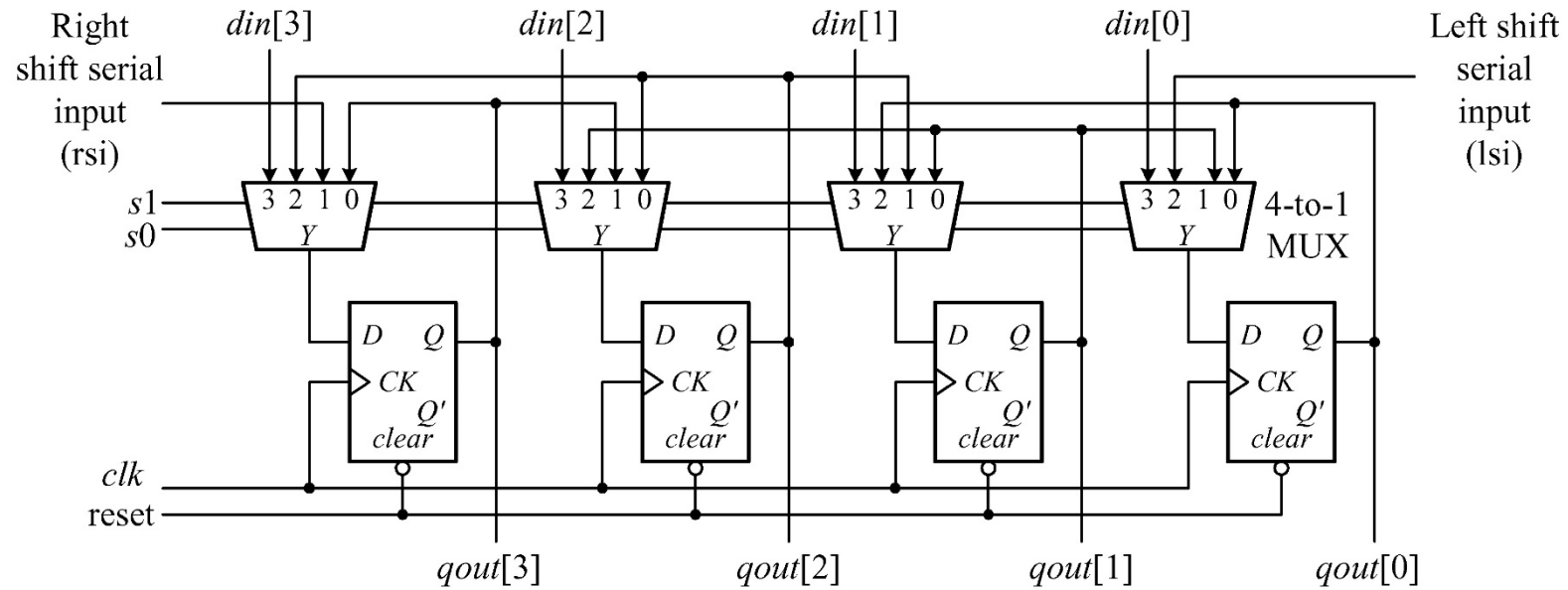

(a) Logic diagram

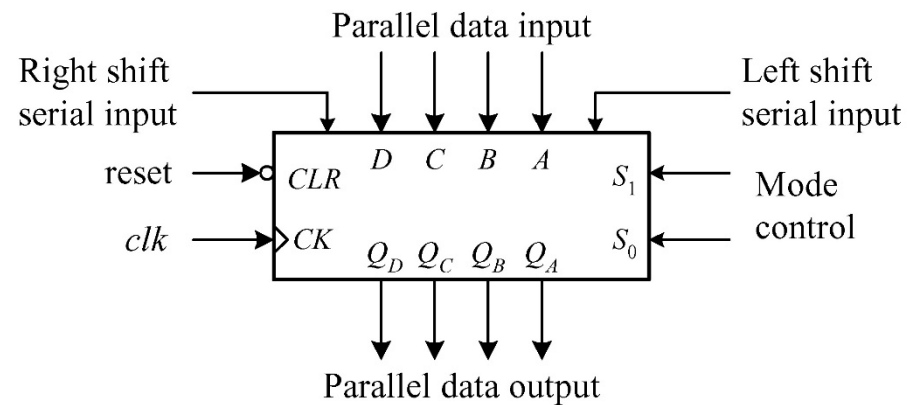

(b) Logic symbol

s1	s0	Function
0	0	No change
0	1	Right shift
1	0	Left shift
1	1	Load data

(c) Function table






# Outline

---



- Flip-Flops
- Memory elements
- Shift registers
- **Counters**
- Finite-state machine (FSM)

# Counters: Binary Ripple Counters

 
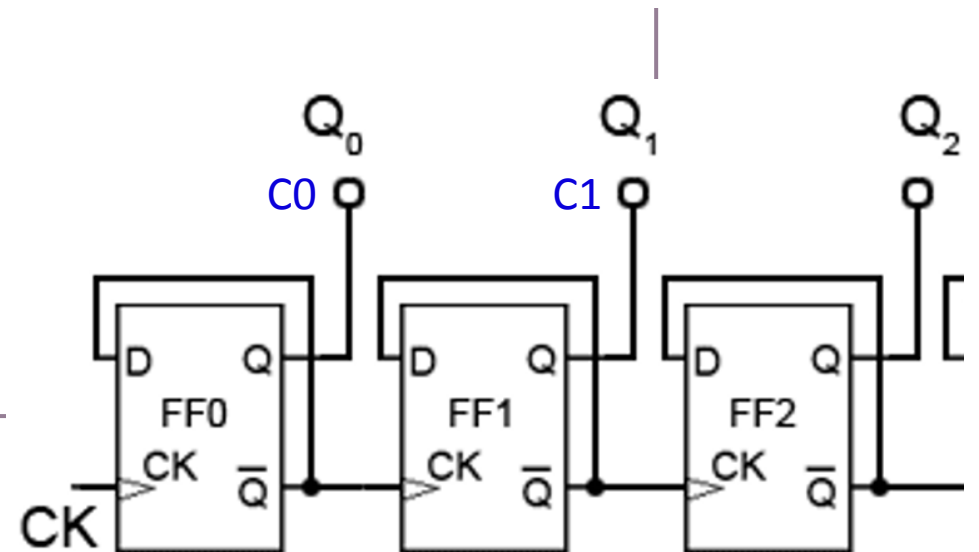 
# Counters: Binary Ripple Counters

```
// a 3-bit ripple counter module example
module ripple_counter(clk, qout);
input          clk;
output reg [2:0] qout;
wire          c0, c1;
// the body of the 3-bit ripple counter
assign c0 = qout[0], c1 = qout[1];
always @(negedge clk)
    qout[0] <= ~qout[0];
always @(negedge c0)
    qout[1] <= ~qout[1];
always @(negedge c1)
    qout[2] <= ~qout[2];
endmodule
```



# Counters: Binary Ripple Counters

---

```
// a 3-bit ripple counter with enable control
module ripple_counter_enable(clk, enable, reset_n, qout);
input          clk, enable, reset_n;
output reg     [2:0] qout;
wire          c0, c1;
assign c0 = qout[0], c1 = qout[1];
always @(posedge clk or negedge reset_n)
    if (!reset_n)        qout[0] <= 1'b0;
    else if (enable)      qout[0] <= ~qout[0];
always @(posedge c0 or negedge reset_n)
    if (!reset_n)        qout[1] <= 1'b0;
    else if (enable)      qout[1] <= ~qout[1];
always @(posedge c1 or negedge reset_n)
    if (!reset_n)        qout[2] <= 1'b0;
    else if (enable)      qout[2] <= ~qout[2];
```

# Counters: Binary Ripple Counters

---

```
// an N-bit ripple counter using generate blocks
parameter                N = 4; // define the size of counter
...
output reg    [N-1:0]    qout;
genvar        i;

generate for (i = 0; i < N; i = i + 1) begin: ripple_counter
    if (i == 0) // specify LSB
        always @(negedge clk or negedge reset_n)
            if (!reset_n) qout[0] <= 1'b0;    else qout[0] <= ~qout[0];
    else // specify the rest bits
        always @(negedge qout[i-1] or negedge reset_n)
            if (!reset_n) qout[i] <= 1'b0;    else qout[i] <= ~qout[i];
end endgenerate
```

# Counters: Binary Up/Down Counters

---

```
module updn_bincounter (clk, reset, eup, edn, qout, cout, bout);
parameter              N = 4;
input                  clk, reset, eup, edn;
output reg [N-1:0]     qout;
output                cout, bout;

always @(posedge clk)
    if (reset)          qout <= {N{1'b0}}; // synchronous reset
    else if (eup)       qout <= qout + 1;
    else if (edn)       qout <= qout - 1;
assign #1 cout = (&qout)& eup;              // generate carry out
assign #1 bout = (~|qout)& edn;            // generate borrow out
```

# Outline

---

- Flip-Flops
- Memory elements
- Shift registers
- Counters
- **Finite-state machine (FSM)**
  - **Definition**
  - **Modeling styles**
  - **FSM examples**

# FSM: Definition

---

- A **finite-state machine (FSM)** is

$$M = (I, O, S, \delta, \lambda)$$



where  $I$ ,  $O$ , and  $S$  are finite, nonempty sets of inputs, outputs, and states

- State transition function  
 $\delta: I \times S \rightarrow S$
- Output function  
 $\lambda: I \times S \rightarrow O$  (Mealy machine)  
 $\lambda: S \rightarrow O$  (Moore machine)



# FSM: Definition

- Types of FSM: Moore and Mealy

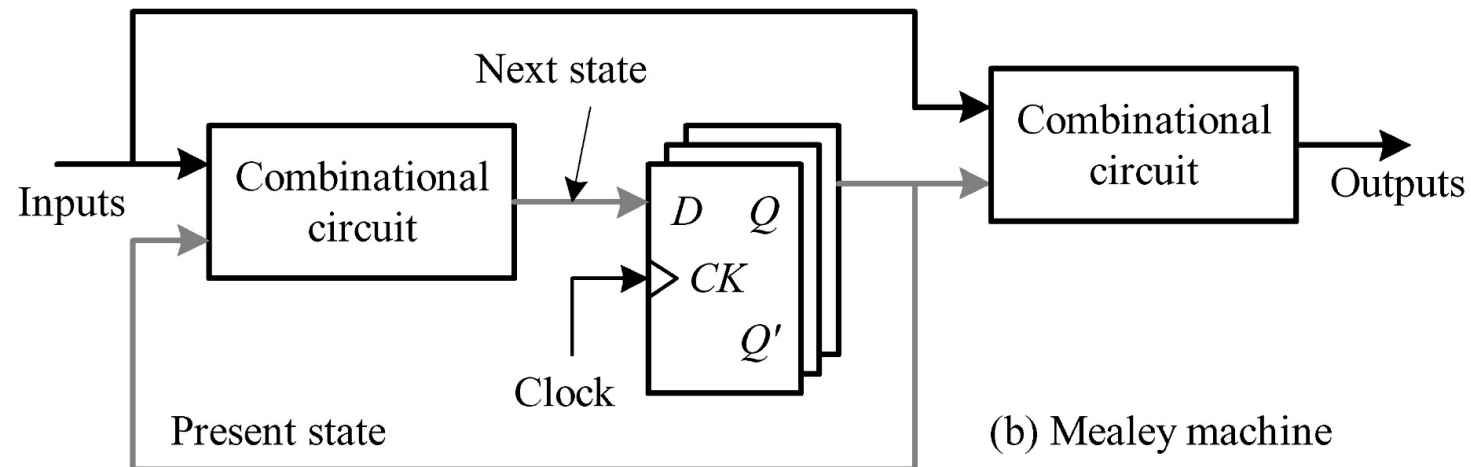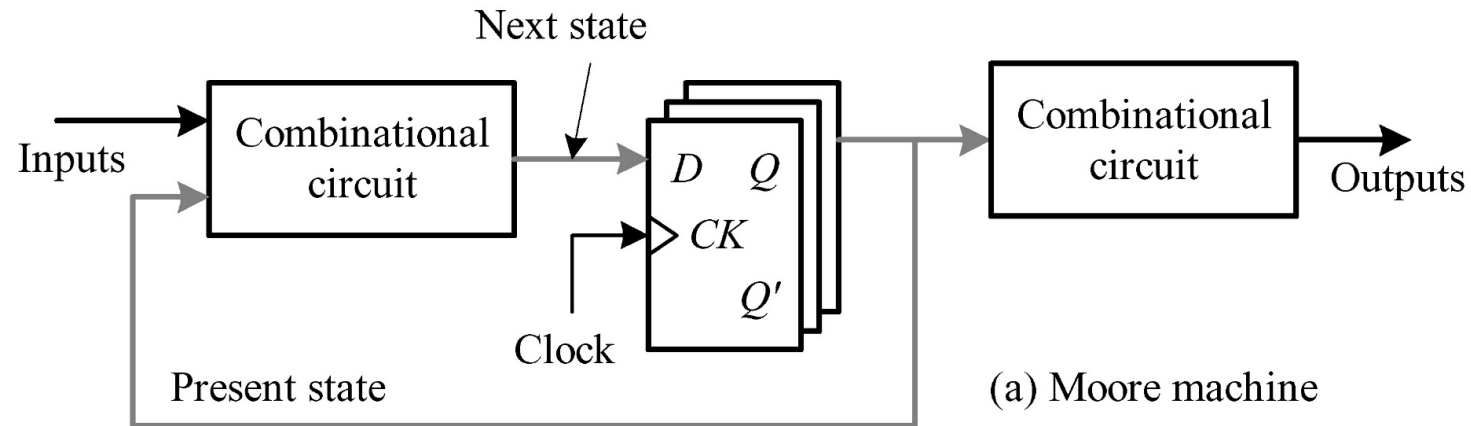


# FSM: Definition
 
## ■ Example FSM

```
module sum_3data_explicit(clk, data, total);
parameter                N = 8;
input                    clk, reset;
input [N-1:0]            data;
output reg [N-1:0]        total;
reg [2:0]                 state;
parameter                A = 3'b001,
                        B = 3'b010,
                        C = 3'b100;

always @(posedge clk and posedge reset)
    if (reset) state <= A;
    else
        case (state)
            A: begin total <= data; state <= B; end
            B: begin total <= total + data; state <= C; end
            C: begin total <= total + data; state <= A; end
        endcase
endmodule
```



data	1	2	3	4	5	6	7	8	...
total	1	3	6	4	9	15	7	15	...

# FSM: Modeling Styles – Moore Machine

- **3 parts of an FSM (Moore Machine)**

- part 1: initialize and update the state register


```
always @(posedge clk or negedge reset_n)
    if (!reset_n) present_state <= A;
    else present_state <= next_state;
```

- part 2: determine next state

```
always@(present_state or x)
    case (present_state) ...
        next_state <= ; or
    assignment statements // always is common
```

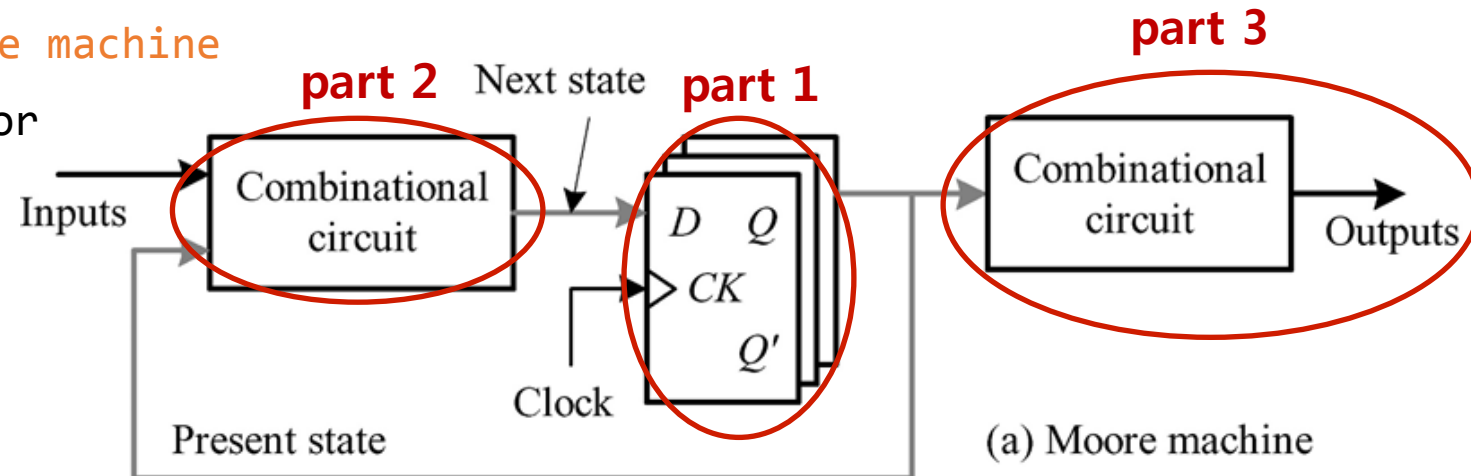- part 3: determine output

```
always @(present_state) // Moore machine
    case (present_state) ... or
    assignment statement
```



# FSM: Modeling Styles – Mealy Machine

- **3 parts of an FSM (Mealy Machine)**

- part 1: initialize and update the state register


```
always @(posedge clk or negedge reset_n)
    if (!reset_n) present_state <= A;
    else present_state <= next_state;
```

- part 2: determine next state

```
always@(present_state or x)
    case (present_state) ...
        next_state <= ; or
    assignment statements // always is common
```

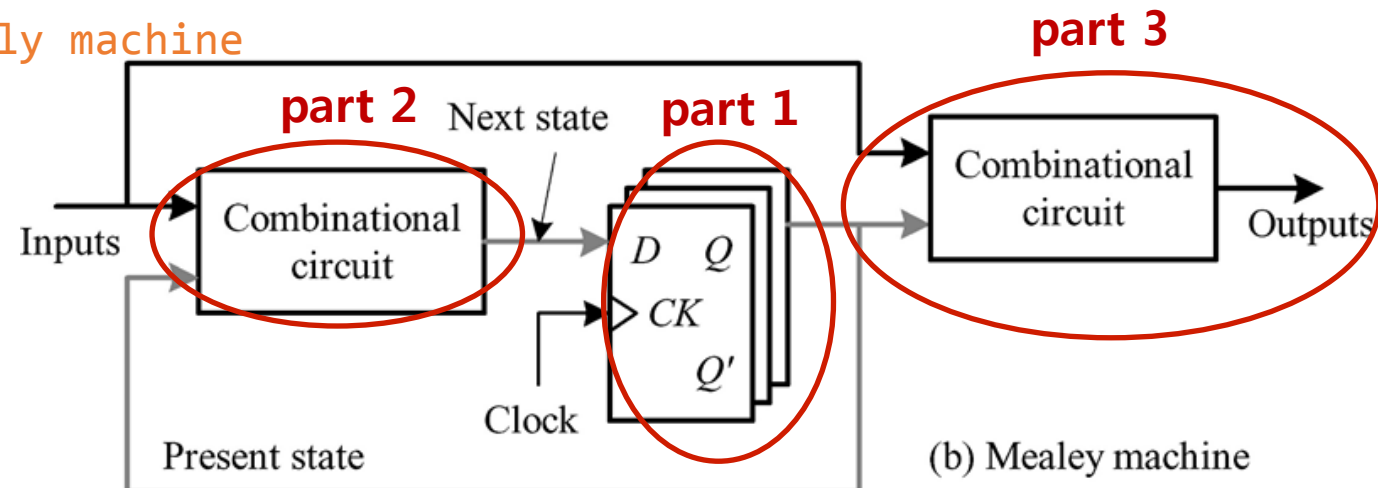
- part 3: determine output

```
always @(present_state or x) // Mealy machine
    case (present_state) ... or
    assignment statement
```



 
# FSM Example #1: 0101 Sequence Detector


- Design an FSM to detect the pattern **0101** in the input sequence  $x$ 
  - Assume that overlapping pattern is allowed



(a) Block diagram

 

(b) State diagram

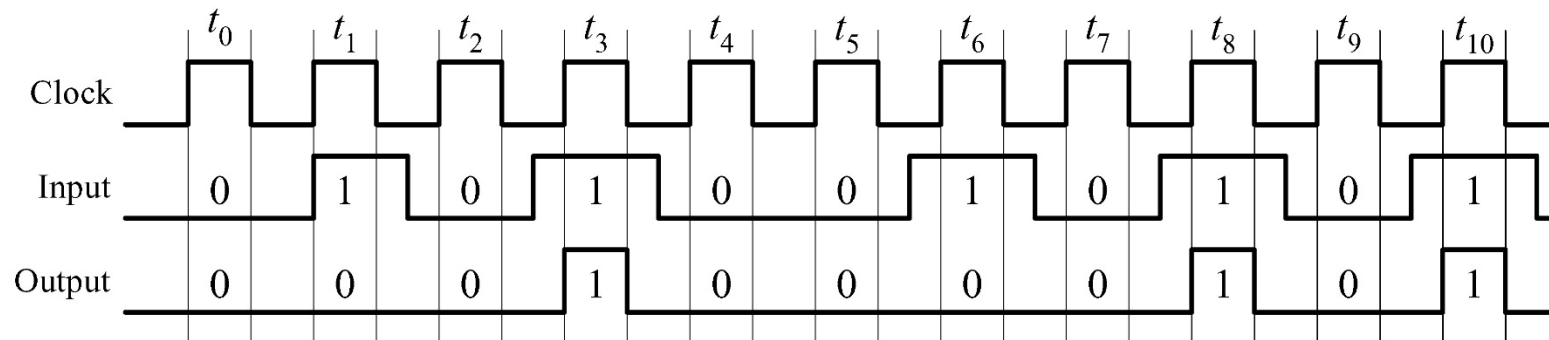



(c) Timing chart

# FSM Example #1: 0101 Sequence Detector

```

module sequence_detector_mealy (clk, reset_n, x, z);
    input          clk, reset_n, x; output reg z;
    reg            [1:0]  present_state, next_state; // present state and next state
    parameter      A = 2'b00, B = 2'b01, C = 2'b10, D = 2'b11;
    // part 1: initialize to state A and update present state register
    always @(posedge clk or negedge reset_n)
        if(!reset_n) present_state <= A; else present_state <= next_state;
    // part 2: determine next state
    always @(present_state or x)
        case(present_state)
            A: if (x) next_state = A; else next_state = B;
            B: if (x) next_state = C; else next_state = B;
            C: if (x) next_state = A; else next_state = D;
            D: if (x) next_state = C; else next_state = B;
        endcase
    // part 3: evaluate output z
    always @(present_state or x) // mealey machine
        case (present_state)
            A: if (x) z = 1'b0; else z = 1'b0;
            B: if (x) z = 1'b0; else z = 1'b0;
            C: if (x) z = 1'b0; else z = 1'b0;
            D: if (x) z = 1'b1; else z = 1'b0;
        endcase
endmodule



```

 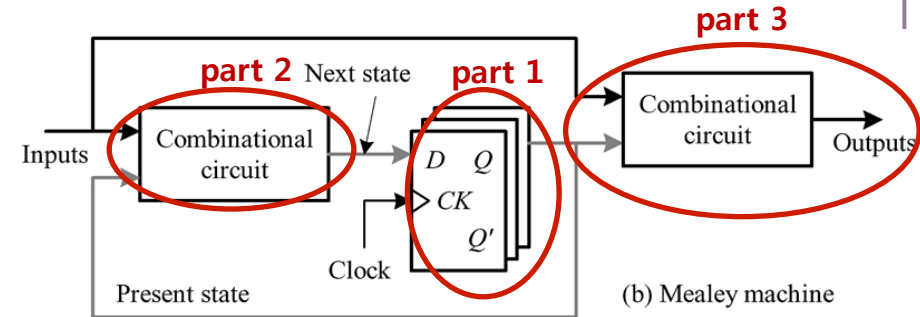

(b) State diagram
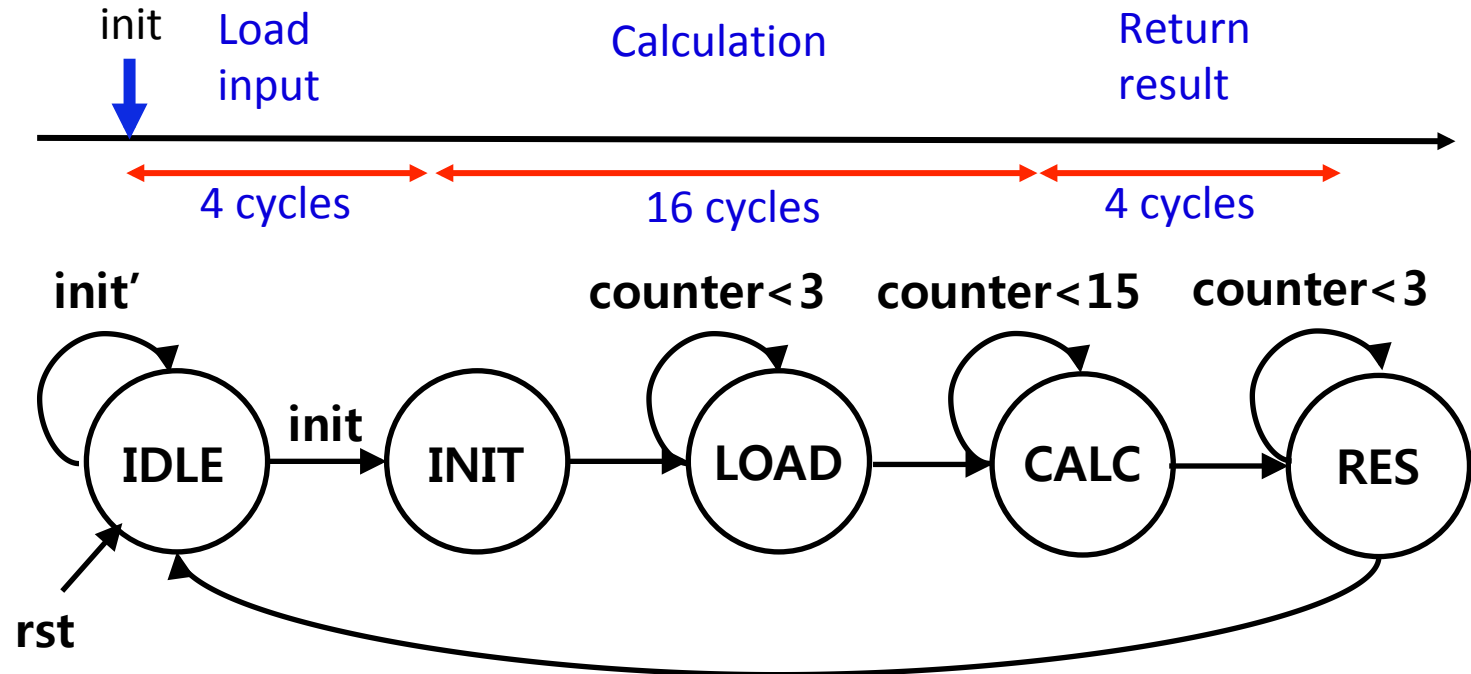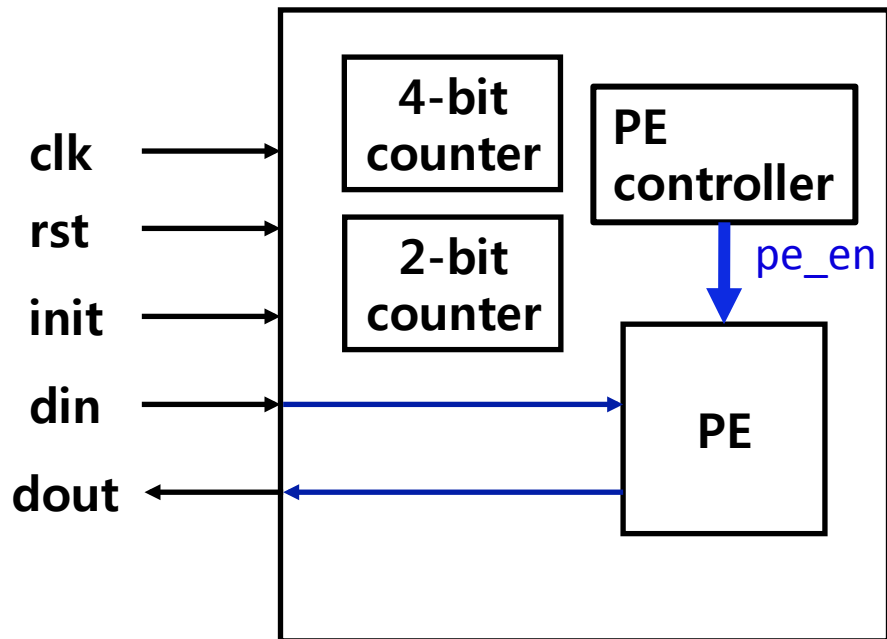
# FSM Example #2: Simple PE Controller

- Simple PE (Processing Element) controller
  - IDLE**: PE waits for input data.
  - INIT**: When *init* is changed into 1. PE controller starts to get data from outside (*din*). Internal signal, 'pe\_en', is changed into 1.
  - LOAD**: PE controller gets 4 data entries from outside (*din*) and gives it to PE for 4 cycles.
  - CALC**: PE computes output data for 16 cycles.
  - RES**: PE controller gets 4 data entries (result) from PE and gives it to outside (*dout*) for 4 cycles. State is turned into IDLE and 'pe\_en' is changed into 0 when it finishes operation



# FSM Example #2: Simple PE Controller

```
module pe_controller (clk, rst, init, din, dout);
    input          clk, rst, init;
    input [31:0]    din;
    output [31:0]   dout;
    reg            [1:0] present_state, next_state; // present state and next state
    reg            [3:0] count15; // register for counter
    reg            [1:0] count3;
    reg            counter_rst15;
    reg            counter_rst3;
    reg            pe_en; // enable for PE
    parameter      IDLE = 3'd0, INIT = 3'd1, LOAD = 3'd2, CALC = 3'd3, RES = 3'd4;

// PE
    PE my_pe (
        .clk(clk),
        .rst(rst),
        .en(pe_en),
        .din(din),
        .dout(dout)
    );

// counter
    always @(posedge clk or posedge counter_rst15)
        if(counter_rst15) count15 <= 0;
        else count15 <= count15+1;
    always @(posedge clk or posedge counter_rst3)
        if(counter_rst3) count3 <= 0;
        else count3 <= count3+1;
```



# FSM Example #2: Simple PE Controller

```
// part 1: initialize to state IDLE and update present state register
always @(posedge clk or posedge rst)
    if(rst) present_state <= IDLE; else present_state <= next_state;
// part 2: determine next state
always @(*)
    case(present_state)
        IDLE: if(init) next_state = INIT; else next_state = present_state;
        INIT: next_state = LOAD;
        LOAD: if(count3==3) next_state = CALC; else next_state = present_state;
        CALC: if(count15==15) next_state = RES; else next_state = present_state;
        RES: if(count3==3) next_state = IDLE; else next_state = present_state;
    endcase
// part 3: evaluate output (in this case internal registers)
always @(*)
    case (present_state)
        CALC: counter_rst15 = 0; // counter for CALC continues to tick
        default: counter_rst15 = 1;
    endcase
always @(*)
    case (present_state)
        LOAD: counter_rst3 = 0;
        RES: counter_rst3 = 0;
        default: counter_rst3 = 1;
    endcase
always @(*)
    case (present_state)
        IDLE: pe_en = 0;
        default: pe_en = 1;
    endcase
endmodule
```

