

1. Consider an electron moving in a circular path of radius R with constant speed v . What is the current due to this motion of electron?

2. A uniformly charged sphere of radius R centered on the origin of a rectangular coordinate system is rotated around the z -axis with a constant angular speed ω . The total charge of the sphere is Q .

(a) Find the current density within the sphere.


(b) What is the current through a circle of radius $R/2$ centered on $(R/2, 0, 0)$ that is fixed on the xz -plane?

(You don't have to use the rectangular coordinate system in your answer.)


3. Consider two coaxial conducting cylindrical shells. Their radii are R_1 and R_2 ($R_1 < R_2$) respectively. Their electric potential difference is V (constant). If the region between the shells is filled with a material with the resistivity ρ , what is the current density within the medium? Assume that the cylinders are very long.

(Hint : You can use Gauss' theorem to get the electric field within the medium.)

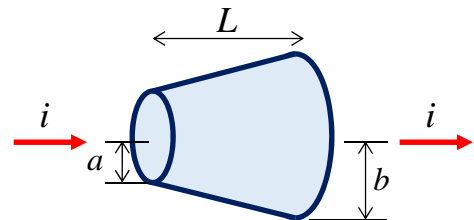
4. As shown in the figure, current is set up through a truncated right circular cone of resistivity ρ , left radius a , right radius b , and length L . Assume that the current density is uniform across any cross section taken perpendicular to the length. Find the resistance of the cone.



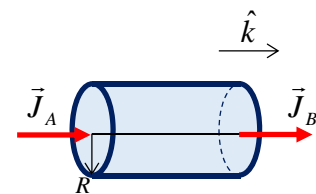
5. A cylindrical, unidentified device is set in a conducting loop as shown in the figure. The current densities are $\vec{J}_A = J_0(1 - (r/R)^2)\hat{k}$ and $\vec{J}_B = J_0(1 - r/R)\hat{k}$ (r is the distance from the central axis). Find the currents at the two circular surfaces and the time-rate of change of net free charge in the device.



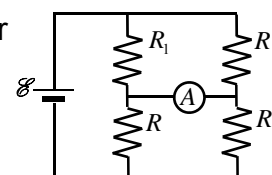
6. Consider a circuit shown in the figure. Assume that the ammeter resistance is zero, and the battery is ideal. What multiple of \mathcal{E}/R gives the current in the ammeter?



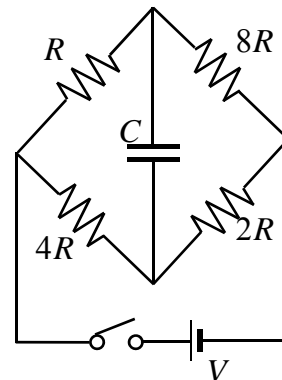
7. The switch in the following circuit is closed at $t = 0$. Find the voltage across the capacitor as a function of time.



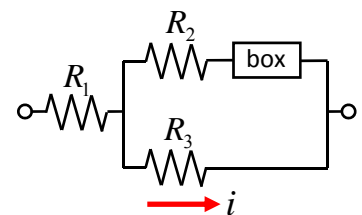8. A section of a circuit is shown in the figure. The potential difference between the two terminals is V . What is the energy transfer rate from the device represented by "box" to the circuit?



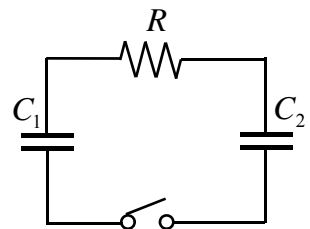9. Consider a circuit shown in the figure. Initially, capacitor 1 (capacitance C_1) is charged to Q and capacitor 2 (capacitance C_2) is uncharged. At $t = 0$, the circuit is closed.



- Find the current in the circuit.
- What is the energy dissipated as thermal energy until the steady state is reached?

10. Find the equivalent resistance between A and B . Assume that the all edges of the cubes have the same resistance R .

