

Chapter 27

Circuits

Lecture 10

Seon-Hee Seo

2016.09.28

27 Summary

Emf

- The **emf** (work per unit charge) of the device is

$$\mathcal{E} = \frac{dW}{dq} \quad (\text{definition of } \mathcal{E}). \quad \text{Eq. 27-1}$$

Single-Loop Circuits

- Current in a single-loop circuit:

$$i = \frac{\mathcal{E}}{R + r}, \quad \text{Eq. 27-4}$$

Power

- The rate P of energy transfer to the charge carriers is $P = iV$. **Eq. 27-14**

- The rate P_r at which energy is dissipated as thermal energy in the battery is $P_r = i^2 r$. **Eq. 27-16**

- The rate P_{emf} at which the chemical energy in the battery changes is

$$P_{\text{emf}} = i\mathcal{E}. \quad \text{Eq. 27-17}$$

Series Resistance

- When resistances are in series

$$R_{\text{eq}} = \sum_{j=1}^n R_j \quad \text{Eq. 27-7}$$

Parallel Resistance

- When resistances are in parallel

$$\frac{1}{R_{\text{eq}}} = \sum_{j=1}^n \frac{1}{R_j} \quad \text{Eq. 27-24}$$

RC Circuits

- The charge on the capacitor increases according to

$$q = C\mathcal{E}(1 - e^{-t/RC}) \quad \text{Eq. 27-33}$$

- During the charging, the current is

$$i = \frac{dq}{dt} = \left(\frac{\mathcal{E}}{R} \right) e^{-t/RC} \quad \text{Eq. 27-34}$$

- During the discharging, the current is

$$i = \frac{dq}{dt} = - \left(\frac{q_0}{RC} \right) e^{-t/RC} \quad \text{Eq. 27-40}$$

27-1 Single-Loop Circuits

Learning Objectives

27.01 Identify the action of an *emf* source in terms of the work it does.

27.02 For an ideal battery, apply the relationship between the *emf*, the current, and the power (rate of energy transfer).

27.03 Draw a schematic diagram for a single-loop circuit containing a battery and three resistors.

27.04 Apply the loop rule to write a loop equation that relates the potential differences of the circuit elements around a

(complete) loop.

27.05 Apply the resistance rule in crossing through a resistor.

27.06 Apply the *emf* rule in crossing through an *emf*.

27.07 Identify that resistors in series have the same current, which is the same value that their equivalent resistor has.

27.08 Calculate the equivalent of series resistors.

27.09 Identify that a potential applied to resistors wired in series is equal to the sum of the potentials across the individual resistors.

27-1 Single-Loop Circuits

Learning Objectives (Cont'd.)

27.10 Calculate the potential difference between any two points in a circuit.

27.11 Distinguish a real battery from an ideal battery and, in a circuit diagram, replace a real battery with an ideal battery and an explicitly shown resistance.

27.12 With a real battery in a circuit, calculate the potential difference between its terminals for current in the direction of the *emf* and in the opposite direction.

27.13 Identify what is meant by grounding a circuit, and draw a schematic diagram for such a connection.

27.14 Identify that grounding a circuit does not affect the current in a circuit.

27.15 Calculate the dissipation rate of energy in a real battery.


27.16 Calculate the net rate of energy transfer in a real battery for current in the direction of the *emf* and in the opposite direction.

27-1 Single-Loop Circuits

To produce a steady flow of charge, you need a “charge pump,” a device that—by doing work on the charge carriers—maintains a potential difference between a pair of terminals. We call such a device an **emf device**, and the device is said to provide an **emf** \mathcal{E} , which means that it does work on charge carriers.

Figure shows an *emf* device (consider it to be a battery) that is part of a simple circuit containing a single resistance R . The *emf* device keeps one of its terminals (called the positive terminal and often labeled +) at a higher electric potential than the other terminal (called the negative terminal and labeled -). We can represent the *emf* of the device with an arrow that points from the negative terminal toward the positive terminal as in Figure. A small circle on the tail of the *emf* arrow distinguishes it from the arrows that indicate current direction.

emf = Electro Motive Force

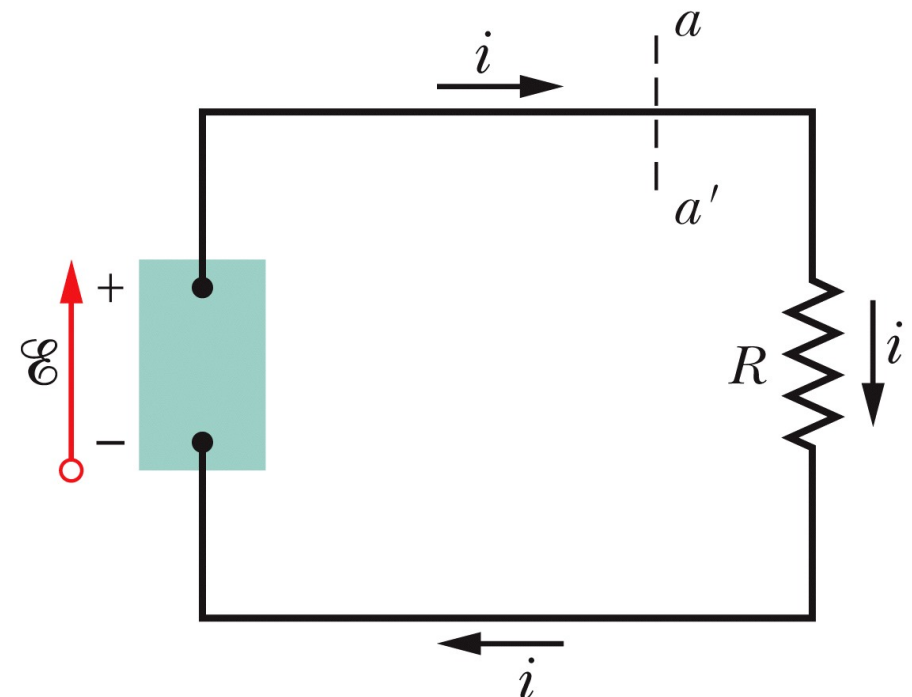

27-1 Single-Loop Circuits


An emf device does work on charges to maintain a potential difference between its output terminals. If dW is the work the device does to force positive charge dq from the negative to the positive terminal, then the **emf** (= work per unit charge) of the device is

$$\mathcal{E} = \frac{dW}{dq} \quad (\text{definition of } \mathcal{E}).$$

An **ideal emf device** is one that **lacks any internal resistance**. The potential difference between its terminals is equal to the *emf*.

A **real emf device** has internal resistance. The potential difference between its terminals is equal to the *emf* only if there is no current through the device.

$$\mathcal{E} \geq V$$

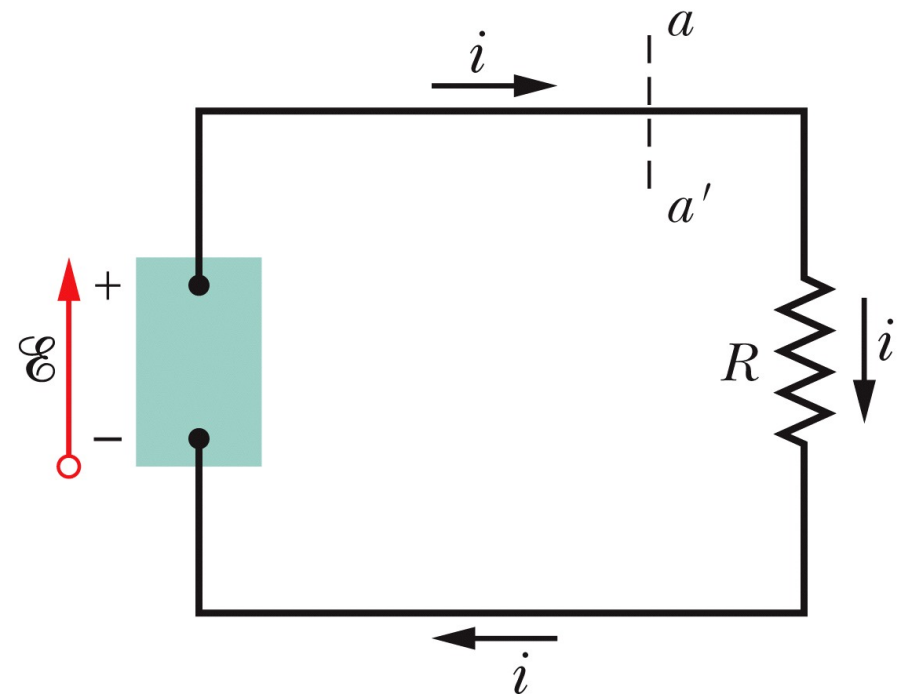

27-1 Single-Loop Circuits

Calculating Current in a Single-Loop Circuits

Energy Method

Equation, $P=i^2R$, tells us that in a time interval dt an amount of energy given by $i^2R dt$ will appear in the resistor (shown in the figure) as thermal energy. This energy is said to be **dissipated**. (Because we assume the wires to have negligible resistance, no thermal energy will appear in them.)

During the same interval, a charge $dq = i dt$ will have moved through battery B, and the work that the battery will have done on this charge is

$$dW = \mathcal{E} dq = \mathcal{E} i dt.$$


From the principle of conservation of energy, the work done by the (ideal) battery must equal the thermal energy that appears in the resistor:

$$\mathcal{E} i dt = i^2 R dt.$$

Which gives us

$$i = \frac{\mathcal{E}}{R}.$$

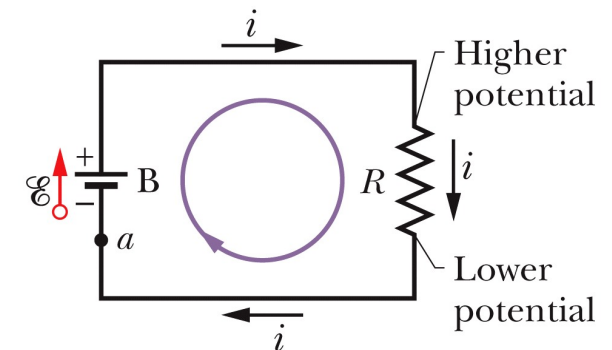The battery drives current through the resistor, from high potential to low potential.



Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

27-1 Single-Loop Circuits

Calculating Current in a Single-Loop Circuits

Potential Method

In the figure, let us start at point a , whose potential is V_a , and mentally walk clockwise around the circuit until we are back at point a , keeping track of potential changes as we move. Our starting point is at the low-potential terminal of the battery. **Because the battery is ideal, the potential difference between its terminals is equal to \mathcal{E} .** When we pass through the battery to the high-potential terminal, the change in potential is $+\mathcal{E}$.

After making a complete loop, our initial potential, as modified for potential changes along the way, must be equal to our final potential; that is,

$$V_a + \mathcal{E} - iR = V_a.$$


The value of V_a cancels from this equation, which becomes

$$\mathcal{E} - iR = 0.$$

Which gives us

$$i = \frac{\mathcal{E}}{R}.$$

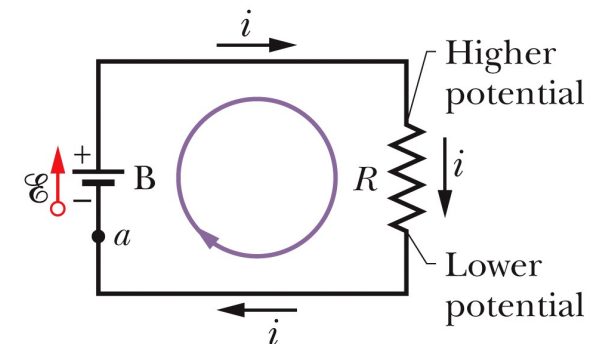The battery drives current through the resistor, from high potential to low potential.



27-1 Single-Loop Circuits

Calculating Current in a Single-Loop Circuits



LOOP RULE: The algebraic sum of the changes in potential encountered in a complete traversal of any loop of a circuit must be zero.




RESISTANCE RULE: For a move through a resistance in the direction of the current, the change in potential is $-iR$; in the opposite direction it is $+iR$.



EMF RULE: For a move through an ideal emf device in the direction of the emf arrow, the change in potential is $+\mathcal{E}$; in the opposite direction it is $-\mathcal{E}$.

27-1 Single-Loop Circuits

Internal Resistance

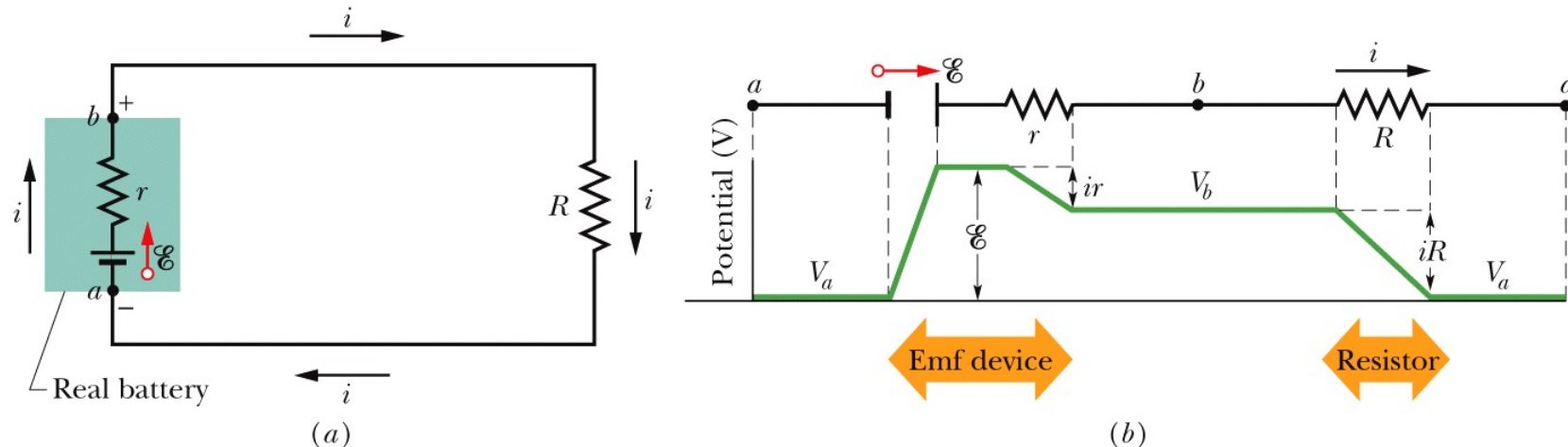

Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

Figure (a) shows **a real battery**, with internal resistance r , wired to an external resistor of resistance R . The internal resistance of the battery is the electrical resistance of the conducting materials of the battery and thus is an unremovable feature of the battery. Figure (b) shows graphically the changes in electric potential around the circuit. Now if we apply the loop rule clockwise beginning at point a , the changes in potential give us

$$\mathcal{E} - ir - iR = 0.$$

Solving for the current we find,

$$i = \frac{\mathcal{E}}{R + r}.$$

27-1 Single-Loop Circuits

Resistance in Series

Figure (a) shows three resistances connected in series to an **ideal battery** with $emf \mathcal{E}$. The resistances are connected one after another between a and b, and a potential difference is maintained across a and b by the battery. The potential differences that then exist across the resistances in the series produce identical currents i in them. To find total resistance R_{eq} in Fig. (b), we apply the loop rule to both circuits. For Fig. (a), starting at a and going clockwise around the circuit, we find

$$\mathcal{E} - iR_1 - iR_2 - iR_3 = 0,$$

$$i = \frac{\mathcal{E}}{R_1 + R_2 + R_3}.$$

For Fig. (b), with the three resistances replaced with a single equivalent resistance R_{eq} , we find

$$\mathcal{E} - iR_{eq} = 0,$$


$$i = \frac{\mathcal{E}}{R_{eq}}.$$

Equating them, we get,

$$R_{eq} = R_1 + R_2 + R_3.$$



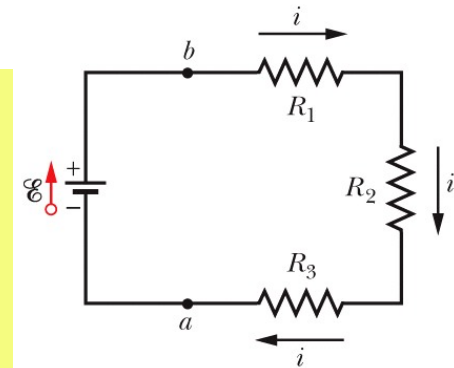
$$R_{eq} = \sum_{j=1}^n R_j \quad (n \text{ resistances in series}).$$



(a)

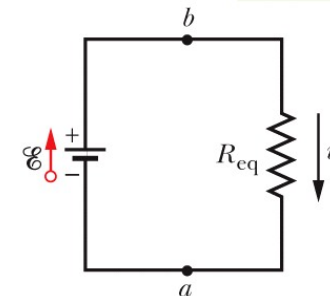Series resistors and their equivalent have the same current (“ser-i”).



(b)

27-1 Single-Loop Circuits

Resistance in Series



When a potential difference V is applied across resistances connected in series, the resistances have identical currents i . The sum of the potential differences across the resistances is equal to the applied potential difference V .




Resistances connected in series can be replaced with an equivalent resistance R_{eq} that has the same current i and the same *total* potential difference V as the actual resistances.



Checkpoint 2


In Fig. *a*, if $R_1 > R_2 > R_3$, rank the three resistances according to (a) the current through them and (b) the potential difference across them, greatest first.

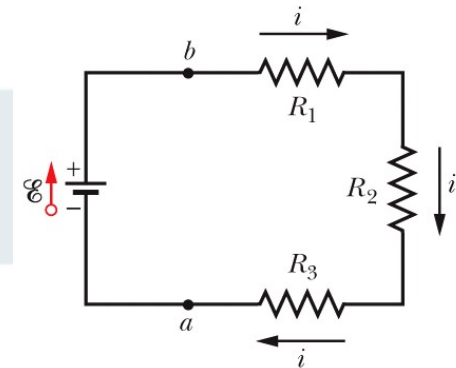Answer: (a) current is same for all resistors in series.
(b) V_1 , V_2 , and V_3



(a)

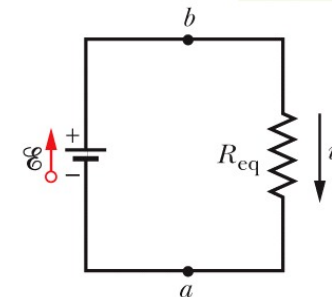Series resistors and their equivalent have the same current (“ser-i”).



(b)

27-1 Single-Loop Circuits

Potential Difference




To find the potential between any two points in a circuit, start at one point and traverse the circuit to the other point, following any path, and add algebraically the changes in potential you encounter.

The internal resistance reduces the potential difference between the terminals.

Potential Difference across a real battery: In the Figure, points a and b are located at the terminals of the battery. Thus, the potential difference $V_b - V_a$ is the terminal-to-terminal potential difference V across the battery and is given by:

$$V = \mathcal{E} - ir.$$

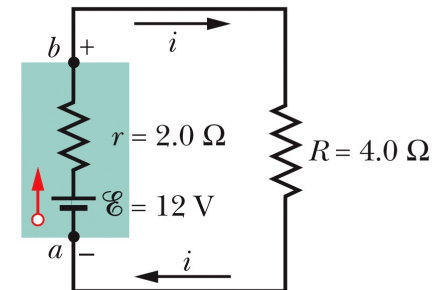

Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

Grounding a Circuit: Grounding a circuit usually means **connecting one point in the circuit to a conducting path to Earth's surface** (actually to the electrically conducting moist dirt and rock below ground)

Power of emf Device: The rate P_{emf} at which the *emf* device transfers energy both to the charge carriers and to internal thermal energy is

$$P_{emf} = i\mathcal{E} \quad (\text{power of emf device}).$$

Why grounding is necessary?


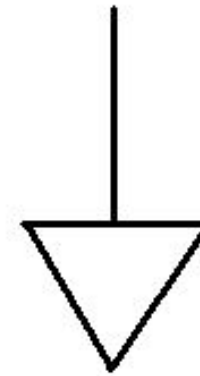
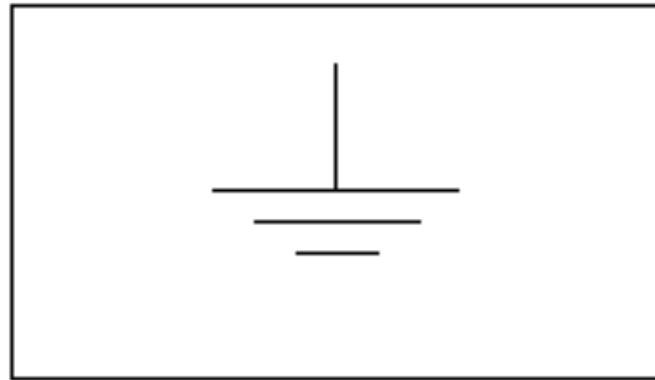


Figure 1 The Symbol for Earth Ground

Why grounding is necessary?

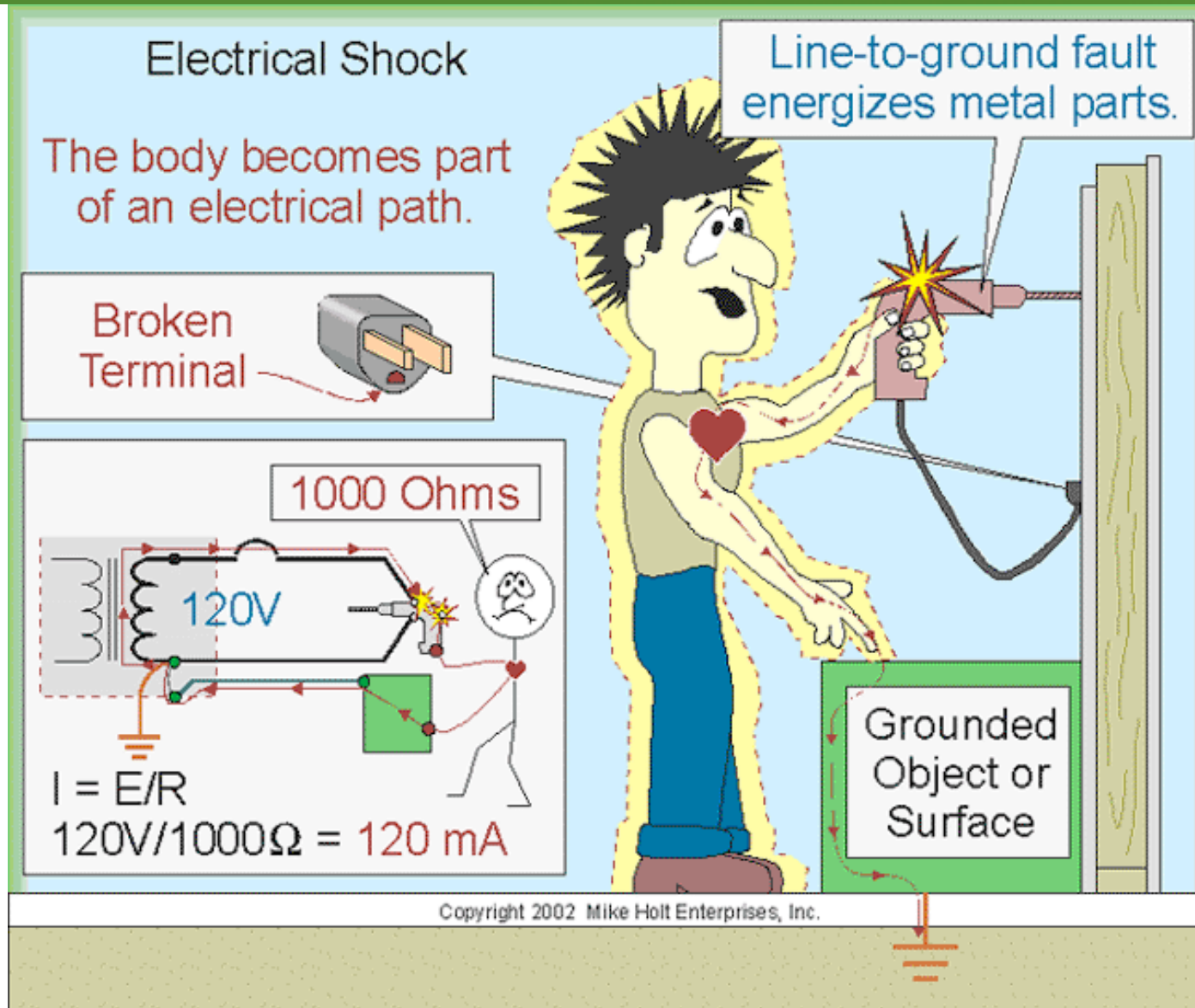

27-2 Multiloop Circuits

Learning Objectives

27.17 Apply the junction rule.

27.18 Draw a schematic diagram for a battery and three parallel resistors and distinguish it from a diagram with a battery and three series resistors.

27.19 Identify that resistors in parallel have the same potential difference across each, which is the same value as that of their equivalent resistor.

27.20 Calculate the resistance of the equivalent resistor of several resistors in parallel.

27.21 Identify that the total current through parallel resistors is the sum of the currents through the individual resistors.

27.22 For a circuit with a battery and some resistors in parallel and some in series, simplify the circuit in steps by finding equivalent resistors, until the current through the battery can be determined, and then reverse the steps to find the currents and potential differences of the individual resistors.

27-2 Multiloop Circuits

Learning Objectives (Continued)

27.23 If a circuit cannot be simplified by using equivalent resistors, identify the several loops in the circuit, choose names and directions for the currents in the branches, set up loop equations for the various loops, and solve these simultaneous equations for the unknown currents.

27.24 In a circuit with identical real batteries in series, replace them with a single ideal battery and a single resistor.

27.25 In a circuit with identical real batteries in parallel, replace them with a single ideal battery and a single resistor.

27-2 Multiloop Circuits




JUNCTION RULE: The sum of the currents entering any junction must be equal to the sum of the currents leaving that junction.

The current into the junction must equal the current out (charge is conserved).

Figure shows a circuit containing more than one loop. If we traverse the left-hand loop in a counterclockwise direction from point b, the loop rule gives us
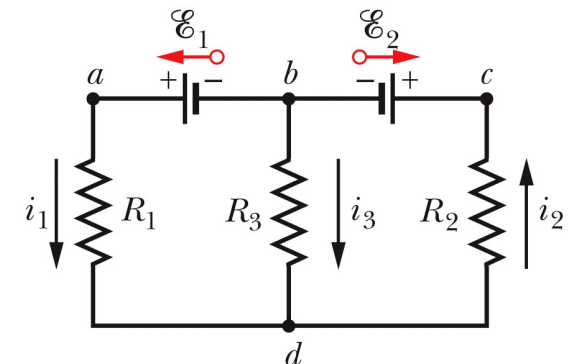
$$\mathcal{E}_1 - i_1 R_1 + i_3 R_3 = 0.$$



Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

If we traverse the right-hand loop in a counterclockwise direction from point b, the loop rule gives us

$$-i_3 R_3 - i_2 R_2 - \mathcal{E}_2 = 0.$$

If we had applied the loop rule to the big loop, we would have obtained (moving counterclockwise from b) the equation

$$\mathcal{E}_1 - i_1 R_1 - i_2 R_2 - \mathcal{E}_2 = 0.$$


which is the sum of two small loops equations.

27-2 Multi-Loop Circuits

Resistances in Parallel

Figure (a) shows three resistances connected in parallel to an ideal battery of $emf \mathcal{E}$. The applied potential difference V is maintained by the battery. Fig. b, the three parallel resistances have been replaced with an equivalent resistance R_{eq} .

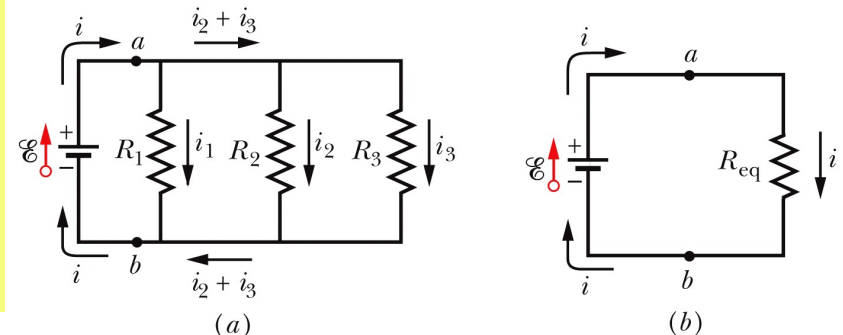Parallel resistors and their equivalent have the same potential difference ("par-V").



Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

To derive an expression for R_{eq} in Fig. (b), we first write the current in each actual resistance in Fig. (a) as

$$i_1 = \frac{V}{R_1}, \quad i_2 = \frac{V}{R_2}, \quad \text{and} \quad i_3 = \frac{V}{R_3},$$

where V is the potential difference between a and b . If we apply the junction rule at point a in Fig. (a) and then substitute these values, we find


$$i = i_1 + i_2 + i_3 = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right).$$

If we replaced the parallel combination with the equivalent resistance R_{eq} (Fig. b), we would have

$$i = \frac{V}{R_{eq}}.$$

and thus substituting the value of i from
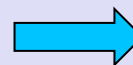
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}.$$



$$\frac{1}{R_{eq}} = \sum_{j=1}^n \frac{1}{R_j} \quad (n \text{ resistances in parallel}).$$

27-2 Multi-Loop Circuits

Resistance and capacitors

Table 27-1 Series and Parallel Resistors and Capacitors

Series	Parallel	Series	Parallel
<u>Resistors</u>		<u>Capacitors</u>	
$R_{\text{eq}} = \sum_{j=1}^n R_j$ Eq. 27-7 Same current through all resistors	$\frac{1}{R_{\text{eq}}} = \sum_{j=1}^n \frac{1}{R_j}$ Eq. 27-24 Same potential difference across all resistors	$\frac{1}{C_{\text{eq}}} = \sum_{j=1}^n \frac{1}{C_j}$ Eq. 25-20 Same charge on all capacitors	$C_{\text{eq}} = \sum_{j=1}^n C_j$ Eq. 25-19 Same potential difference across all capacitors

Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.



Checkpoint 4

A battery, with potential V across it, is connected to a combination of two identical resistors and then has current i through it. What are the potential difference across and the current through either resistor if the resistors are (a) in series and (b) in parallel?

Answer: (a) Potential difference across each resistor: $V/2$
 Current through each resistor: i
 (b) Potential difference across each resistor: V
 Current through each resistor: $i/2$

27-3 The Ammeter and The Voltmeter


WILEY

Learning Objectives

27.26 Explain the use of an ammeter and a voltmeter, including the resistance required of each in order not to affect the measured quantities.

27-3 The Ammeter and The Voltmeter

WILEY

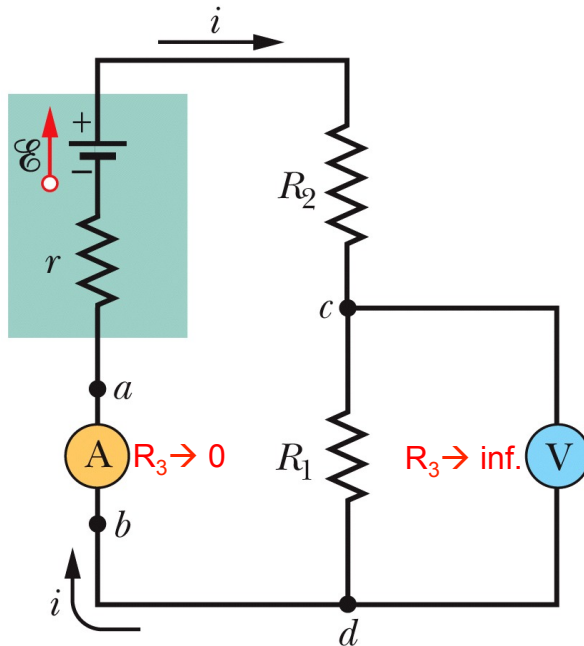

Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

An instrument used to measure currents is called an **ammeter**. To measure the current in a wire, you usually have to break or cut the wire and insert the ammeter so that the current to be measured passes through the meter. In the figure, ammeter A is set up to measure current i . It is essential that the resistance R_A of the ammeter be very much smaller than other resistances in the circuit. Otherwise, the very presence of the meter will change the current to be measured.

$$i = \frac{\mathcal{E}}{R_1 + R_2 + R_3} \rightarrow 0$$

A meter used to measure potential differences is called a **voltmeter**. To find the potential difference between any two points in the circuit, the voltmeter terminals are connected between those points without breaking or cutting the wire. In the Figure, voltmeter V is set up to measure the voltage across R_1 . It is essential that the resistance R_V of a voltmeter be very much larger than the resistance of any circuit element across which the voltmeter is connected. This is to insure that only a negligible current passes through the voltmeter, otherwise, the meter alters the potential difference that is to be measured.

27-4 *RC* Circuits

Learning Objectives

27.27 Draw schematic diagrams of charging and discharging *RC* circuits.

27.28 Write the loop equation (a differential equation) for a charging *RC* circuit.

27.29 Write the loop equation (a differential equation) for a discharging *RC* circuit.

27.30 For a capacitor in a charging or discharging *RC* circuit, apply the relationship giving the charge as a function of time.

27.31 From the function giving the charge as a function of time in a charging or discharging *RC* circuit, find the capacitor's potential difference as a function of time.

27.32 In a charging or discharging *RC* circuit, find the current through and potential difference across the resistor as functions of time.

27.33 Calculate the capacitive time constant τ .

27-4 *RC* Circuits

Learning Objectives (continued)

27.34 For a charging *RC* circuit and a discharging *RC* circuit, determine the capacitor's charge and potential difference at the start of the process and then a long time later.

27-4 RC Circuits

Charging a capacitor: The capacitor of capacitance C in the figure is initially uncharged. To charge it, we close switch S on point a . This completes an RC series circuit consisting of the capacitor, an ideal battery of $emf \mathcal{E}$, and a resistance R .

The charge on the capacitor increases according to

$$q = C\mathcal{E}(1 - e^{-t/RC}) \quad (\text{charging a capacitor}).$$

in which $C\mathcal{E} = q_0$ is the equilibrium (final) charge and $RC = \tau$ is the **capacitive time constant** of the circuit. During the charging, the current is


$$i = \frac{dq}{dt} = \left(\frac{\mathcal{E}}{R}\right)e^{-t/RC} \quad (\text{charging a capacitor}).$$

And the voltage is:

$$V_C = \frac{q}{C} = \mathcal{E}(1 - e^{-t/RC}) \quad (\text{charging a capacitor}).$$


The product RC is called the **capacitive time constant** of the circuit and is represented with the symbol τ .
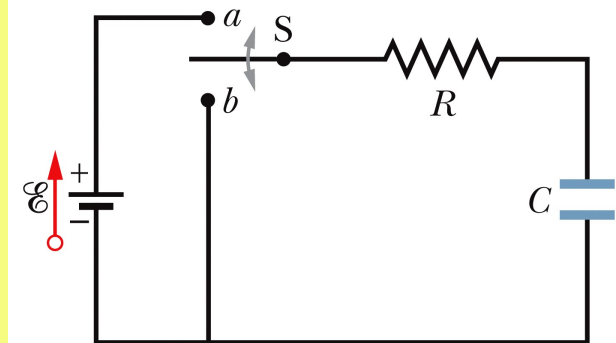
$$\tau = RC \quad (\text{time constant}).$$



Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

Figure: RC circuit

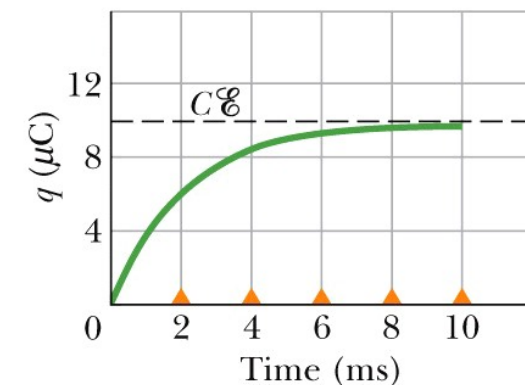

Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

The plot shows the buildup of charge on the capacitor of the above figure.

27-4 RC Circuits

Discharging a capacitor: Assume now that the capacitor of the figure is fully charged to a potential V_0 equal to the emf \mathcal{E} of the battery. At a new time $t=0$, switch S is thrown from a to b so that the capacitor can discharge through resistance R .


When a capacitor discharges through a resistance R , the charge on the capacitor decays according to

$$q = q_0 e^{-t/RC} \quad (\text{discharging a capacitor}),$$

where $q_0 (=CV_0)$ is the initial charge on the capacitor.


During the discharging, the current is
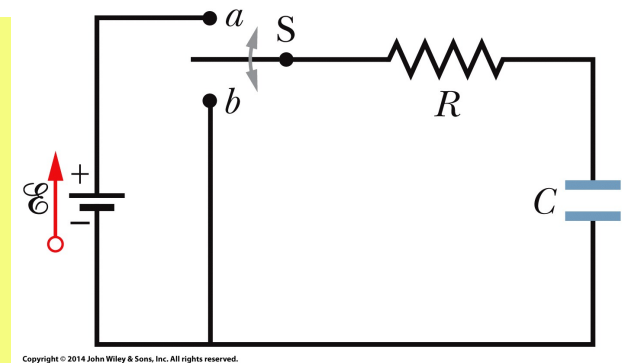
$$i = \frac{dq}{dt} = -\left(\frac{q_0}{RC}\right)e^{-t/RC} \quad (\text{discharging a capacitor}).$$



Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.

Figure: RC circuit

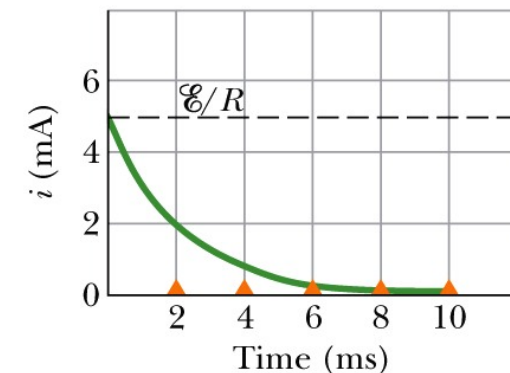

Copyright © 2014 John Wiley & Sons, Inc. All rights reserved.



A capacitor that is being charged initially acts like ordinary connecting wire relative to the charging current. A long time later, it acts like a broken wire.

A plot shows the decline of the charging current in the circuit of the above figure.

27 Summary

Emf

- The **emf** (work per unit charge) of the device is

$$\mathcal{E} = \frac{dW}{dq} \quad (\text{definition of } \mathcal{E}). \quad \text{Eq. 27-1}$$

Single-Loop Circuits

- Current in a single-loop circuit:

$$i = \frac{\mathcal{E}}{R + r}, \quad \text{Eq. 27-4}$$

Power

- The rate P of energy transfer to the charge carriers is $P = iV$. Eq. 27-14

- The rate P_r at which energy is dissipated as thermal energy in the battery is $P_r = i^2 r$. Eq. 27-16

- The rate P_{emf} at which the chemical energy in the battery changes is

$$P_{\text{emf}} = i\mathcal{E}. \quad \text{Eq. 27-17}$$

Series Resistance

- When resistances are in series

$$R_{\text{eq}} = \sum_{j=1}^n R_j \quad \text{Eq. 27-7}$$

Parallel Resistance

- When resistances are in parallel

$$\frac{1}{R_{\text{eq}}} = \sum_{j=1}^n \frac{1}{R_j} \quad \text{Eq. 27-24}$$

RC Circuits

- The charge on the capacitor increases according to Eq. 27-33

$$q = C\mathcal{E}(1 - e^{-t/RC})$$

- During the charging, the current is

$$i = \frac{dq}{dt} = \left(\frac{\mathcal{E}}{R} \right) e^{-t/RC} \quad \text{Eq. 27-34}$$

- During the discharging, the current is

$$i = \frac{dq}{dt} = - \left(\frac{q_0}{RC} \right) e^{-t/RC} \quad \text{Eq. 27-40}$$